
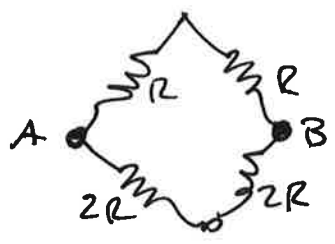


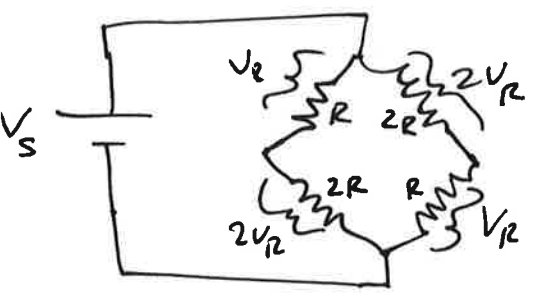① a) based on symmetry, there is no voltage drop across the center R



- from top to bottom, same net resistance going on L or R branch
- thus, I same thru L or R
- thus, voltage at A and B must be the same


b) still, net current in either branch is the same!
 - the R's have half the voltage drop of the 2R's
 - we can just use proportions. Let V_R be the voltage drop on an "R"



the voltage splits into a 2:1 ratio in each branch. That means the net V_s is split into 3. The 2R resistor takes $\frac{2V_s}{3}$, the R takes $\frac{V_s}{3}$

⇒ across the middle, we have the difference between $\frac{V_s}{3}$ and $\frac{2V_s}{3}$, or $\Delta V = \frac{2V_s}{3} - \frac{V_s}{3} = \frac{V_s}{3}$ with the LHS being positive

c) redraw

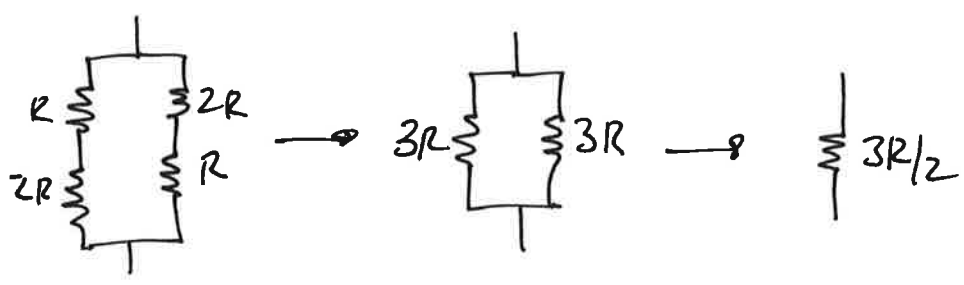

equivalent is $\frac{3R}{2}$, so

$$I = \frac{V_s}{R_{eq}} = \frac{V_s}{3R/2} = \frac{2V_s}{3R}$$

~~$$I = \frac{V_s}{R_{eq}} = \frac{V_s}{3R/2} = \frac{2V_s}{3R} = \frac{2V_s}{3R}$$~~

2

a) $R = \frac{\rho l}{A} = \frac{\rho l}{\pi (\frac{d}{2})^2} \approx \boxed{0.0611 \Omega}$

b) $I = \frac{\Delta V}{R} \approx \boxed{1963 A}$ outlandishly large. a household breaker handles 15A typically.


c) $P = I \Delta V = I^2 R = 2.3 \times 10^5 W = \boxed{235.5 kW}$ This will vaporize the wire. It was stupid to connect a bare wire to our 120V source, and something is broken now.

d) $I = n g v_d A$ $l = v_d t$ (not covered)

$t = \frac{l}{v_d} = \frac{l}{I / n g A} = \frac{l n g \pi d^2}{4 I} \approx \boxed{16.2 \text{ sec}}$

note $A = \frac{\pi d^2}{4}$ note $g = e$

③

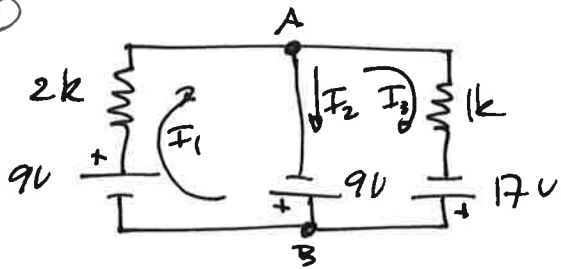

LHS loop: $9V - 2000I_1 + 9V = 0 \Rightarrow 18 = 2000I_1 \Rightarrow I_1 = 9mA$

RHS loop: $9V - 17V + 1000I_3 = 0 \Rightarrow 8V = 1000I_3 \Rightarrow I_3 = 8mA$

top or bottom junction (A or B): $I_1 = I_2 + I_3$

$$\Rightarrow I_2 = I_1 - I_3 = 9mA - 8mA = 1mA$$

4. from LHS box:

$$R_{ab} = 20 \text{ par to } (30+50) \Rightarrow \frac{1}{R_{ab}} = \frac{1}{20} + \frac{1}{80} = \frac{1}{16} \Rightarrow R_{ab} = 16\Omega$$

Similarly, $R_{ac} = 25$ and $R_{bc} = 21$

note now $R_{ab} = R_1 + R_2$ $R_{ac} = R_1 + R_3$ $R_{bc} = R_2 + R_3$

we have then

$$\left. \begin{array}{l} R_1 + R_3 = 25 \\ R_1 + R_2 = 16 \\ R_2 + R_3 = 21 \end{array} \right\} \begin{array}{l} R_3 - R_2 = 9 \\ R_3 + R_2 = 21 \end{array} \rightarrow 2R_3 = 30 \Rightarrow R_3 = 15$$

$$R_1 + R_3 = 25 \Rightarrow R_1 = 10$$

$$R_2 + R_3 = 21 \Rightarrow R_2 = 6$$

$$\begin{array}{l} R_1 = 10\Omega \\ R_2 = 6\Omega \\ R_3 = 15\Omega \end{array}$$