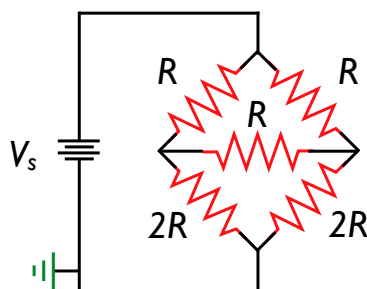


Exam 2


Instructions

1. Solve three of the four problems below.
2. All problems have equal weight. Do your work on separate sheets.
3. You are allowed 1 sheet of standard 8.5×11 in paper and a calculator.

□ **1. Symbolic solution (a)** Consider the “bridge” arrangement of resistors in Fig. 1a. This is an example of an arrangement which cannot be reduced to a single equivalent using only our rules for series and parallel resistance. In this circuit, what is the current through the central (horizontal) resistor? **(b)** In Fig. 1b, two resistors have been swapped, and the central resistor removed. What voltage does the voltmeter read in this case, in terms of the source voltage V_s ? (You do not need to know R ; think about proportions.) **(c)** For the circuit in Fig. 1b, what is the total current leaving the battery?



(a) Find I for the central resistor.

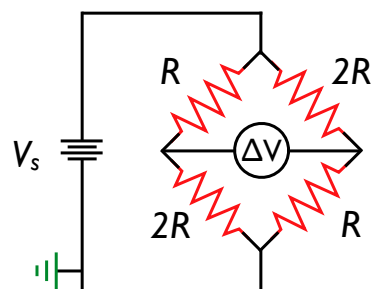

(b) What does the voltmeter read?

Figure 1: Problem 1

□ **2.** A heater coil uses a 3 m length of wire which is 1 mm diameter (approximately 18 gauge). The wire is made of copper with a resistivity of $\rho = 1.6 \times 10^{-8} \Omega \cdot \text{m}$. **(a)** What is the resistance of the wire? The area of a circle is $\pi r^2 = \pi d^2/4$. **(b)** What is the current through the heater coil if it is connected to a 120 V voltage source? **(c)** What is the power dissipated in the heater? **(d)** If the density of electrons in copper is $n = 8.47 \times 10^{28} / \text{m}^3$, how long does it take a single electron to make the 3 m journey through the heater?

- 3. What is the current through the center 9 V battery in the circuit below?


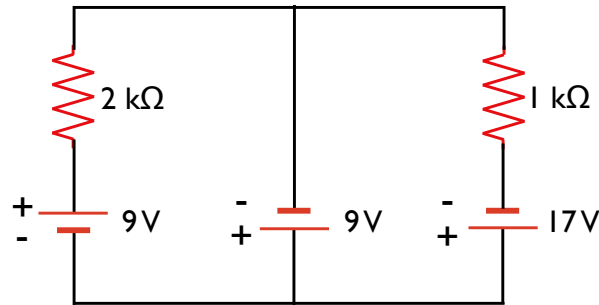


Figure 2: Problem 2

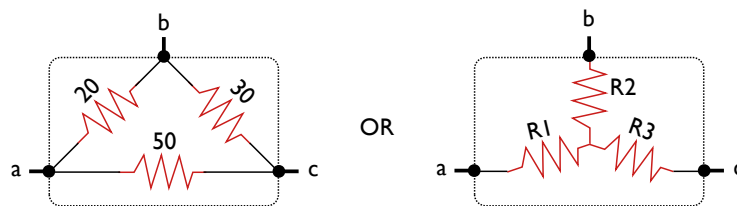- 4. Referring to the figure at left below, a black box with three terminals, a , b , and c , contains nothing but three resistors and connecting wire. You measure the resistance between pairs of terminals, R_{ab} , R_{ac} , and R_{bc} .

What resistances R_1 , R_2 , and R_3 for the box at right below would give the same measurements, R_{ab} , R_{ac} , and R_{bc} ?



Constants:

$$k_e \equiv 1/4\pi\epsilon_o = 8.98755 \times 10^9 \text{ N} \cdot \text{m}^2 \cdot \text{C}^{-2}$$

$$\epsilon_o = 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2$$

$$e = 1.60218 \times 10^{-19} \text{ C}$$

Current/resistors/circuits:

$$I = \frac{\Delta Q}{\Delta t} = nqAv_d$$

$$J = \frac{I}{A} = nqv_d$$

$$v_d = -\frac{e\tau}{m}E \quad \tau = \text{scattering time}$$

$$\rho = \frac{m}{ne^2\tau}$$

$$\Delta V = \frac{\rho l}{A}I = RI$$

$$R = \frac{\Delta V}{I} = \frac{\rho l}{A}$$

$$\mathcal{P} = I\Delta V = I^2R = \frac{[\Delta V]^2}{R} \text{ power}$$

$$R_{\text{eq, series}} = R_1 + R_2$$

$$\frac{1}{R_{\text{eq, par}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

| Power | Prefix | Abbreviation |
|------------|--------|--------------|
| 10^{-12} | pico | p |
| 10^{-9} | nano | n |
| 10^{-6} | micro | μ |
| 10^{-3} | milli | m |
| 10^{-2} | centi | c |
| 10^3 | kilo | k |
| 10^6 | mega | M |
| 10^9 | giga | G |
| 10^{12} | tera | T |

| Unit | Symbol | equivalent to |
|---------------|---------------------------------------|--|
| newton | N | $\text{kg} \cdot \text{m}/\text{s}^2$ |
| joule | J | $\text{kg} \cdot \text{m}^2/\text{s}^2 = \text{N} \cdot \text{m}$ |
| watt | W | $\text{J}/\text{s} = \text{m}^2 \cdot \text{kg}/\text{s}^3$ |
| coulomb | C | A·s |
| amp | A | C/s |
| volt | V | $\text{W}/\text{A} = \text{m}^2 \cdot \text{kg}/\text{s}^3 \cdot \text{A}$ |
| farad | F | $\text{C}/\text{V} = \text{A}^2 \cdot \text{s}^4/\text{m}^2 \cdot \text{kg}$ |
| ohm | Ω | $\text{V}/\text{A} = \text{m}^2 \cdot \text{kg}/\text{s}^3 \cdot \text{A}^2$ |
| tesla | T | $\text{Wb}/\text{m}^2 = \text{kg}/\text{s}^2 \cdot \text{A}$ |
| electron volt | eV | $1.6 \times 10^{-19} \text{ J}$ |
| - | $1 \text{ T} \cdot \text{m}/\text{A}$ | $1 \text{ N}/\text{A}^2$ |
| - | $1 \text{ T} \cdot \text{m}^2$ | $1 \text{ V} \cdot \text{s}$ |
| - | $1 \text{ N}/\text{C}$ | $1 \text{ V}/\text{m}$ |