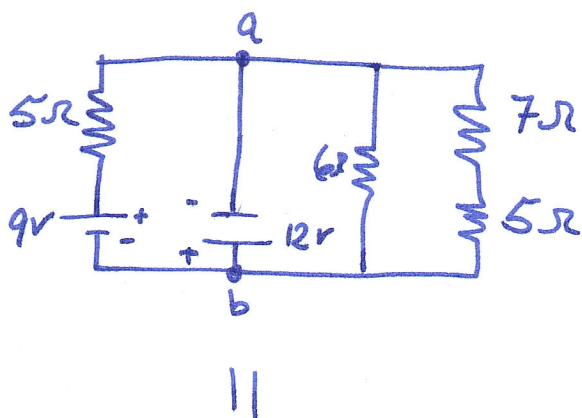



①

works $\therefore$ no battery w/ 6Ω and no R w/ $12V$!

* shortcut: must have $V_a - V_b = 12V$
 $\Rightarrow 12V$ across 6Ω too! $\therefore I = \frac{12}{6} = 2A$

Longway

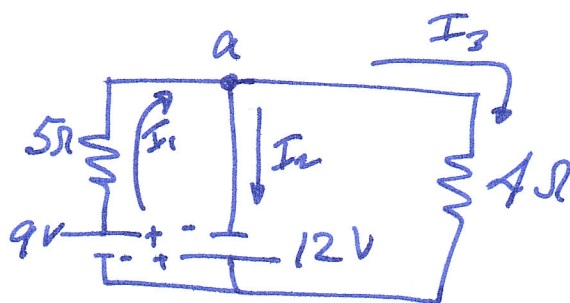- combine 5Ω & 7Ω (series) $\Rightarrow 12\Omega$
- combine that w/ 6Ω (par) $\Rightarrow 4\Omega$



- assign currents
- our choice, w/ conv. chg @ a gives $I_1 = I_2 + I_3$
- note I_2 will not matter, goes thru no resistor!

New walk loops.


(1) LHS loop, from a, CW

$$+12V + 9V - 5I_2 = 0 \quad \text{or} \quad 5I_2 = 21 \quad I_2 \approx 4.2A$$

(2) RHS loop, from a, CW

$$-4I_3 - 12 = 0 \Rightarrow I_3 = -3A \quad (\text{dir. was wrong})$$

4Ω is really 3 resistors

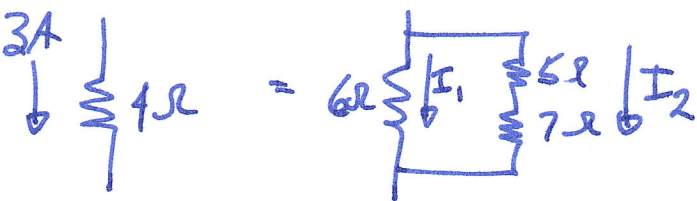


$$\Delta V_4 = 3A \cdot 4\Omega = 12V = \Delta V \text{ on } 6\Omega$$

$$I_1 = \text{thru } 6\Omega = \frac{12V}{6\Omega} = 2A$$

2A thru 6Ω

2

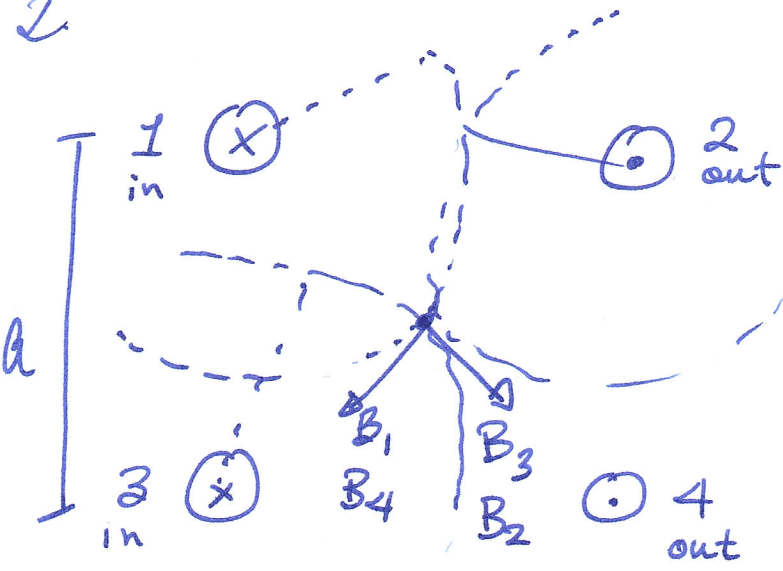

- draw circles on wires that intersect center
- field is tangent to circle & follows RH rule

- Do this: B_1, B_4 point down & to left at 45°
 B_2, B_3 point down & to right at 45°
- by symmetry, all cancel in horz. direction - equal & opposite
- mag same for all, $B_1 = B_2 = B_3 = B_4 = \frac{\mu_0 I}{2\pi(a\sqrt{2}/2)} = B$
- vertical component of any one is $B \sin 45 = B \frac{\sqrt{2}}{2}$
- we have 4 of these

$$B_{net} = 4B \sin 45 = \frac{4\mu_0 I}{2\pi a \sqrt{2}/2} \cdot \frac{\sqrt{2}}{2} = \frac{2\mu_0 I}{\pi a}$$



$$\sim 4.4 \mu T$$

3. a) if proton moves CCW in circle, B must be into page
(RH rule)

b) radius given by force balance $F_B = F_{\text{centr}}$ for either

$$qvB = \frac{mv^2}{r} \Rightarrow r = \frac{mv}{qB}$$

$$r_e = \frac{m_e v_e}{eB} = r_p = \frac{m_p v_p}{eB}$$


$$\Rightarrow \boxed{\frac{v_e}{v_p} = \frac{m_p}{m_e}}$$

4.) b, c) inductor pass low freq, cap shorts high freq
 $\Rightarrow$ this passes low freq speech

c) $L_{\text{tot}} = 10.26 \text{ mH}$ $C = 22 \text{ nF}$

cutoff: $X_L = X_C \quad \omega L = \frac{1}{\omega C} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}} \approx 10 \text{ kHz} \quad \text{nicely btw voice and data}$$

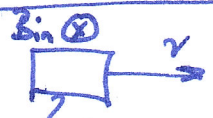5)  a) motional: $\mathcal{E} = qvB = q \frac{\Delta V}{l}$
cond. $\Rightarrow \Delta V = Blv \approx 2.55 \text{ mV}$
88 kph = 24.4 m/s

b) top view at left...
 $F_{\text{on } \oplus}$ is up
 $\Rightarrow$ driver's side is $\oplus$