

UNIVERSITY OF ALABAMA
Department of Physics and Astronomy

PH 102-2 / LeClair

Spring 2008

Problem Set 4: Current & Resistance


Instructions:

- Answer all questions below. Show your work for full credit.
- Due before 5pm, 11 Feb 2008
- Problem sets may be turned in *via* email or hard copy
- Hard copies may be left in Dr. LeClair's mailbox (Gallalee 206) or office (Bevill 228)
- You may collaborate, but everyone must turn in their own work

1. 10 points. An 11.0 W compact fluorescent bulb is designed to produce the same illumination as a conventional 40.0 W incandescent bulb. Assuming a cost of \$0.0800/kWh for electrical power, how much money does the user of the fluorescent bulb save over 100 hr of use?

2. 5 points. If the voltage at the terminals of an automobile battery drops from 12.3 to 9.8 V when a $0.5\ \Omega$ resistor is connected across the battery, what is the internal resistance?

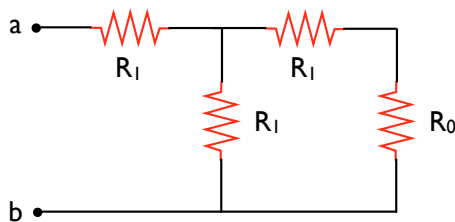3. 15 points. In the circuit below, if R_0 is given, what value must the R_1 have for the equivalent resistance between the two terminals a and b to be R_0 ?



4. 10 points. An aluminum wire with a cross-sectional area of $4.00 \times 10^{-6}\ \text{m}^2$ carries a current of 5.00 A. Find the drift speed of the electrons in the wire. The density of aluminum is $2.70\ \text{g/cm}^3$; assume each Al atom provides a single electron for conduction. *Hint: how many atoms per unit volume are there? How many charges per unit volume does this imply?*


5. 15 points. A regular tetrahedron is a pyramid with a triangular base. Six $14.0\ \Omega$ resistors are placed along its six edges, with junctions at its four vertices. A 9.0 V battery is connected to any two of the vertices. **(a)** Find the equivalent resistance of the tetrahedron between these vertices. **(b)** Find the current in the battery.

6. 5 points. A conductor of uniform radius 1.2 cm carries a current of 3.0 A produced by an electric field of 120 V/m. What is the resistivity of the material?

7. 5 points. A common 1.5 V "D" cell battery can supply about 0.100 A of current for about 100 h, hence its capacity rating of 10000 mA·h. How high could you lift yourself with one "D" cell battery powering a 50% efficient winch? Note that your mass in kg can be found by dividing your weight in pounds by 2.2.

8. **10 points.** If the current carried by a conductor is doubled, what happens to the (a) charge carrier density? (b) Current density? (c) Electron drift velocity? (d) Average time between collisions?

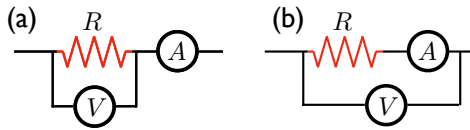9. **15 points.** The value of an unknown resistor is to be determined with an ammeter and voltmeter, as shown below. The ammeter has an internal resistance of $0.500\ \Omega$, and the voltmeter has an internal resistance of $20\ \text{k}\Omega$. Within what range of actual values of R will the measured values be correct to within 5% if the measurement is made using the circuit shown in (a) and (b)?



10. **10 points.** All of the resistors in the figure below are equal, and have a value R . What is the equivalent resistance between the end points?

