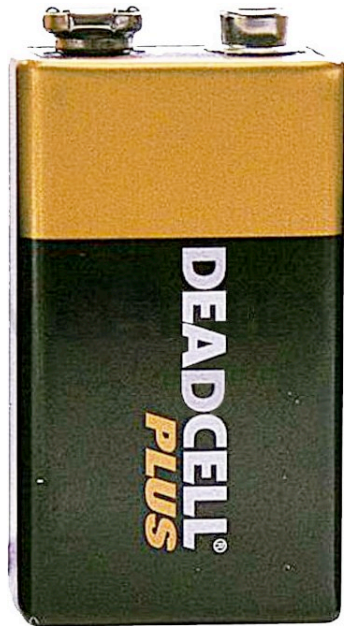


today: dc circuits


Friday's quiz:

- 5 question multiple choice. Only two require calculation.
- Formulas given.
- Electric forces & fields, current & resistance.
- Nothing beyond material from Wednesday's lecture.

real battery = ideal battery + R




=

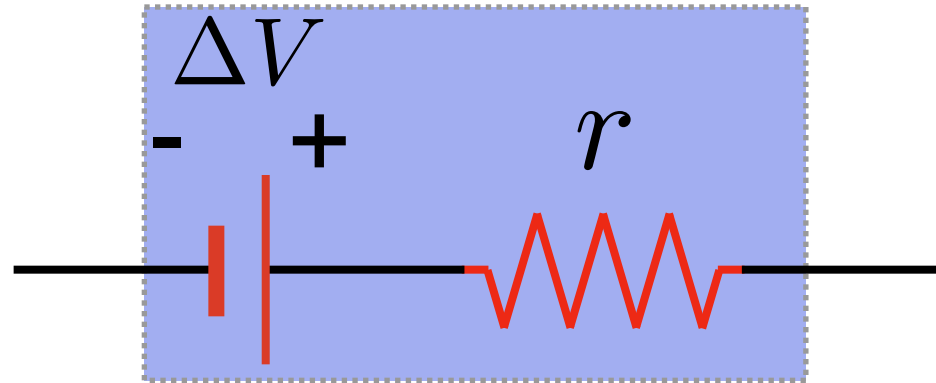


actual circuit has a parasitic r




b)

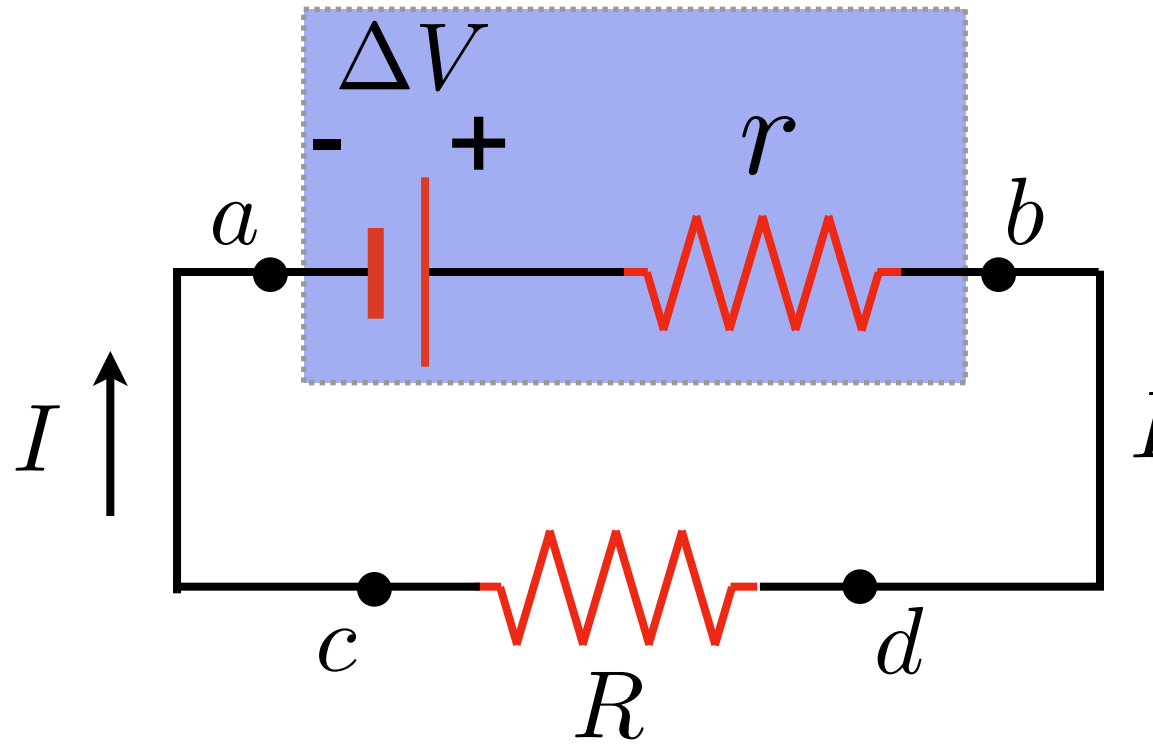

real current sources

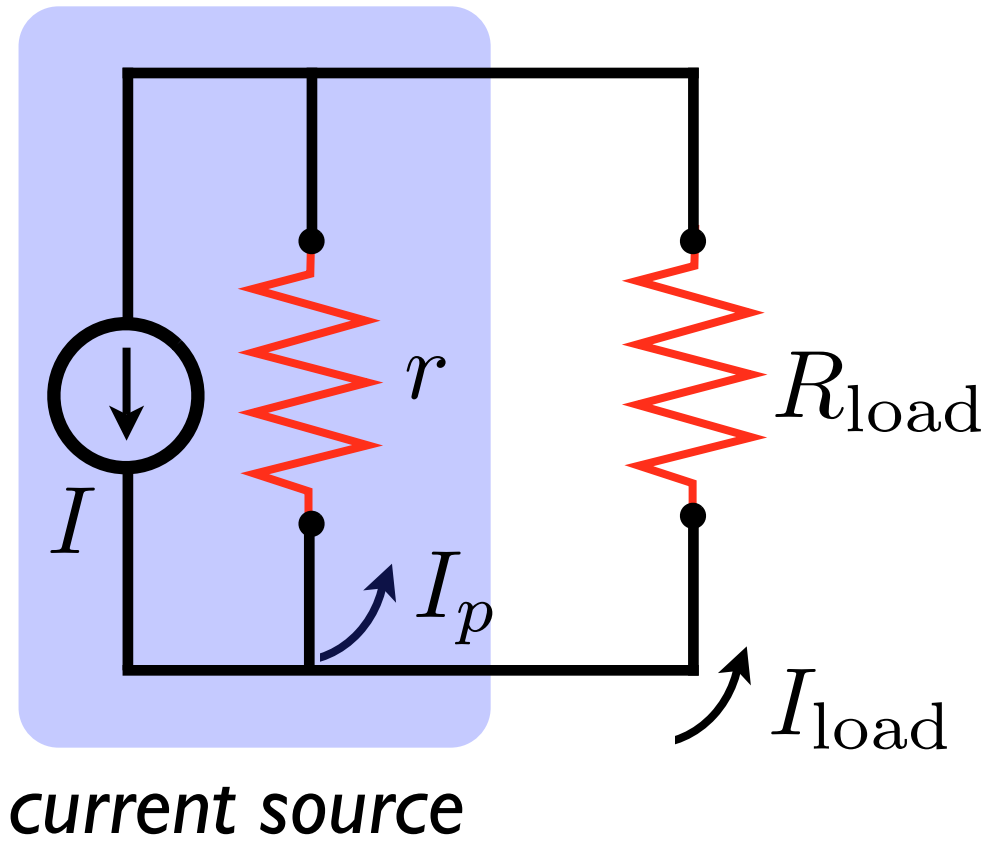

series resistors: conservation of energy

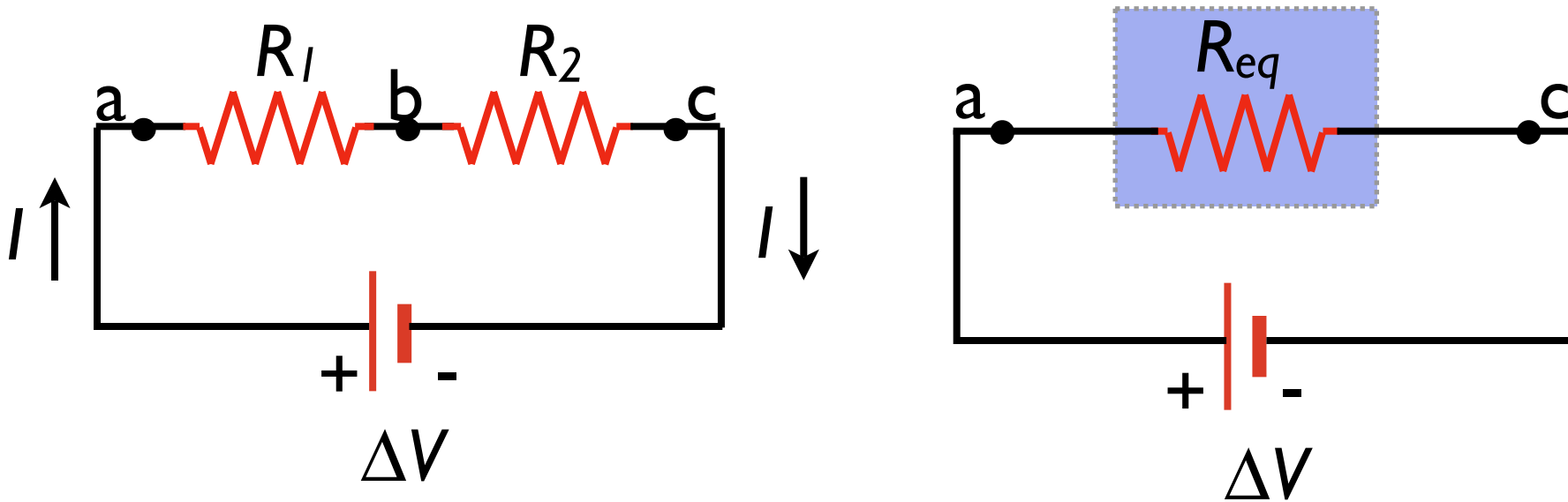

Two Resistors in Series:


$$R_{eq} = R_1 + R_2$$

Three or More Resistors in Series:


$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

The current through resistors in series is the same.

voltage divider

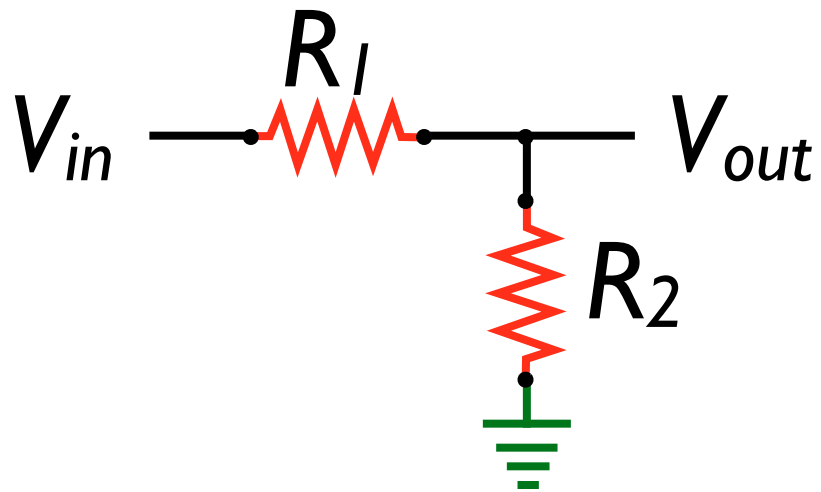

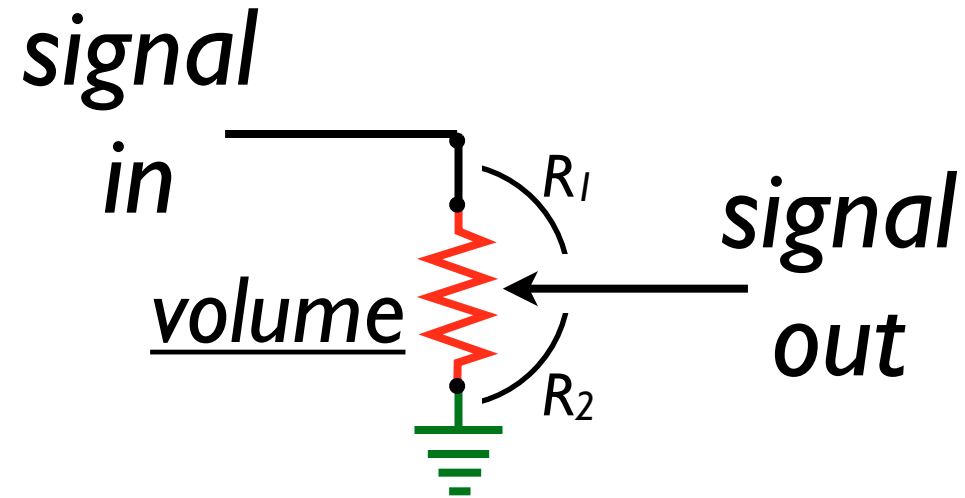
$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$




parallel resistors: conservation of charge

$$\Delta V_1 = \Delta V_2 = \Delta V$$

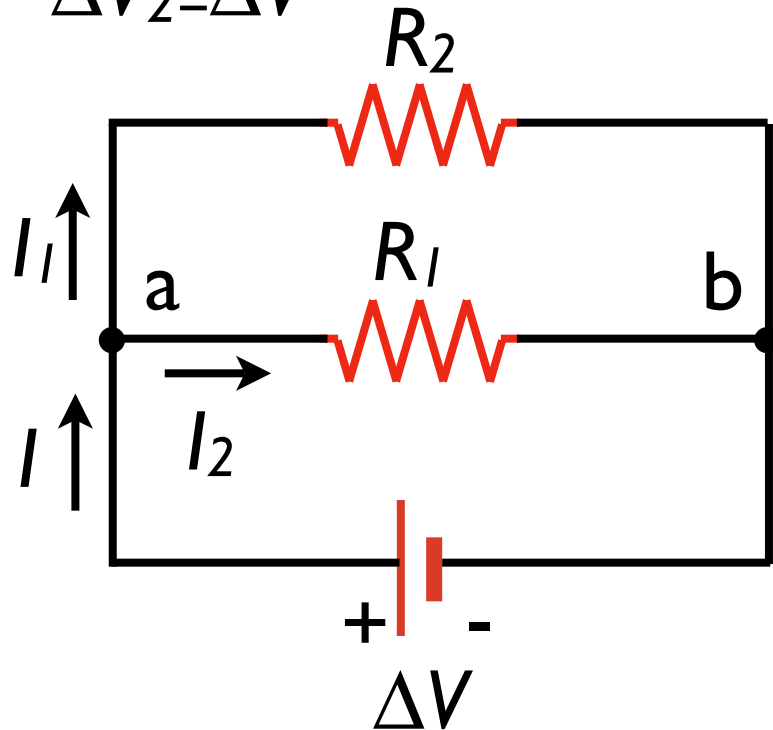
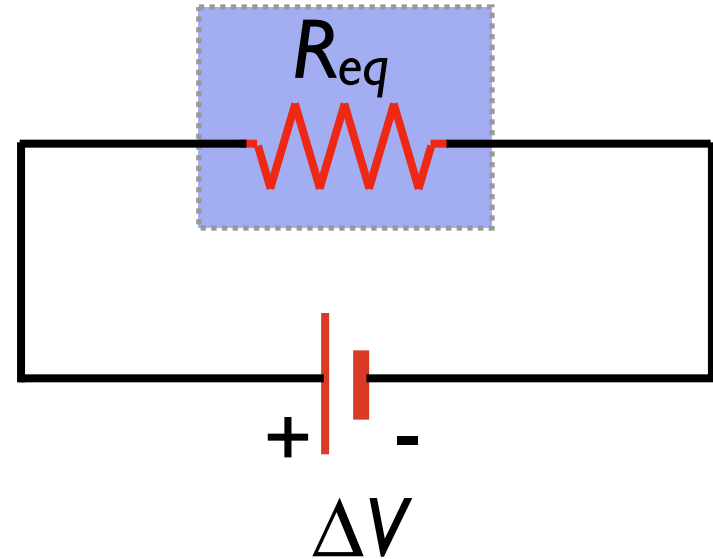
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Two Resistors in Parallel:





$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Three or More Resistors in Parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$


current divider

more complex arrangements

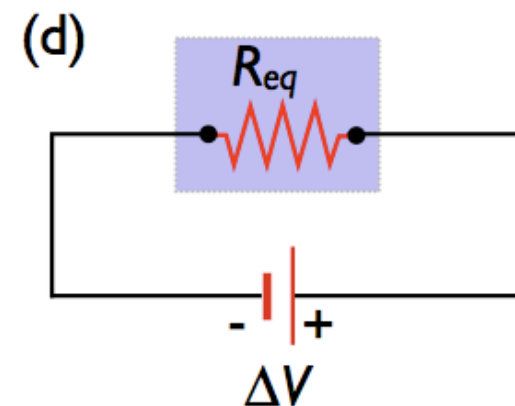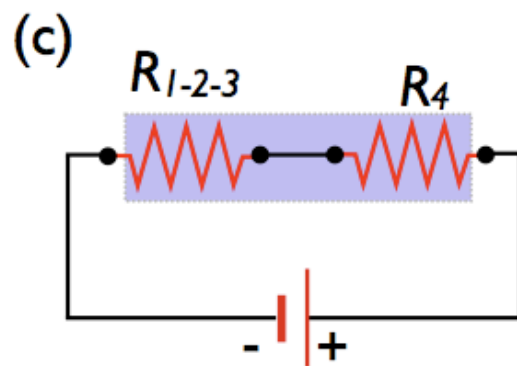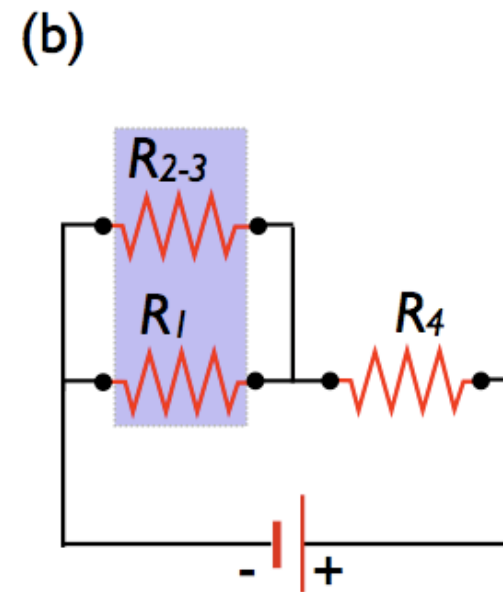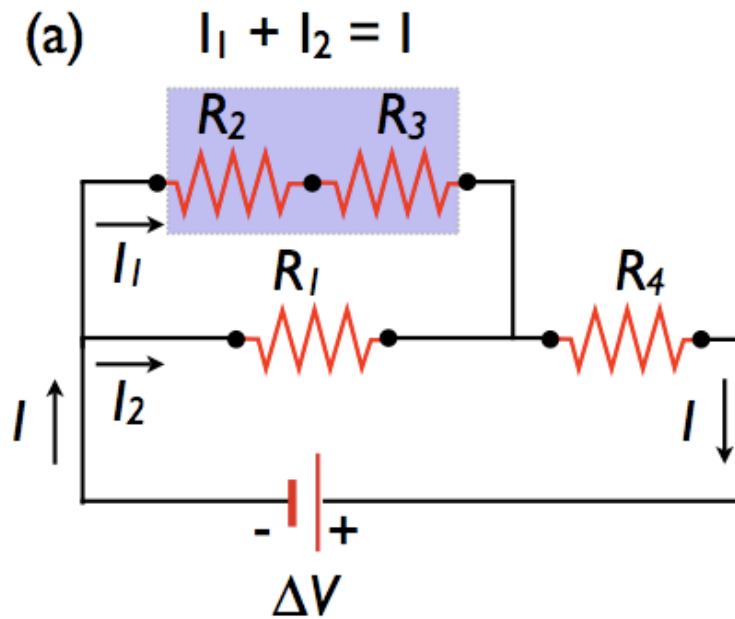


measuring voltage

a)

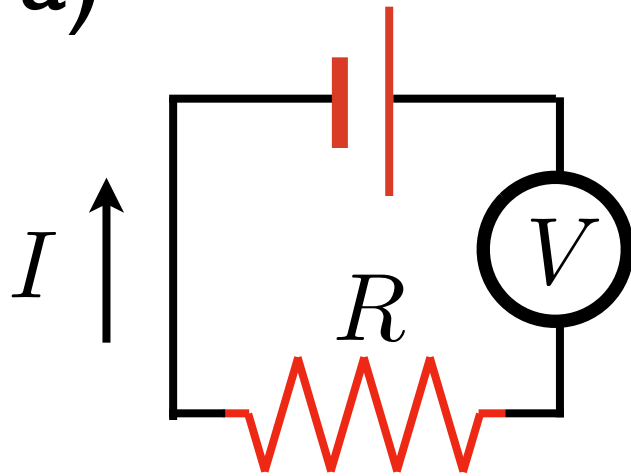

! INCORRECT !


b)

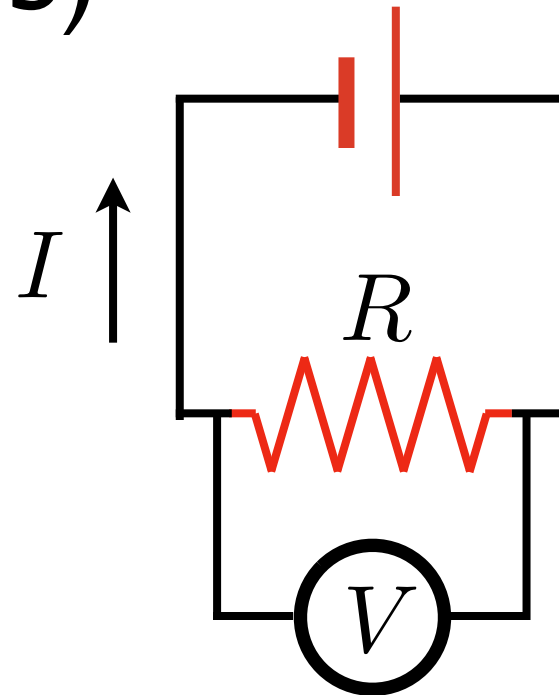


CORRECT

real voltmeters

(a)

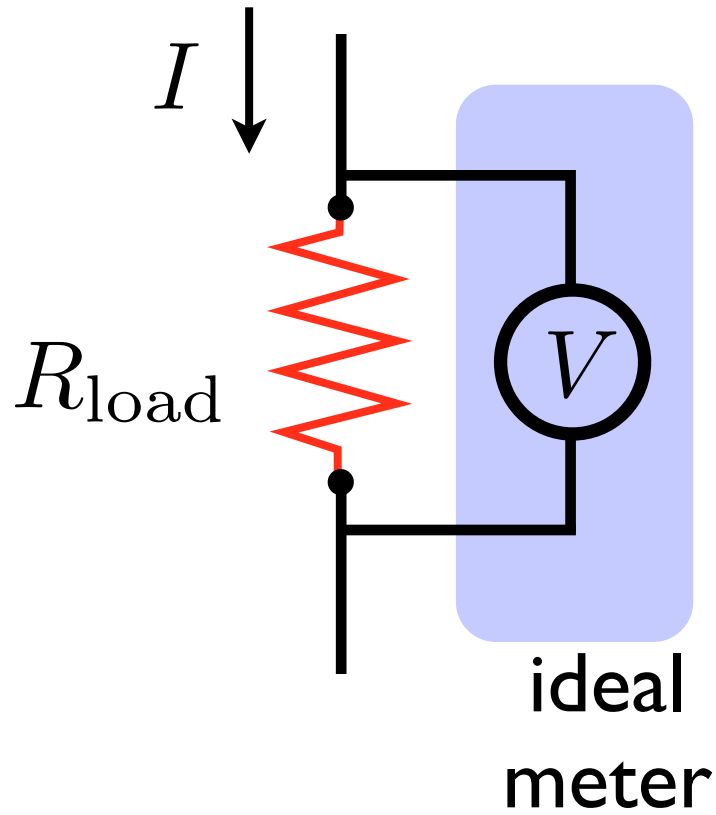


(b)

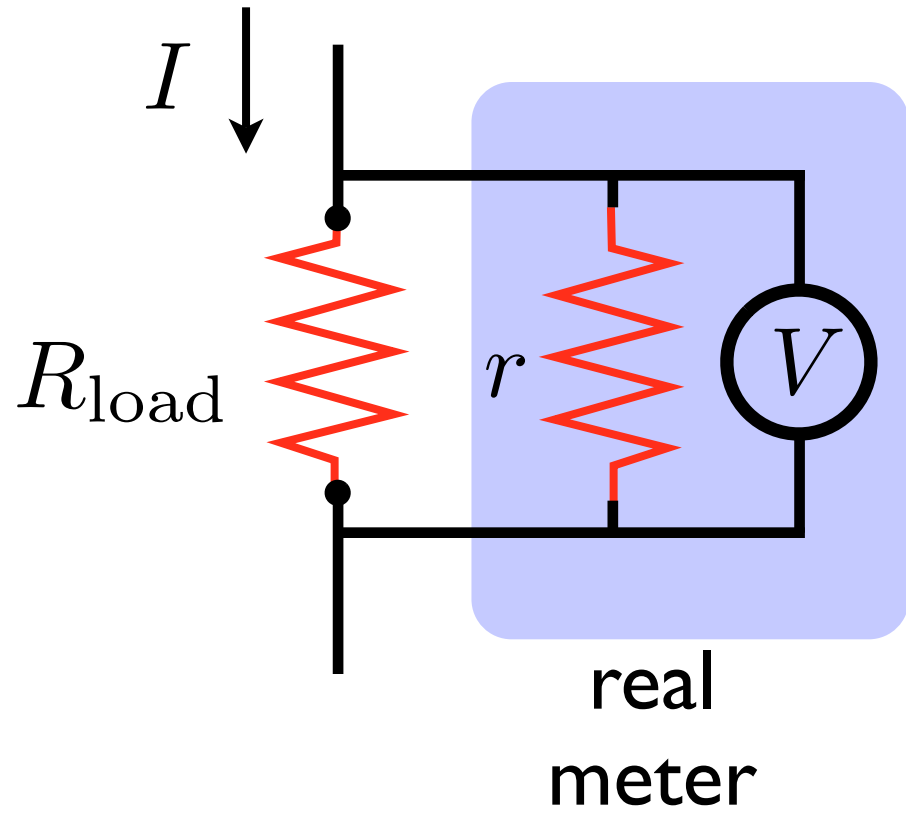


measuring current

a)

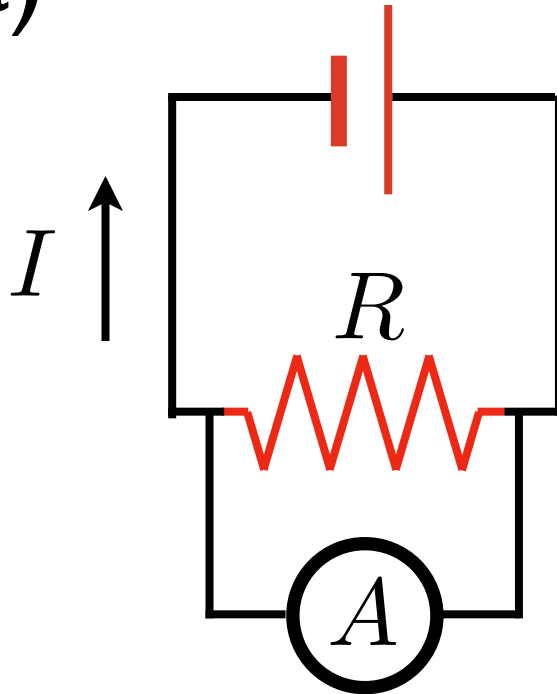


! INCORRECT !

b)

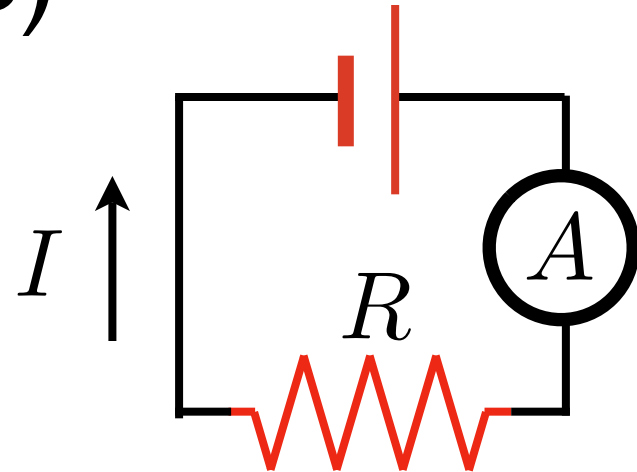


CORRECT

a simple ammeter

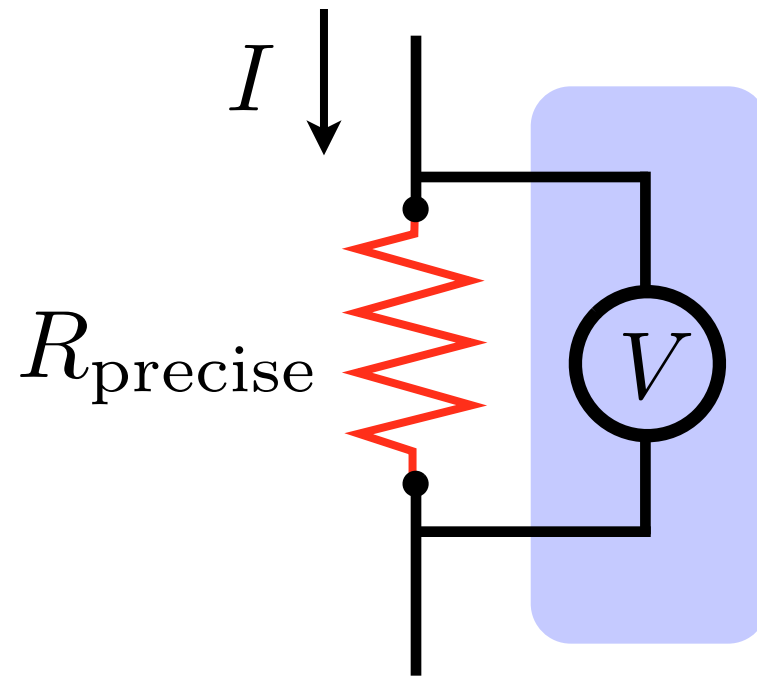

Thévenin equivalents

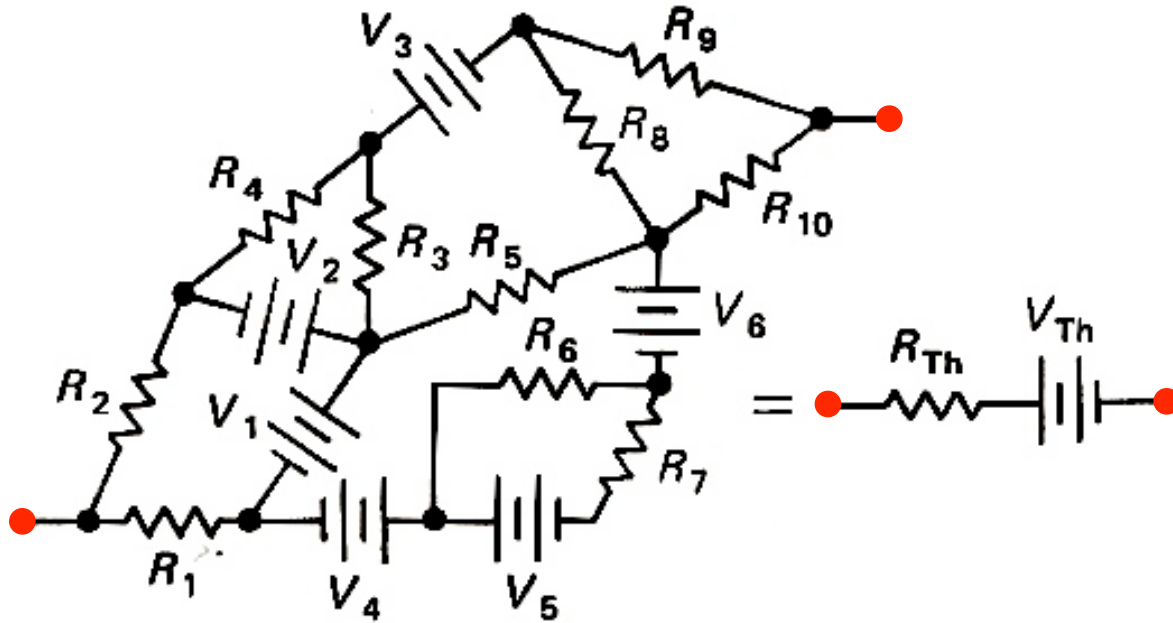


$$V_{th} = V \text{ (open circuit)}$$

$$R_{th} = \frac{V \text{ (open circuit)}}{I \text{ (closed circuit)}}$$


any weird combinations of R's and V's
is equivalent
to a
SINGLE R and V

(or a single I source
in parallel with R)


so what?

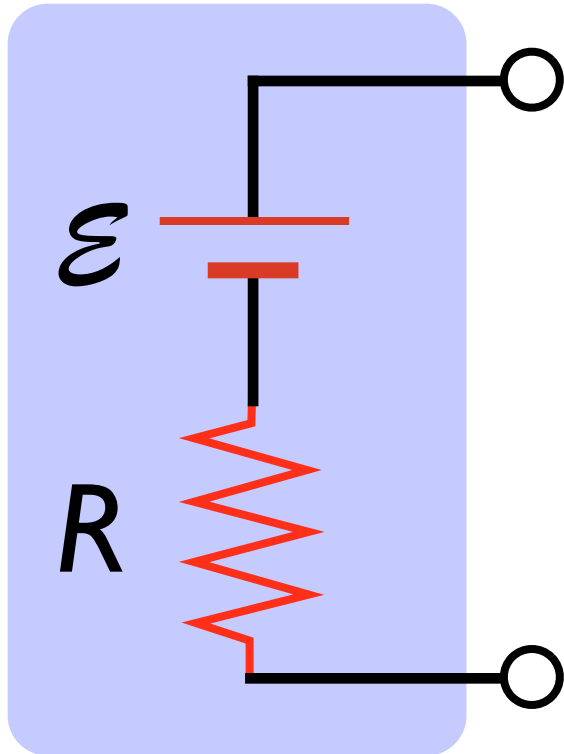


real sources =
ideal sources + R

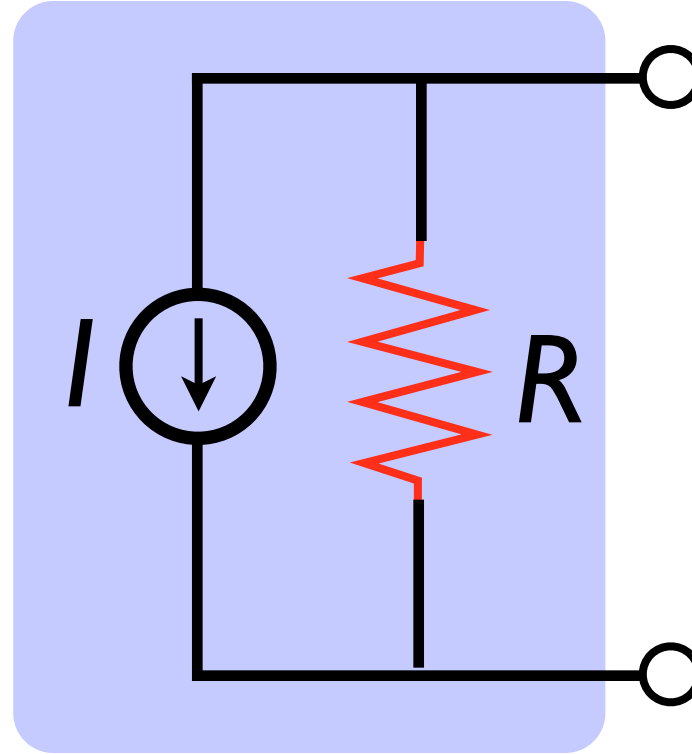

real meter =
ideal meter with R

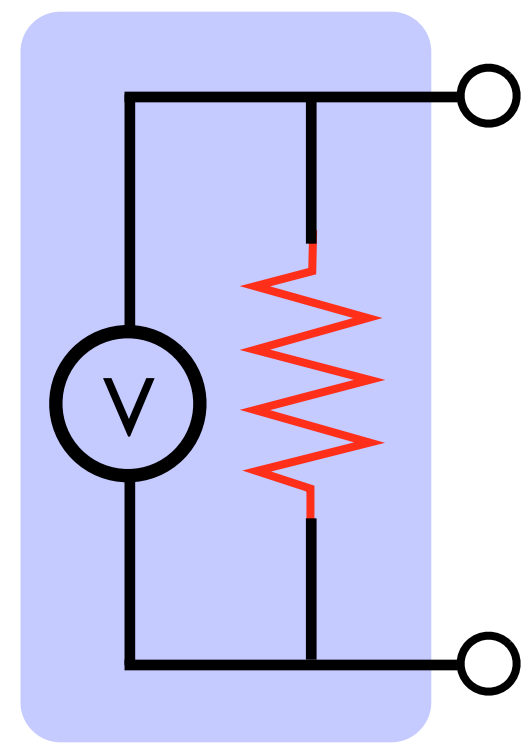

V source loading

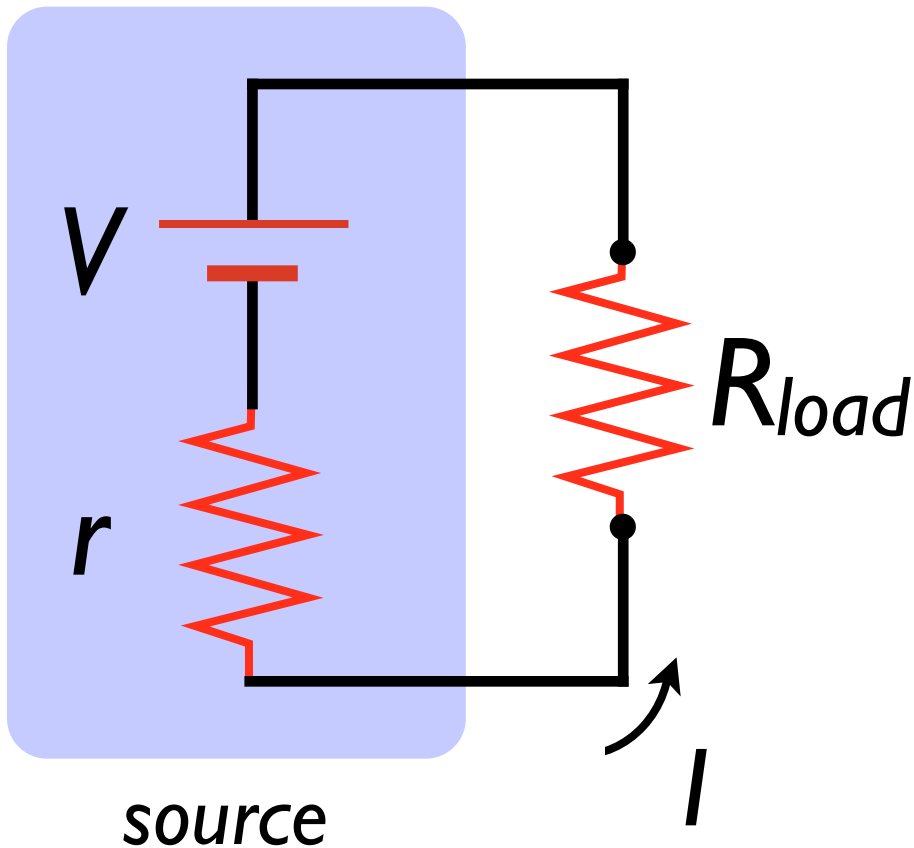

$$\Delta V_{load} = V - Ir$$

for $r \ll R_{load}$,


$$\Delta V_{load} \approx V$$

V source wants R **high**

like a battery

one easy solution:
large resistor in parallel with load

I source loading

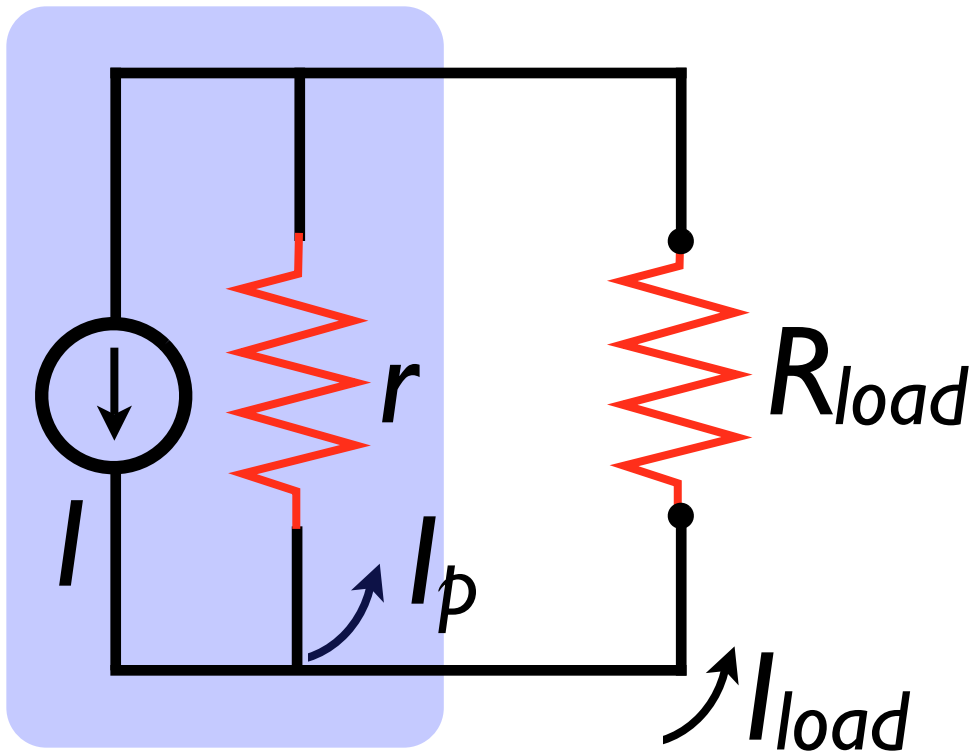

$$I_{load} = I \frac{r}{r+R}$$



for $R_{load} \ll r$,

$$I_{load} \approx I$$

source

I source wants R **low**
sourcing currents at high R_{load} is hard

measuring the meter

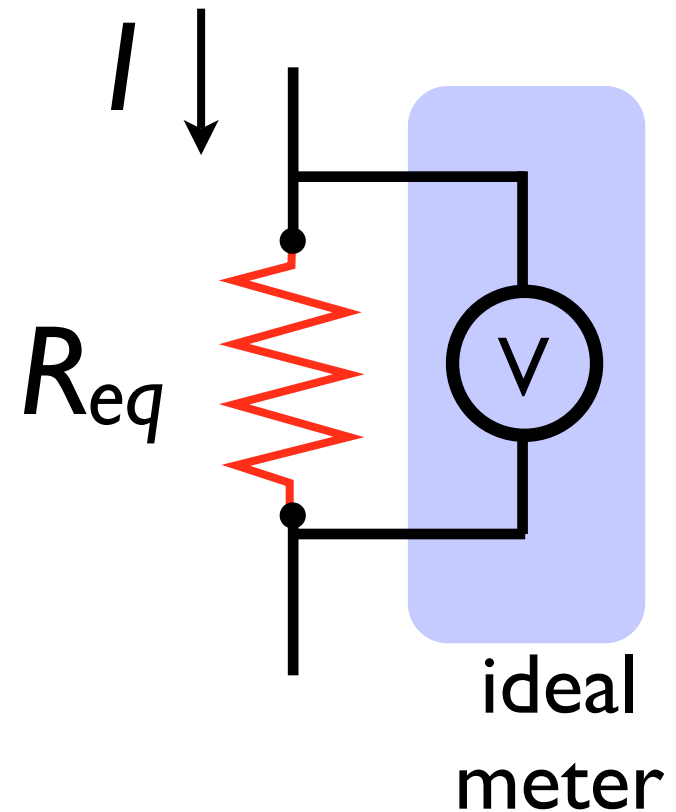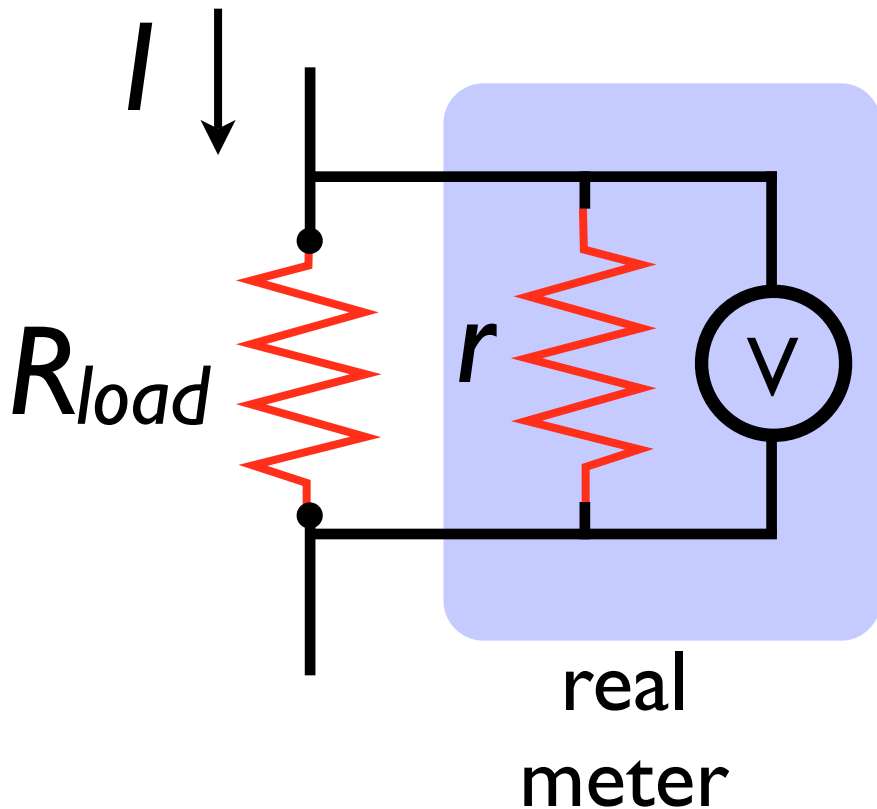


$$\Delta V_{load} = IR_{eq} = \frac{R}{1+R/r} I$$

$$R_{load} \ll r, \Delta V_{load} \approx IR$$

summary

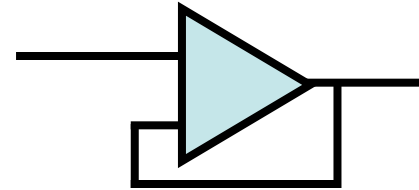voltmeter wants R **low!**
can use a buffer/follower




I source wants R **low**
transformer pre-amp
consider sourcing V

V source wants R **high**
large series + parallel resistors
present large R

Sourcing current


This is what a hand meter does.

Why is it no good?

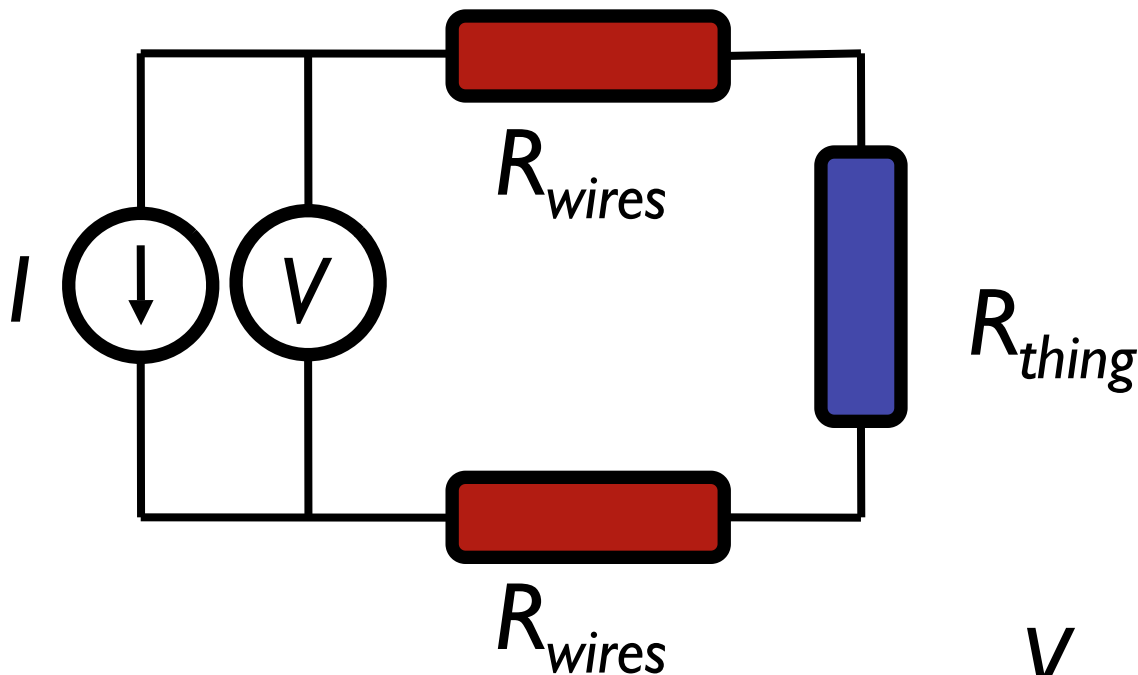

$$V_{meter} = I(R_{thing} + 2R_{wires})$$


Sourcing current, properly

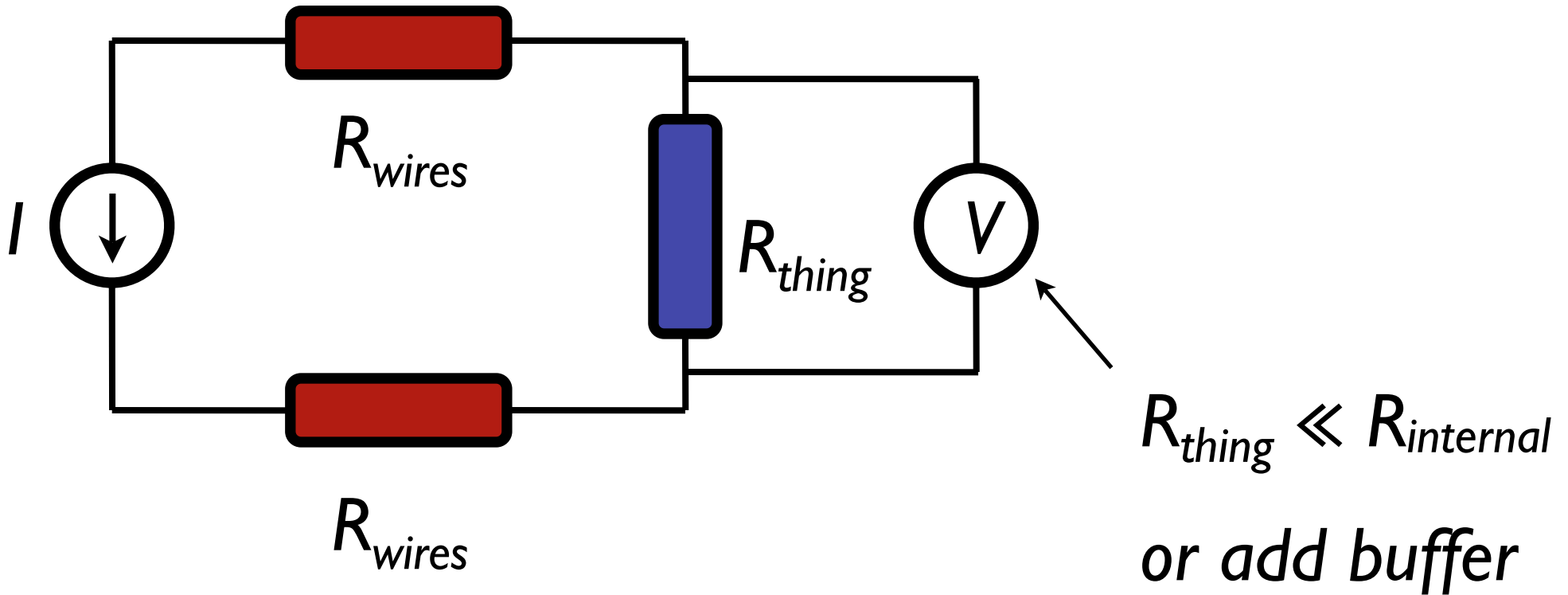

No problem.
You just need four wires.


What is still wrong?

Sourcing voltage

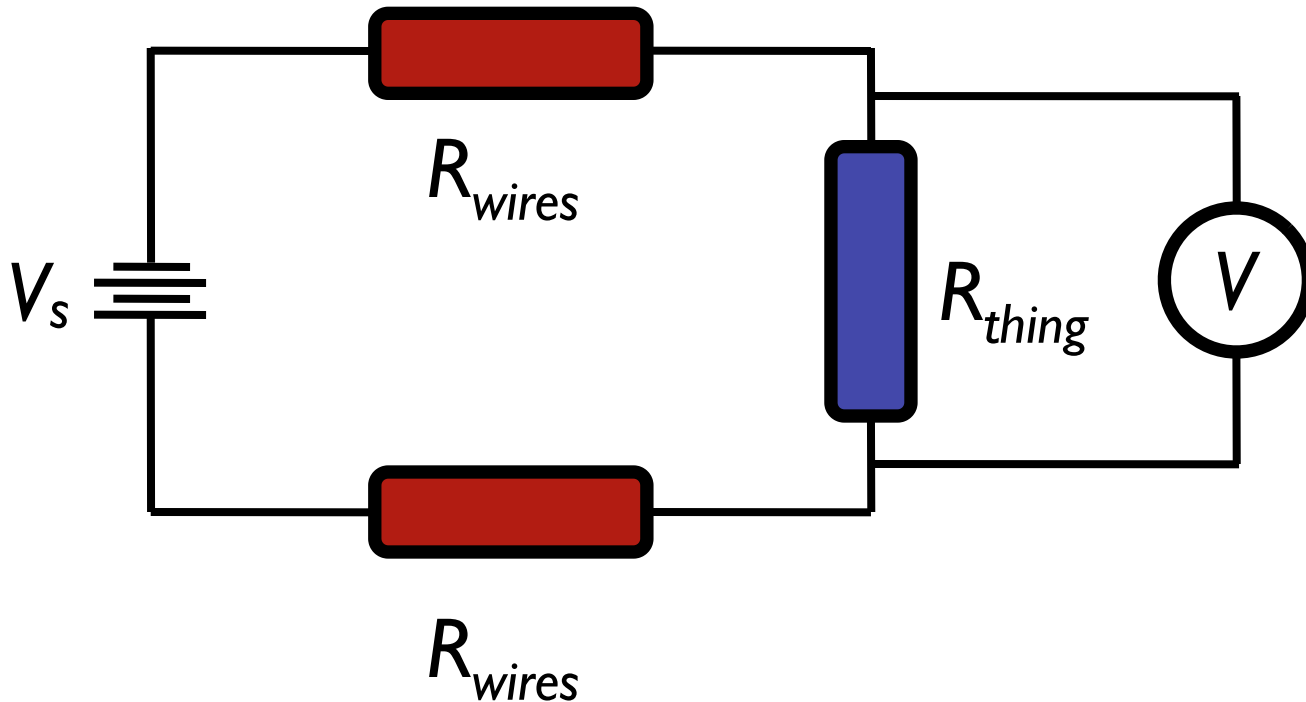


Still have to measure voltage on device
the wires still use up some of V
What about current?

Sourcing voltage II

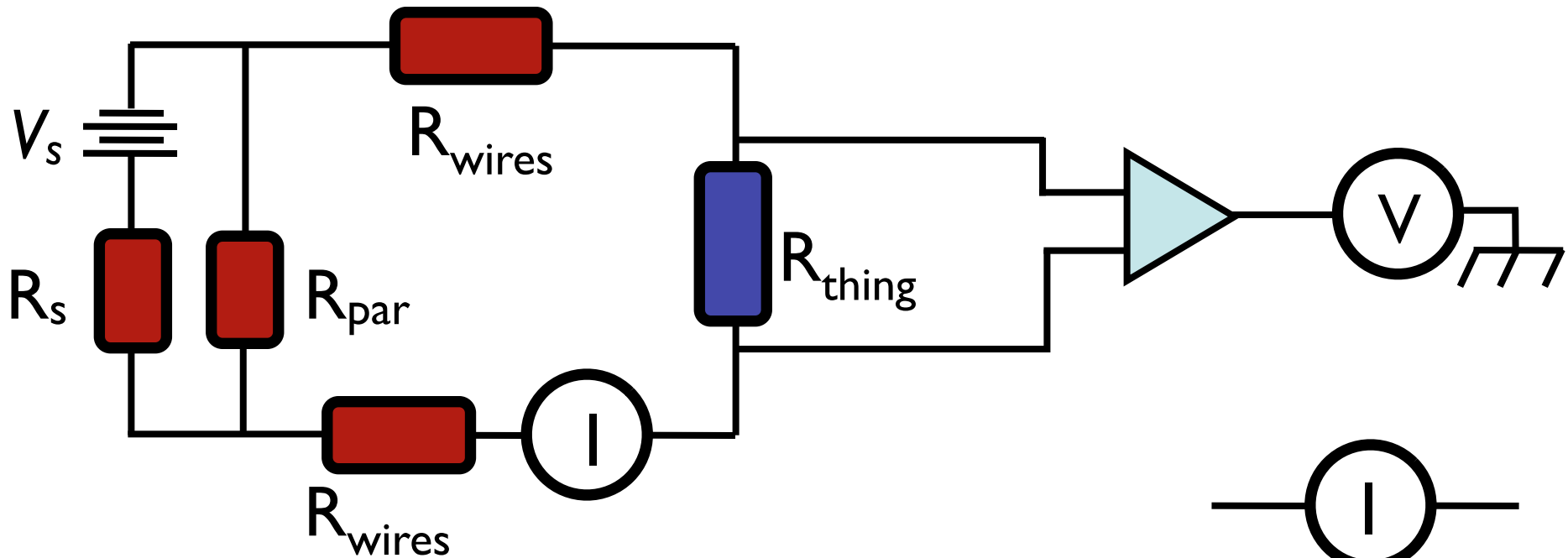

$$R = \Delta V / I$$

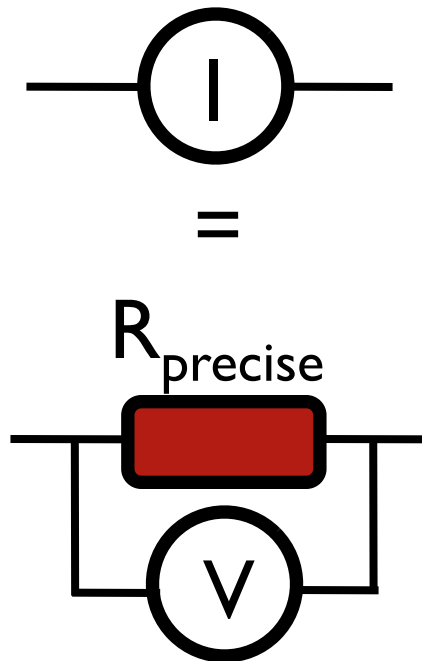Note we need 4 wires again
current meter - not hard
still problems?




source/meter resistances

voltmeter wants R low
but V source wants R high

need buffer/amp on V meter
resistor in parallel with source

if V source is problem, R is too low
consider sourcing I

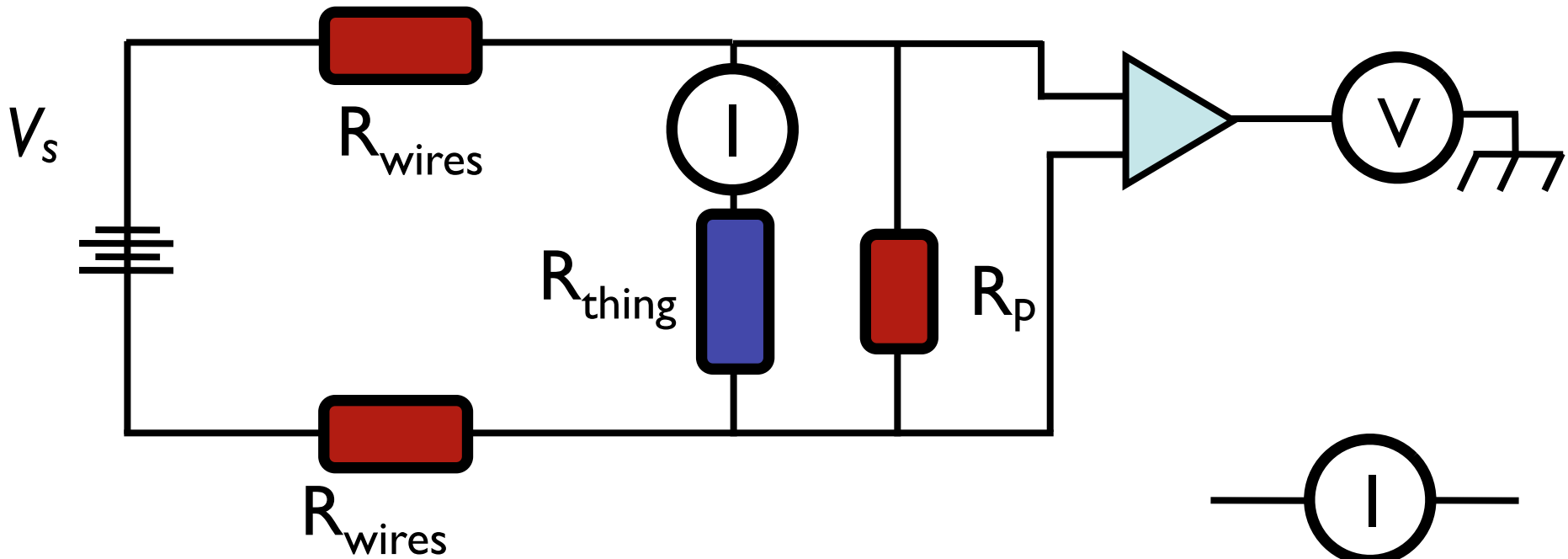what if I want to measure a *really* high R?




source voltage


R_p has same voltage as R_{thing}

R_s has same current

have done $> 10^{10}$ Ohm

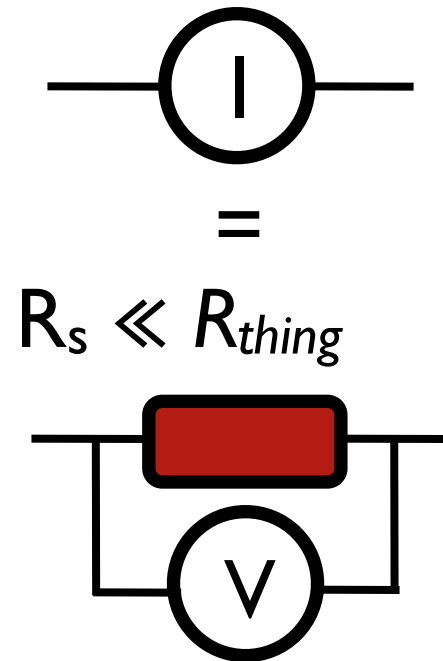

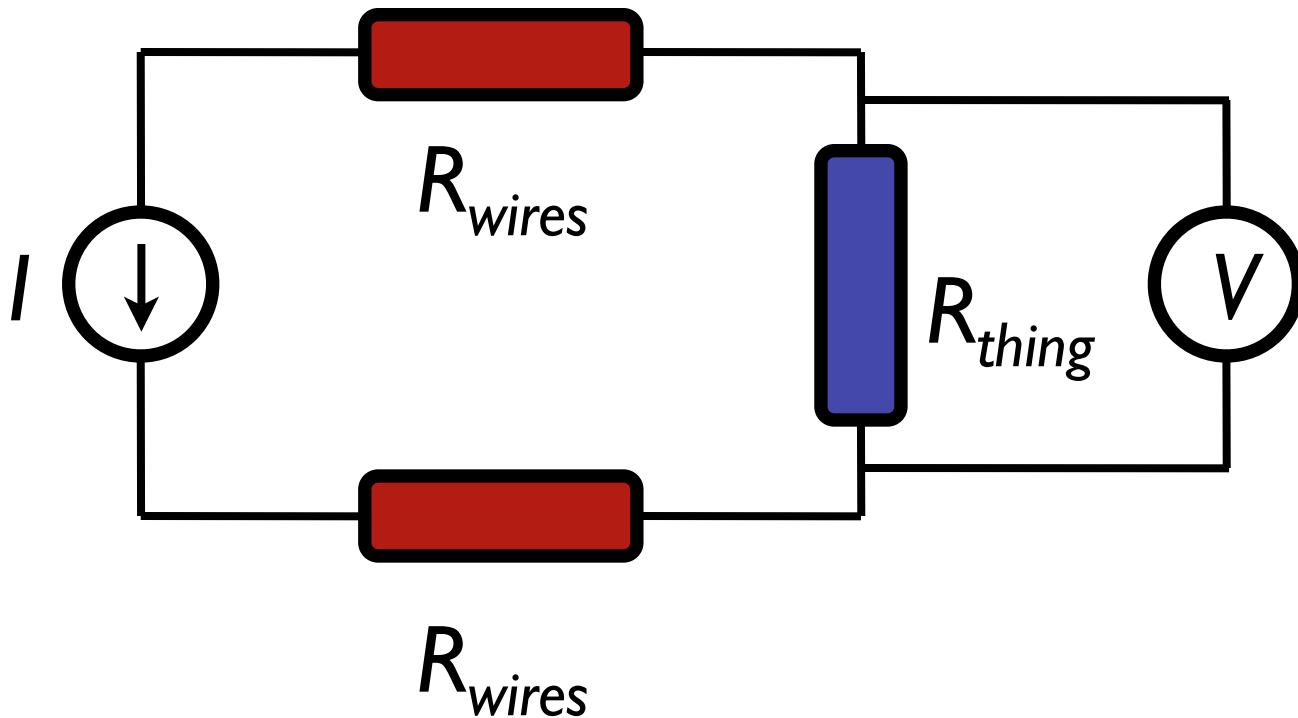what if I want to measure a *really* low R?




this works just fine ...

so long as your V meter is good

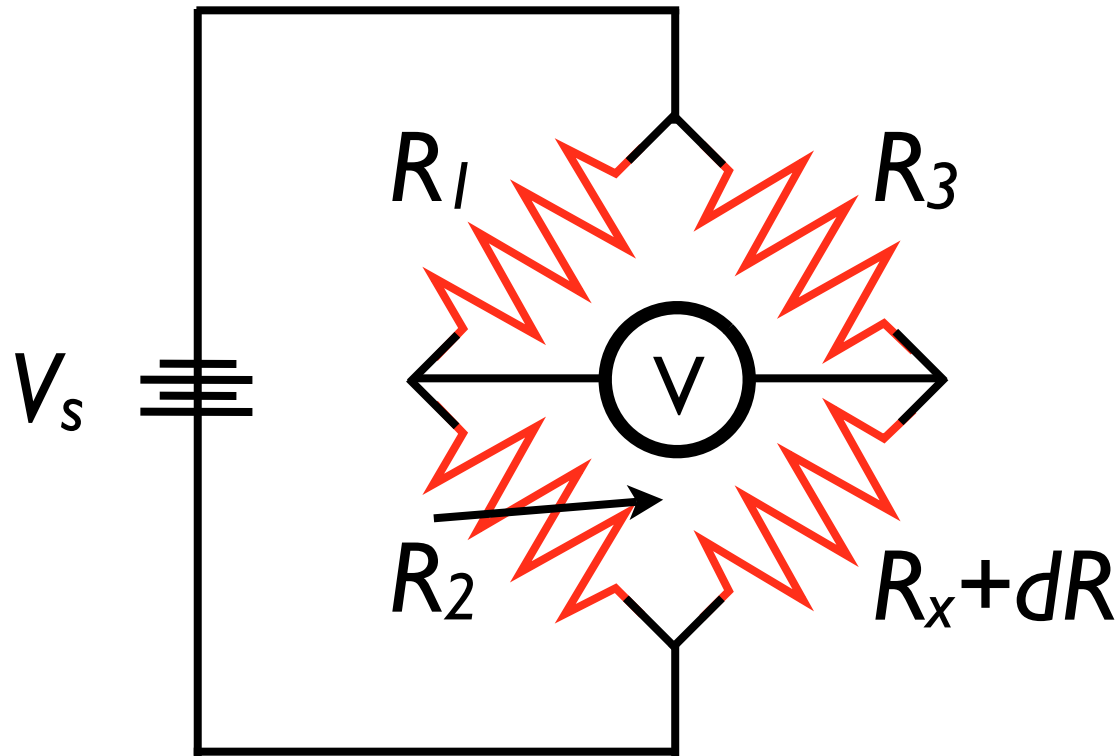v. good amp / part of a bridge

what if I want to measure a small change in R?





balance bridge to $V=0$
detect small changes from null

$$R_2 = \text{trimming resistor} \approx R_3$$


make R_1 - R_3 about the same
trimming resistor on $R_2 = dR$

$$V = \left(\frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2} \right) V_s$$

$$R_x = \frac{R_3 R_2}{R_1}$$

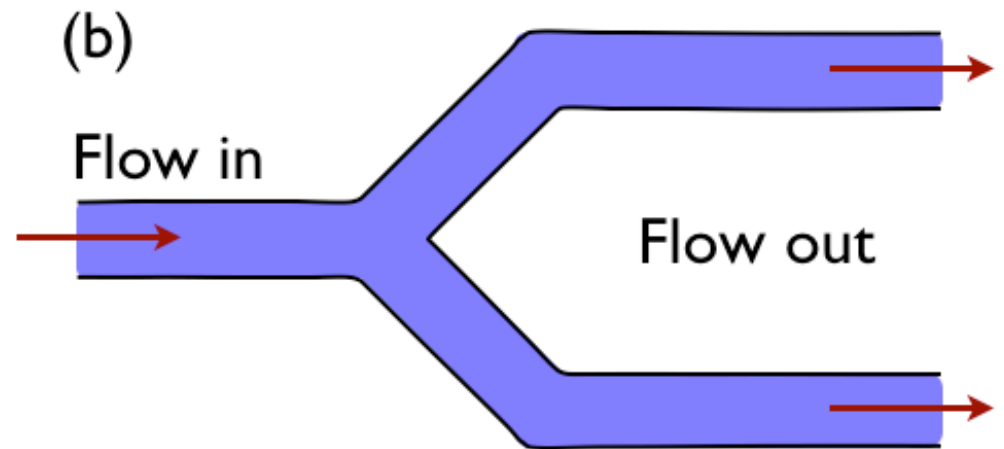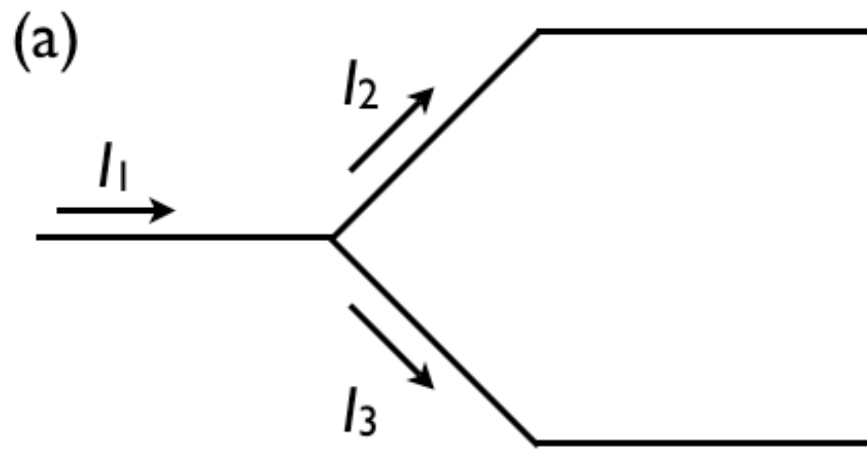


(a)

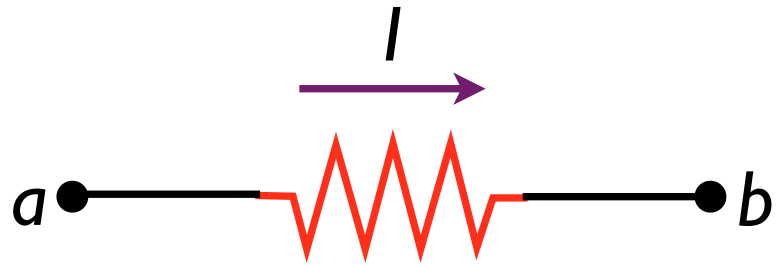


$$\Delta V = V_b - V_a = -IR$$

(c)

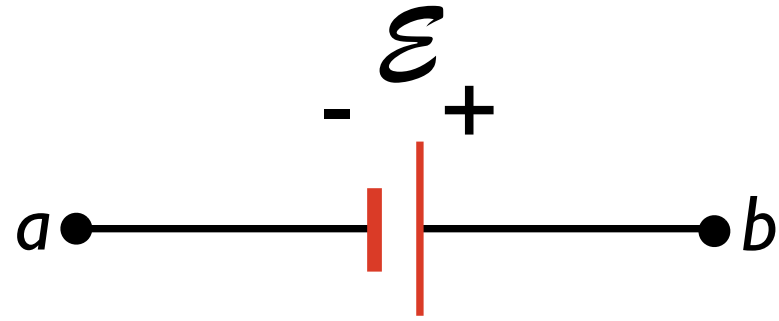


$$\Delta V = V_b - V_a = +\mathcal{E}$$

(b)

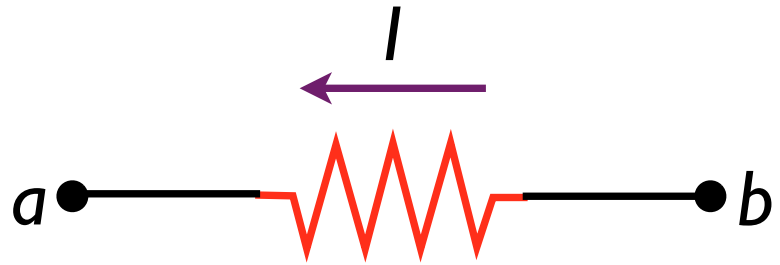


$$\Delta V = V_b - V_a = +IR$$

(d)

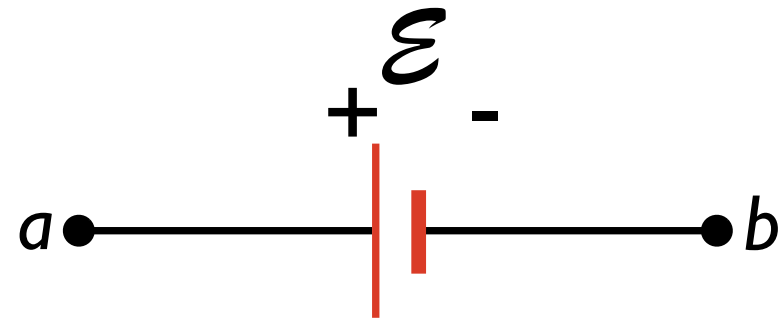



$$\Delta V = V_b - V_a = -\mathcal{E}$$

(a)

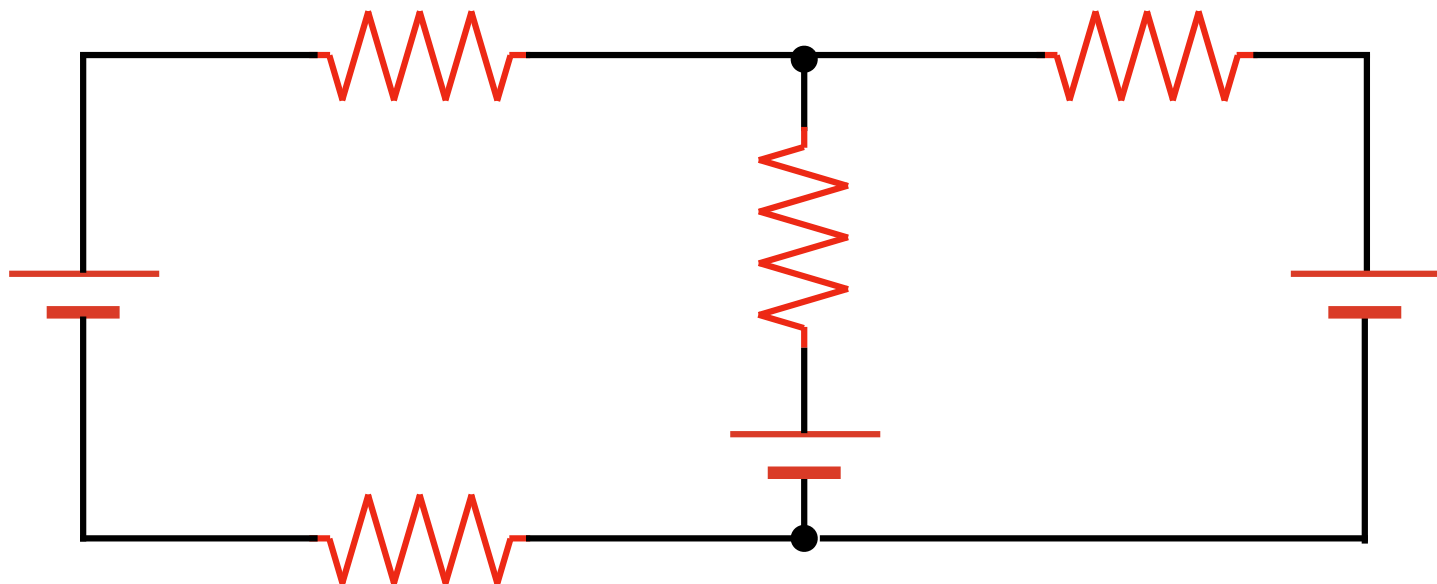


(b)

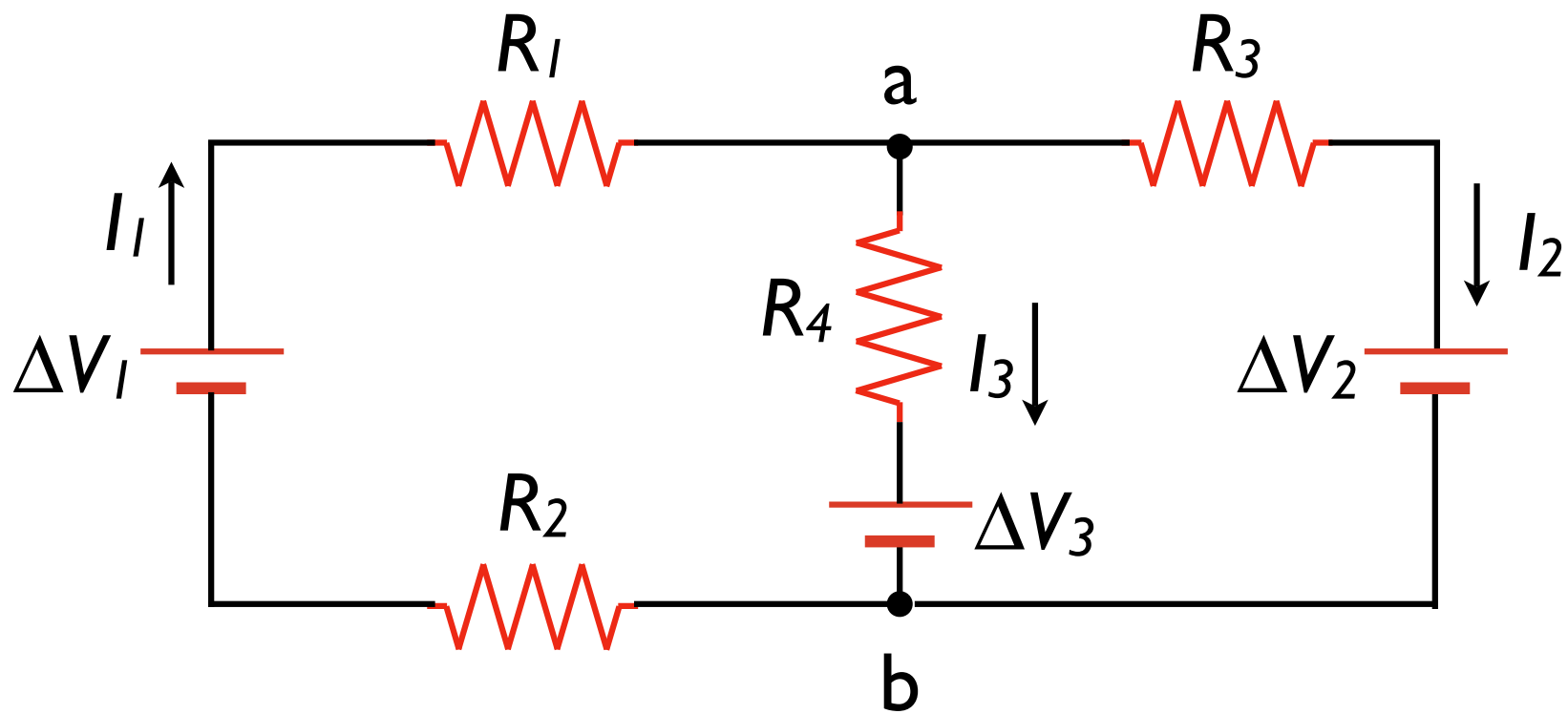

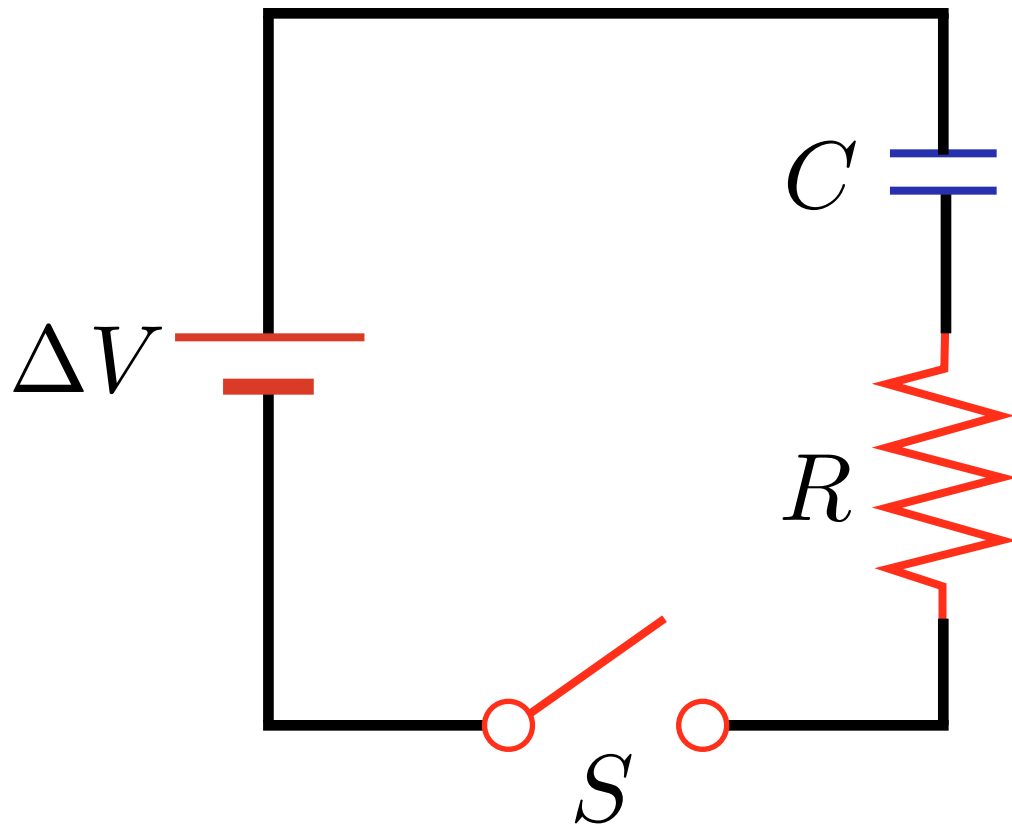

(a)

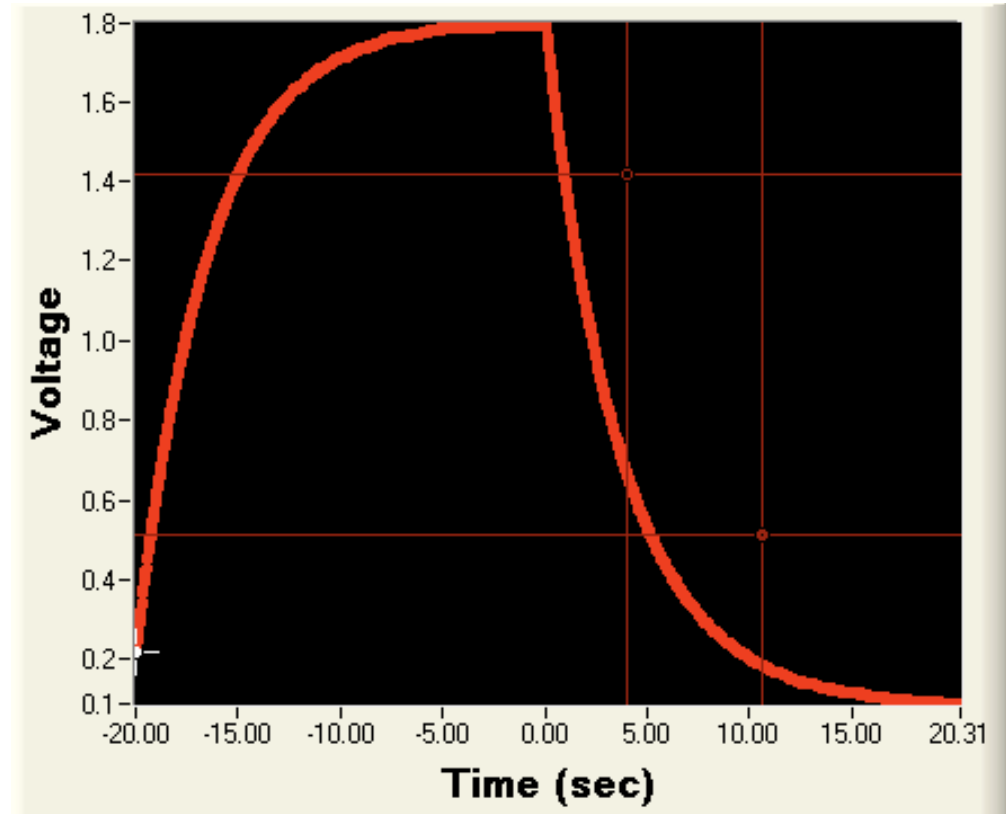

(b)