
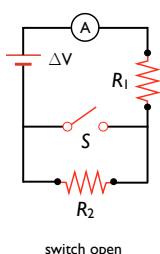


Quiz 4: Solutions

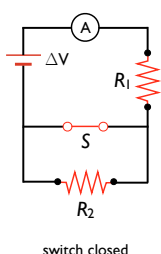1. If the current carried by a conductor is doubled, what happens to the average time between collisions?

- Nothing.
- It doubles.
- It decreases by two times.
- It increases by 4 times.
- It decreases by 4 times.

In our model of conduction, the average time between collisions is a property of the material and temperature, but it does not depend on the current. At a given temperature for a given material, it is a fixed constant that the *current depends on*, not the other way around.



2. Refer to the figures at left. What happens to the reading on the ammeter when the switch S is opened?

- the reading goes up
- the reading goes down
- the reading does not change

When switch S is closed, resistor R_2 is shorted by a perfect wire, and plays no role (or, if you like, it is in parallel with a resistance of zero, which gives an equivalent resistance of zero). The current in the circuit would then be $\Delta V/R_1$. With switch S open, R_1 and R_2 are in series. This means more resistance at the same battery voltage, so the current must go down, to a value $\Delta V/(R_1 + R_2)$.

3. When we power a light bulb, are we using up charges and converting them to light?

- Yes, moving charges produce “friction” which heats up the filament and produces light
- Yes, charges are emitted and observed as light
- No, charge is conserved. It is simply converted to another form such as heat and light.
- No, charge is conserved. Moving charges produce “friction” which heats up the filament and produces light.

Charge is always, always conserved, and it can't be converted to anything else. In an *incandescent bulb*, collisions within the conducting filament convert electrical energy (but not charge!) to heat, enough that the filament temperature rises to the point of glowing.

4. An electric current of 1 mA flows through a conductor, which results in a 150 mV potential difference. The resistance of the conductor is:

- 150Ω
- $6.7 \times 10^{-4} \Omega$
- $1.5 \times 10^{-6} \Omega$
- 6.7Ω

The resistance is the potential difference across the conductor divided by the resulting current:

$$R = \frac{\Delta V}{I} = \frac{150 \text{ mV}}{1 \text{ mA}} = \frac{0.150 \text{ V}}{0.001 \text{ A}} = 150 \Omega$$