

Quiz 4: Capacitors and Such

$$Q = C\Delta V \quad \text{Energy} = \frac{1}{2}Q\Delta V = \frac{1}{2}C(\Delta V)^2 = Q^2/2C$$

$$C = \epsilon_0 A/d \quad \text{parallel plate} \quad \epsilon_0 = \frac{1}{4\pi k_e} = 8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2 \quad e = 1.60218 \times 10^{-19} \text{ C}$$

$$\frac{1}{C_{\text{eq, series}}} = \frac{1}{C_1} + \frac{1}{C_2} \quad C_{\text{eq, par}} = C_1 + C_2$$

1. A fully charged defibrillator contains 1.20 kJ of stored electrical energy in a 1.1×10^{-4} F capacitor. Find the voltage needed to store 1.20 kJ in the unit.

2. Five $5 \mu\text{F}$ capacitors are connected in parallel. What is the equivalent capacitance? How about if all five are connected in series?

3. I have two batteries and three capacitors. How should I connect them to store the most electrical energy? Describe in words or as a circuit diagram as you choose.