

The Plan

- complex combos of capacitors
- dielectrics, quickly
- current & resistance
- HW3 hints
- time permitting, bits on dc circuits

Exam I

- During lab period ... but only 60-90min
 - electric forces & fields
 - electrical potential & energy
 - current & resistance
 - NO RELATIVITY
- study quick quizzes, example probs
- our HW and quizzes (and old ones)
- problems in notes
- choice of problems / partial credit

relax.
it will be ok.

1. It takes 3×10^6 J of energy to fully recharge a 9 V battery. How many electrons must be moved across the $\Delta V = 9$ V potential difference to fully recharge the battery? One electron has a charge of $-e$, given above.

$$PE = qV = neV$$

$$n = PE/eV$$

2. An electron initially at rest is accelerated through a potential difference of 1 V, and gains kinetic energy KE_e . A proton, also initially at rest, is accelerated through a potential difference of -1 V, and gains kinetic energy KE_p . Is the electron's kinetic energy larger, smaller, or the same compared to the protons? Justify your answer. Note that the proton mass m_p is about 1000 times the electron mass m_e .


same charge, same potential diff = same PE change

same PE change = same KE


velocity will be different, since m is

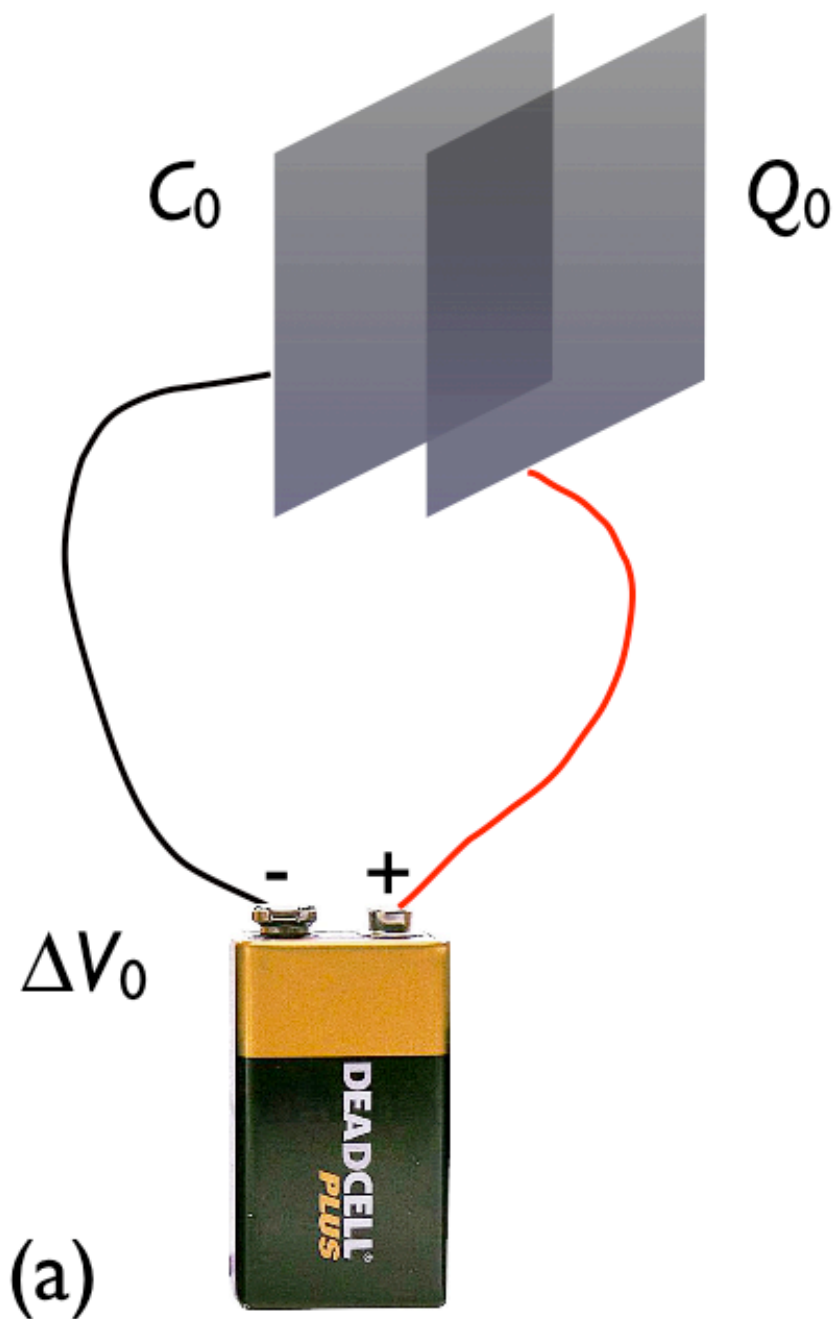3. A “free” electron and a “free” proton are placed in an identical electric field. Which of the following statements are true? *Check all that apply.*

- Each particle is acted on by the same electric force and has the same acceleration.
- The electric force on the proton is greater in magnitude than the force on the electron, but in the opposite direction.
- The electric force on the proton is equal in magnitude to the force on the electron, but in the opposite direction.
- The magnitude of the acceleration of the electron is greater than that of the proton.
- Both particles have the same acceleration.




(a)

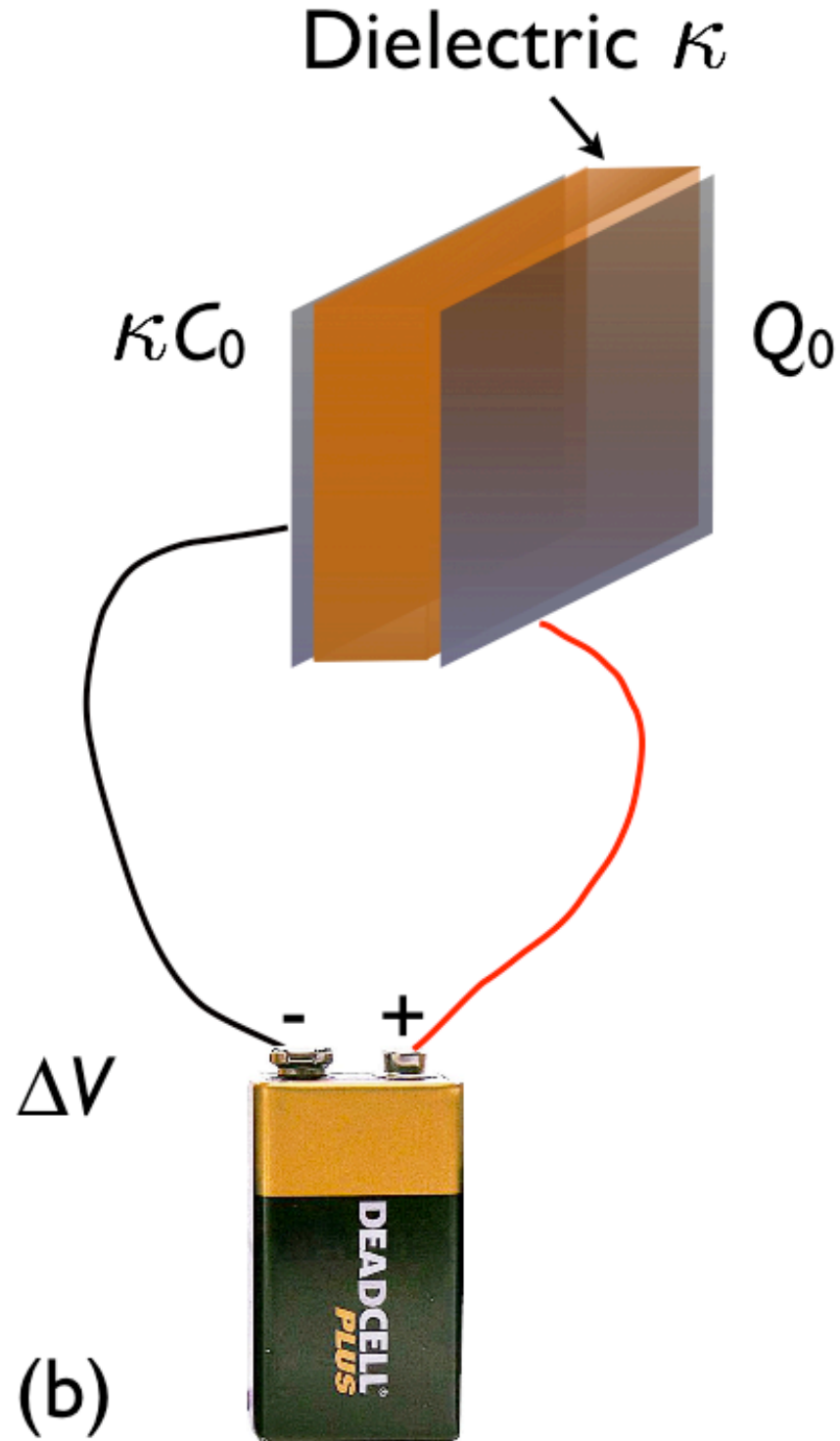


(b)


(a)



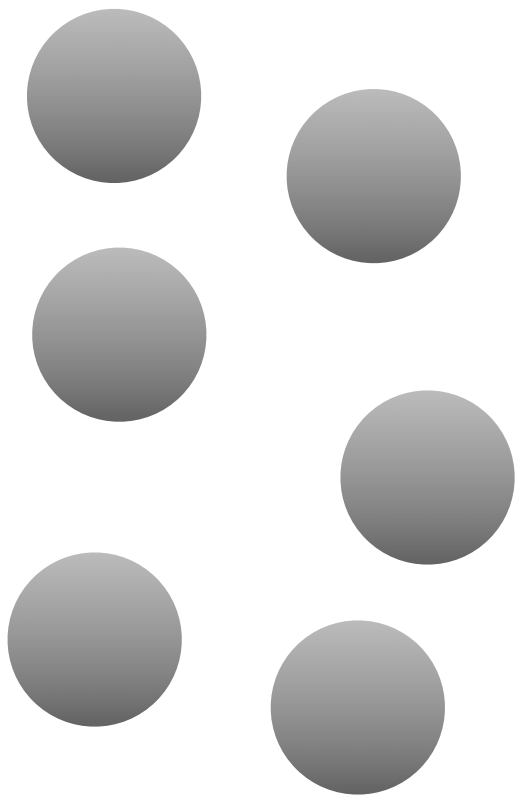


(b)

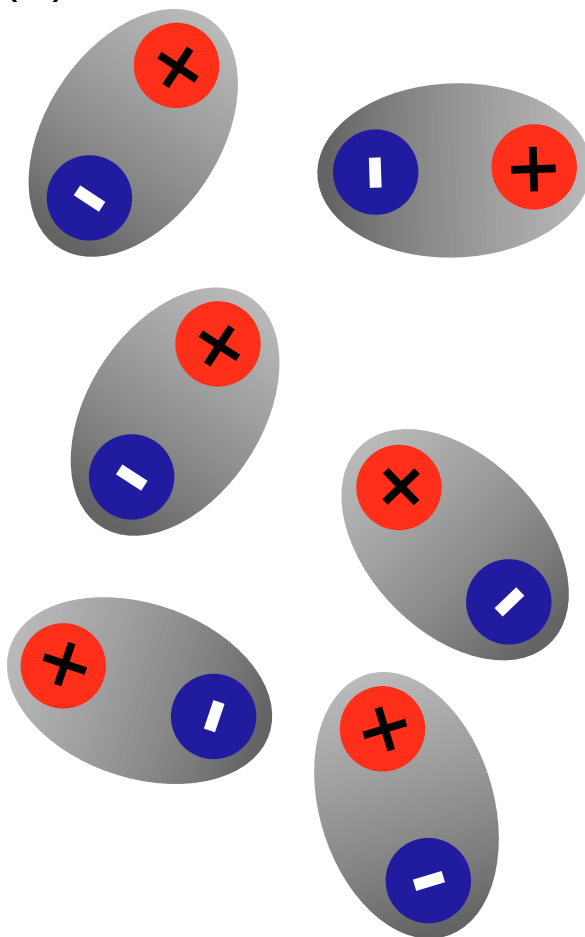


(c)

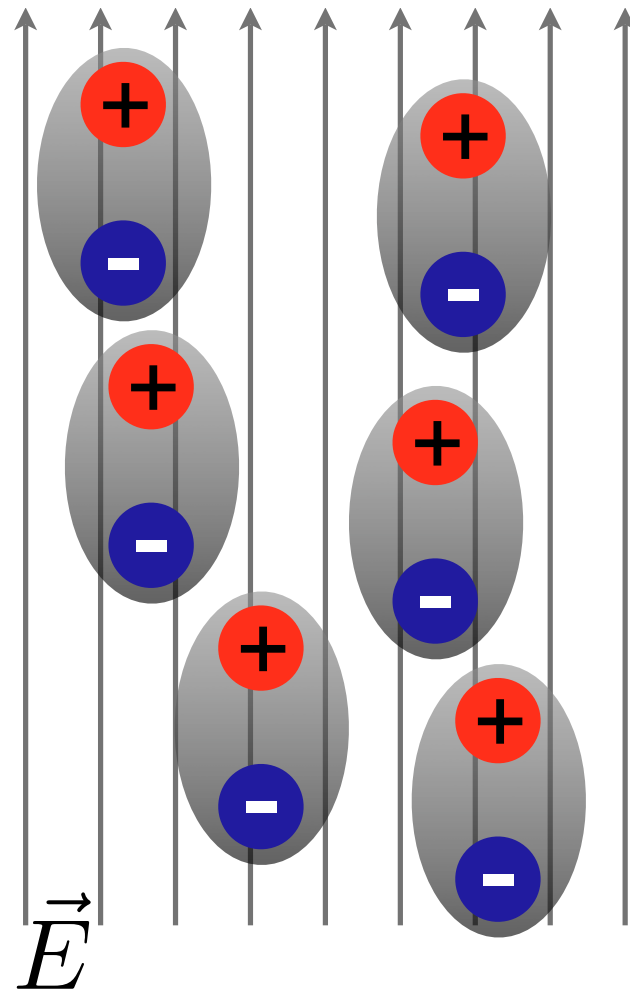


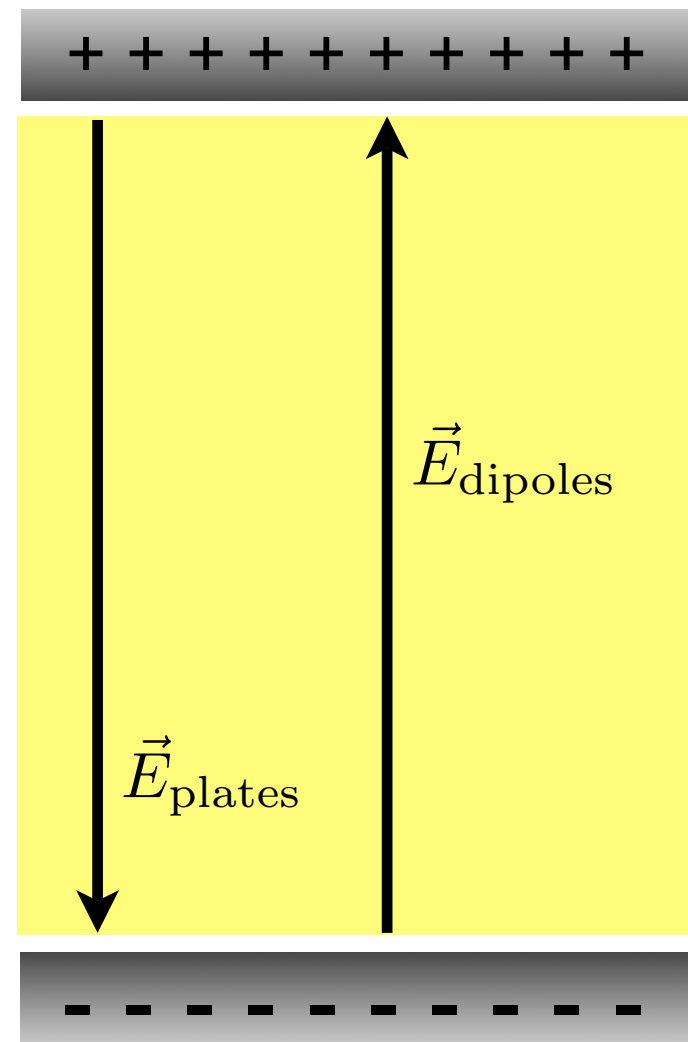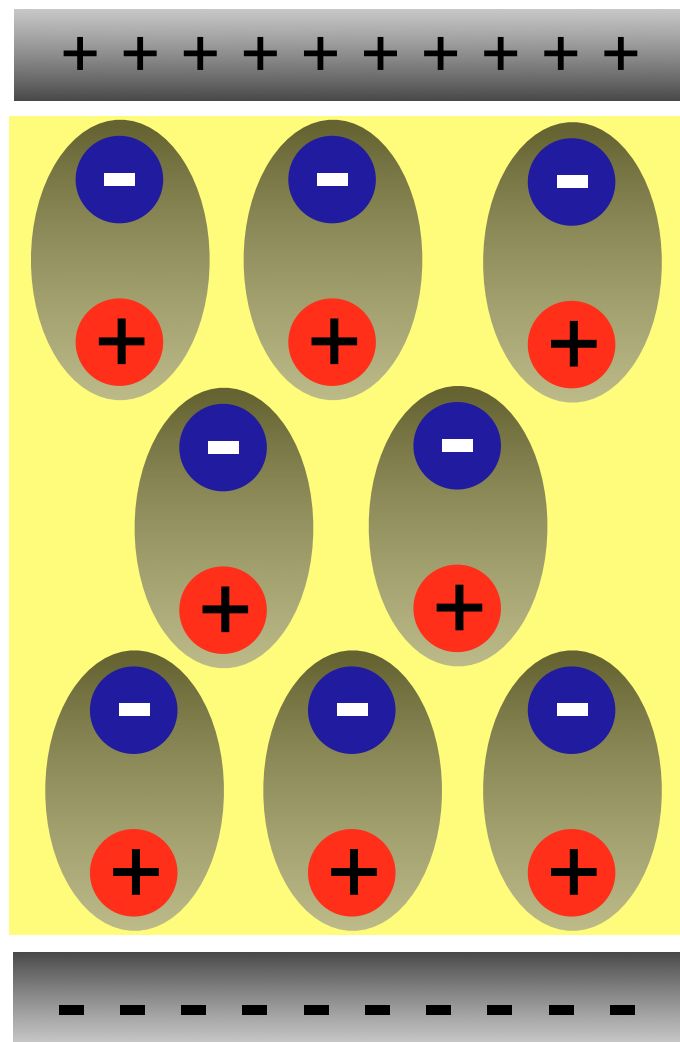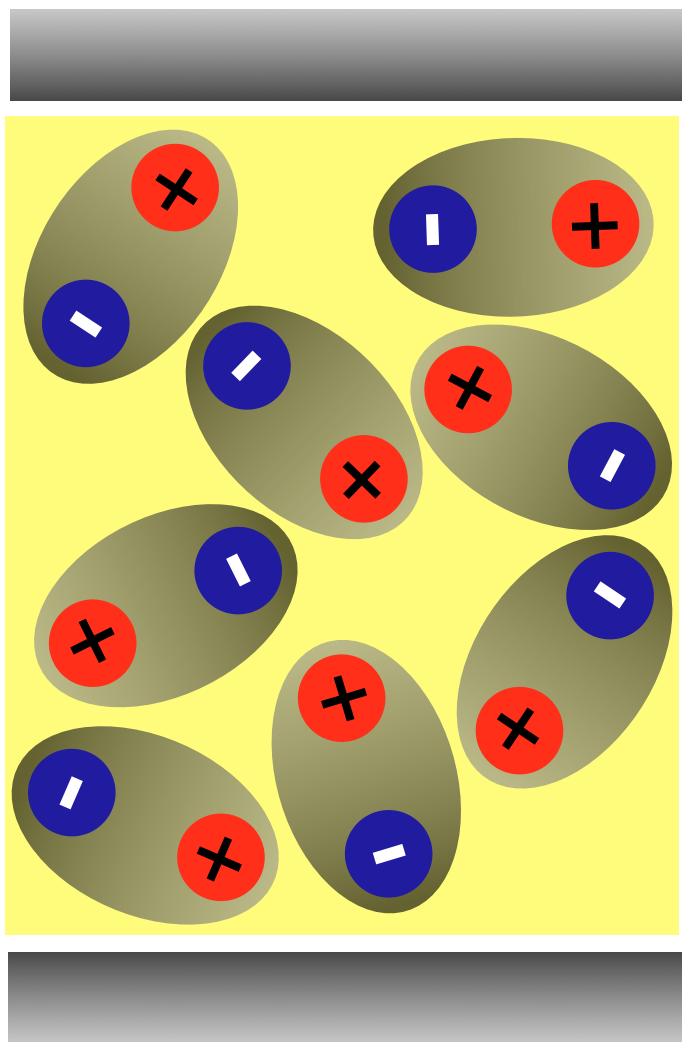


$$I = \frac{\Delta Q}{\Delta t}$$

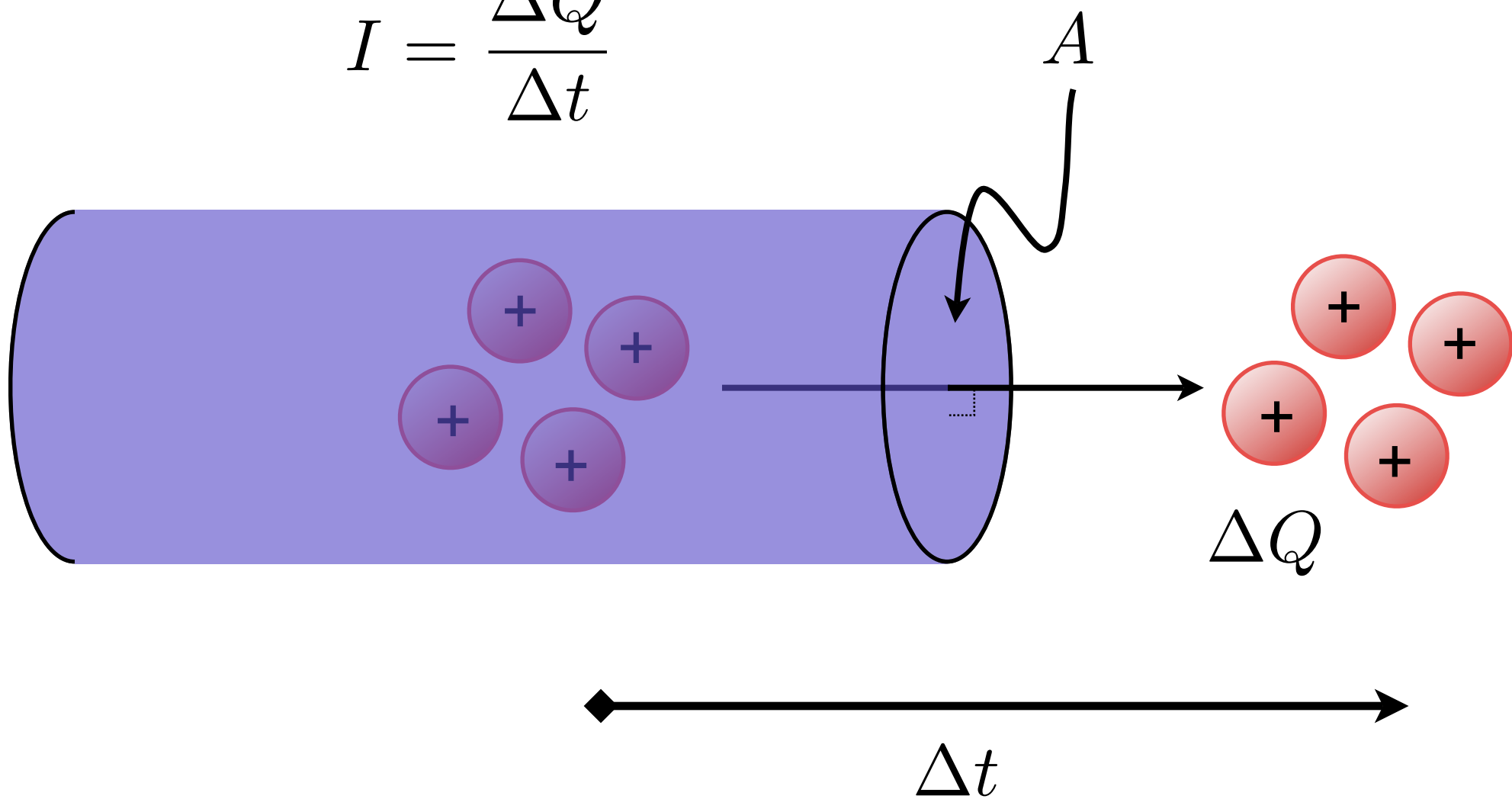


$+x$

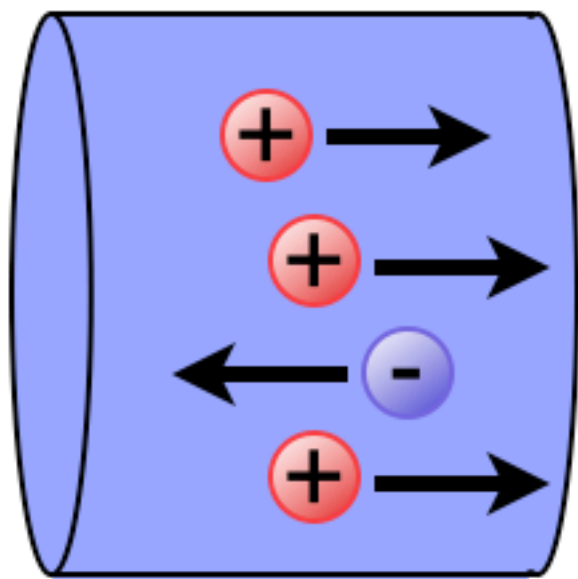

A

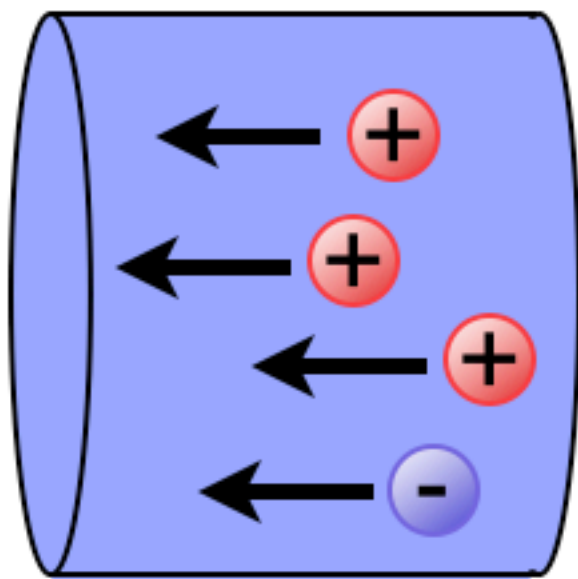

B

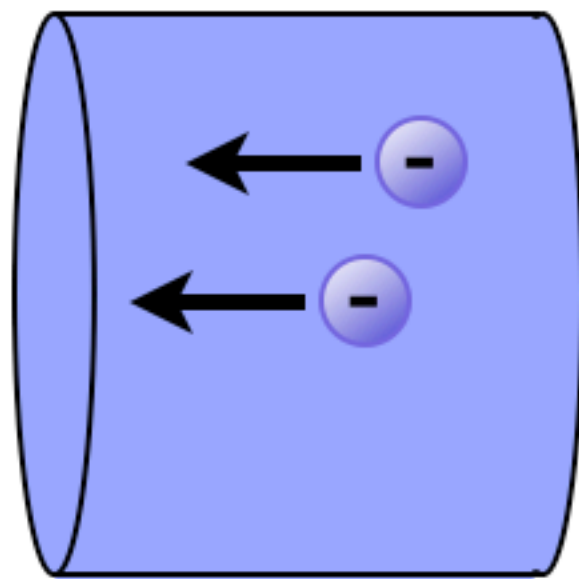

C

BENJAMIN FRANKLIN?

I BRING A MESSAGE
FROM THE FUTURE!
I DON'T HAVE MUCH TIME.

YES?


WHAT IS IT?


THE CONVENTION YOU'RE SETTING
FOR ELECTRIC CHARGE IS BACKWARD.
THE ONE LEFT ON GLASS BY SILK
SHOULD BE THE *NEGATIVE* CHARGE.



WE WERE GOING TO USE THE TIME MACHINE TO
PREVENT THE ROBOT APOCALYPSE, BUT THE
GUY WHO BUILT IT WAS AN ELECTRICAL ENGINEER.

not so funny now.

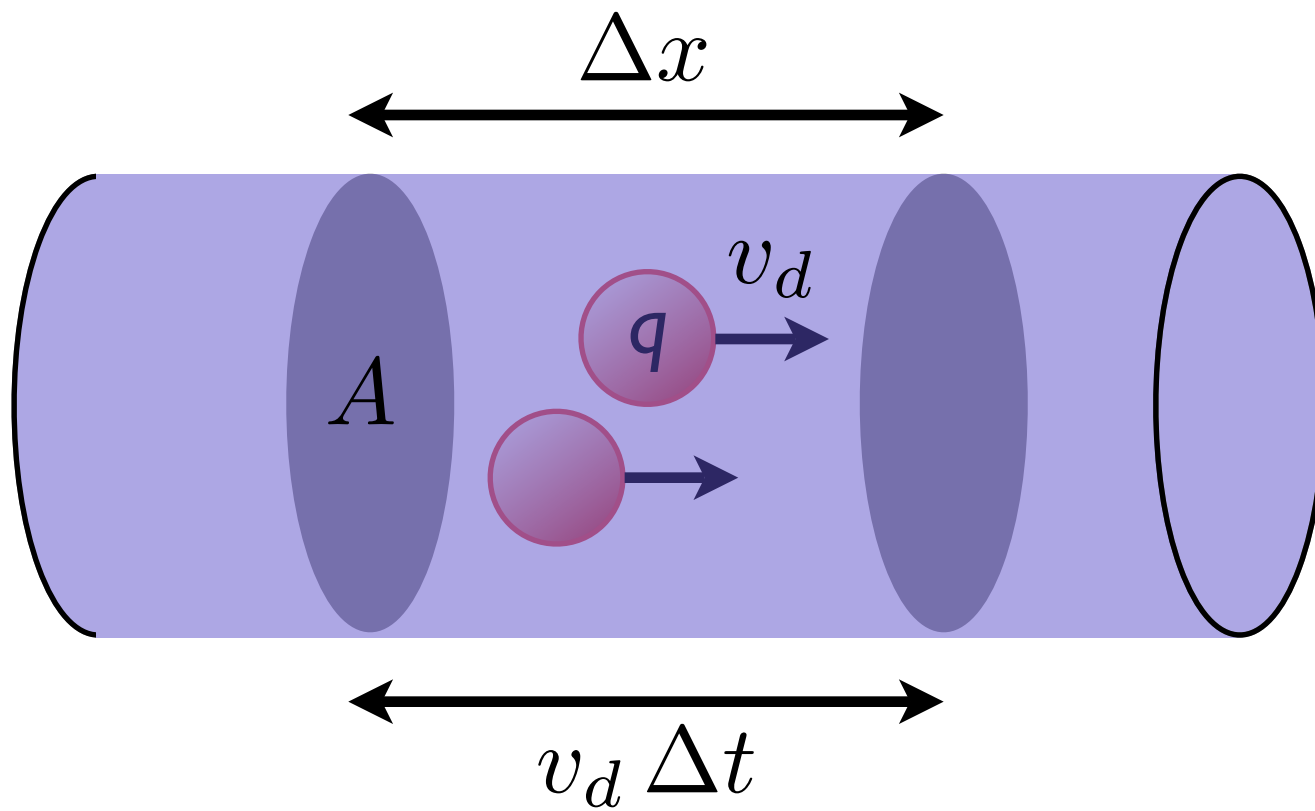

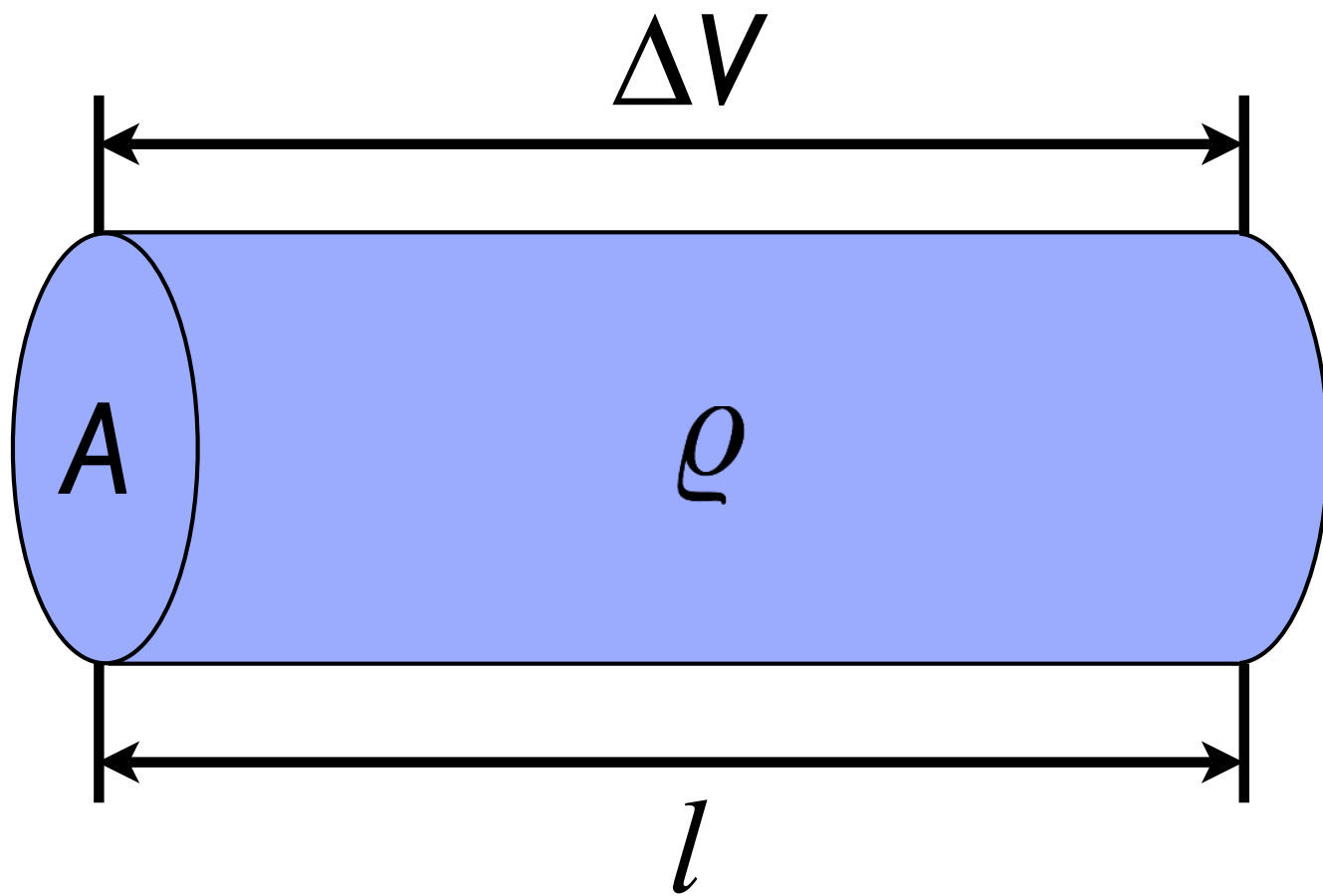


$$R = \frac{\rho l}{A} = \frac{\Delta V}{I}$$


$$I = \text{Cause}/\text{Resistance}$$

I is the current, or flow rate,
describes different scenes:


(a) Heat flow
through
a wall

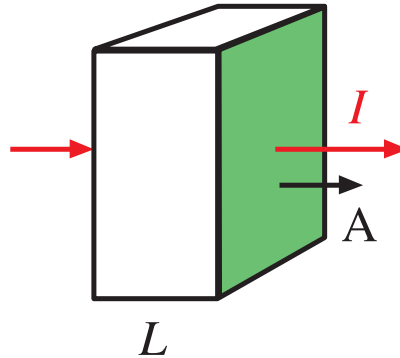

(b) Charge
flow
through
a wire

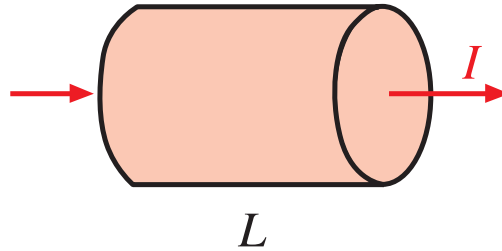

(c) Fluid
flow
through
a pipe

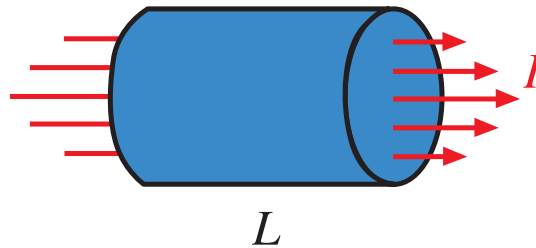


Resistance R
has the same form in most cases,


$$R = \rho L/A$$

| Transport what? | Heat | Electric charges | Displacement of a molecule in a fluid | Volume of fluid |
|--|-------------------------------------|--|---------------------------------------|------------------------|
| Current form (items/second) | $I = -\Delta T/R$ | $I = -\Delta V/R$ | $v_{av} \equiv I = -\Delta P/R$ | $I = -\Delta P/R$ |
| Current units | J/s or W | C/s or amperes | m/s | m³/s |
| Resistance form | $R = \rho L/A$ | $R = \rho L/A$ | $R = \rho L/A$ | $R = \rho L/A^2$ |
| Detail of ρ (resistivity) | $\rho = 1/\text{heat conductivity}$ | $\rho = \text{electrical resistivity}$ | $\rho = 6\eta\pi$ | $\rho = 8\eta\pi$ |

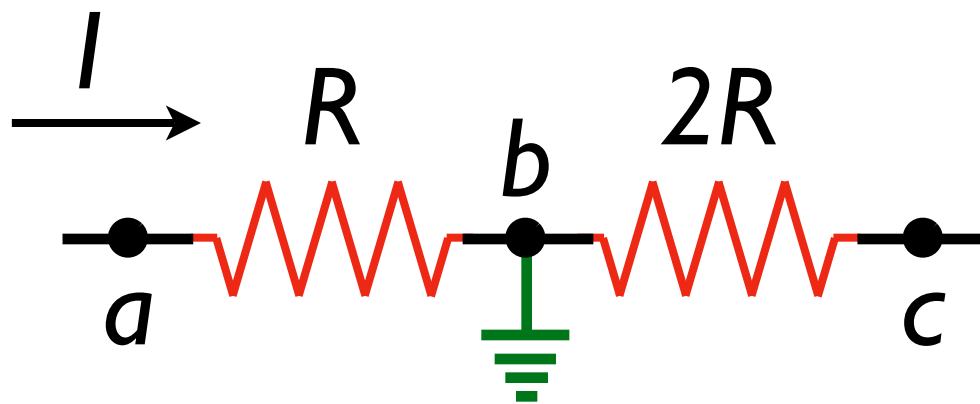
battery = pump
 voltage = pressure
 current = flow
 resistor = constriction
 capacitor = diaphragm / flexible reservoir
 diode = check valve
 inductor = paddle wheel




(a)

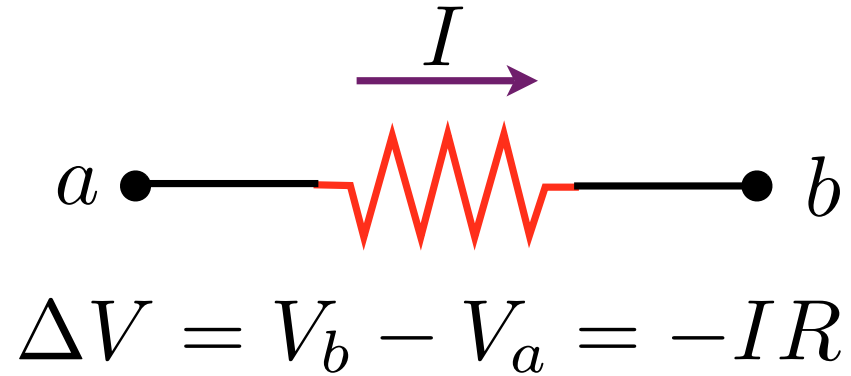



(b)

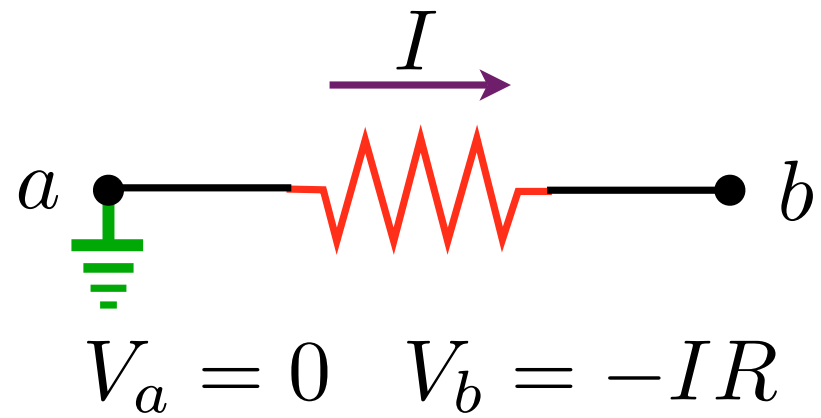


(c)

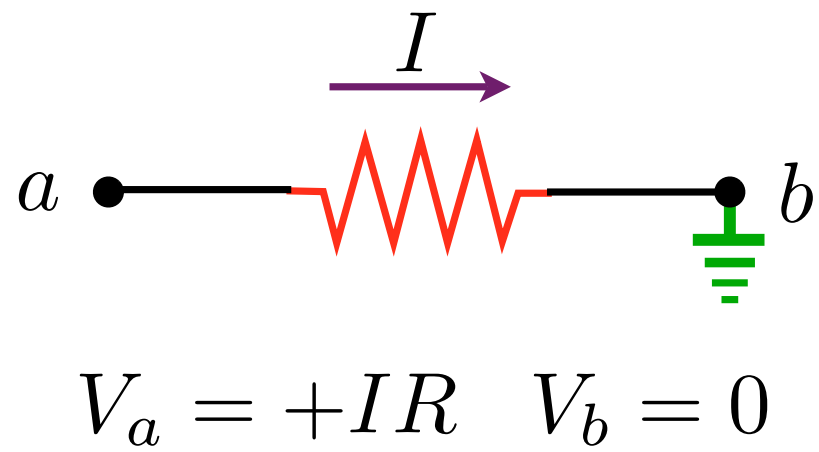

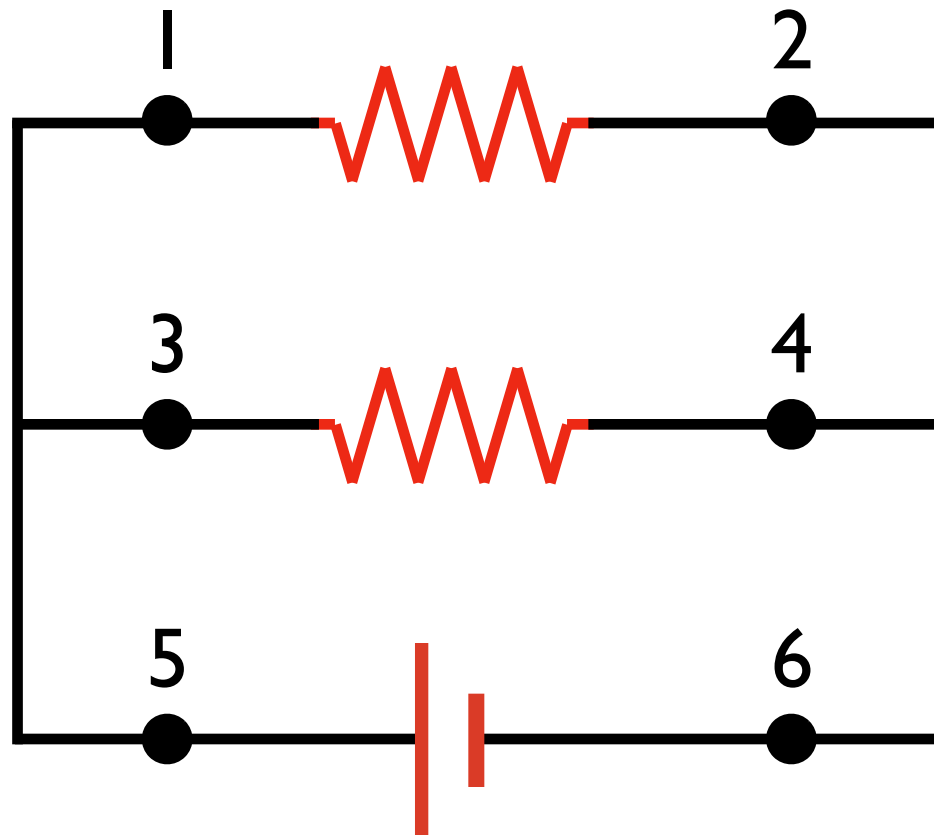


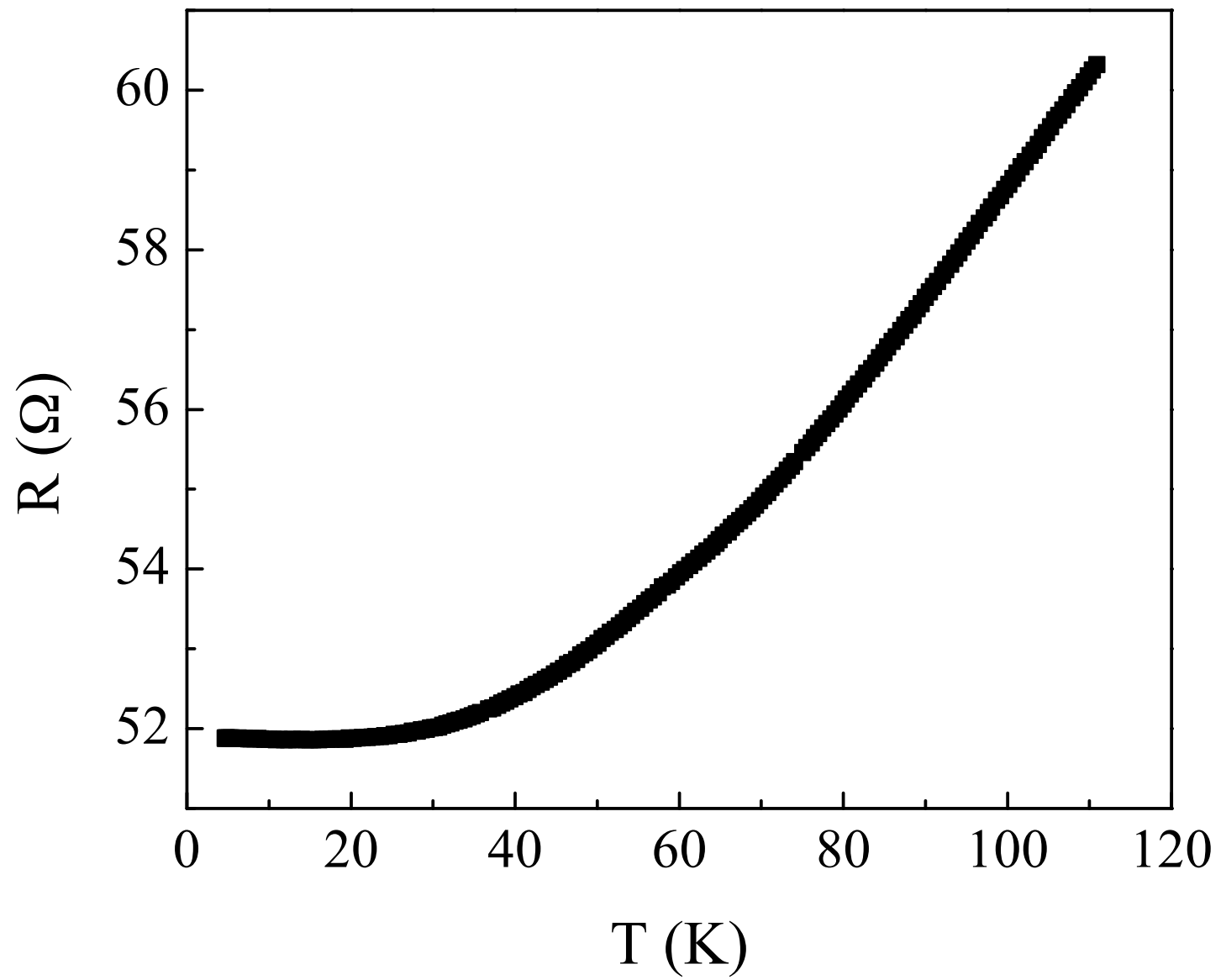


(a)

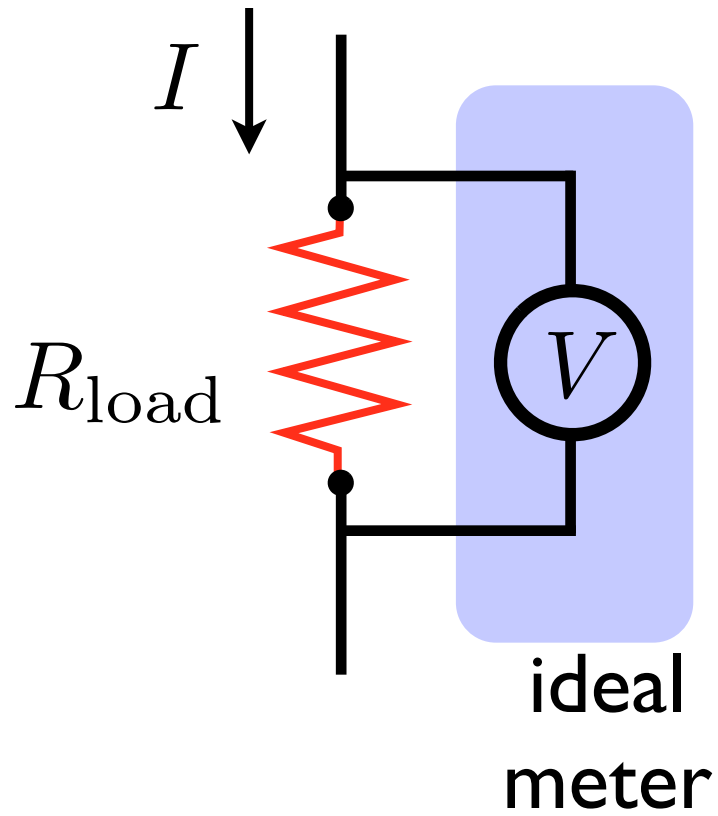

(b)

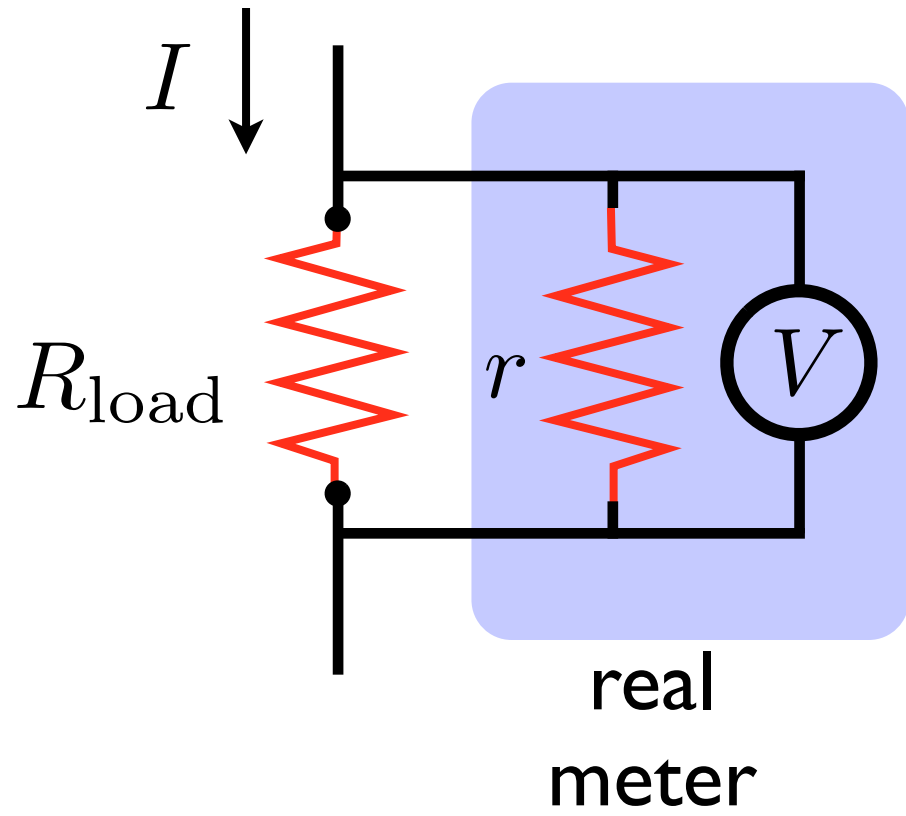


a)

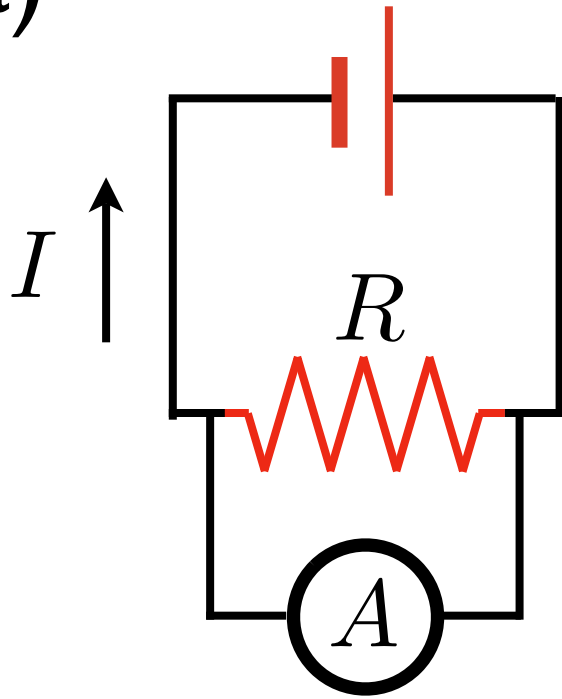



! INCORRECT !

b)

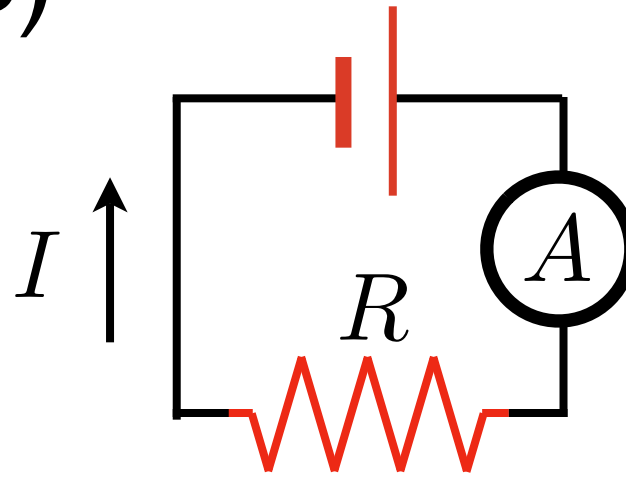

CORRECT

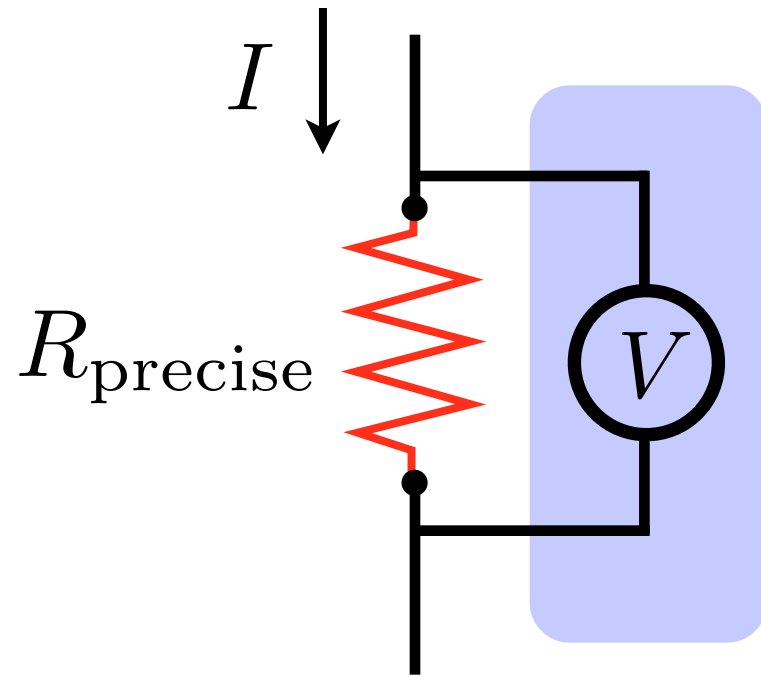

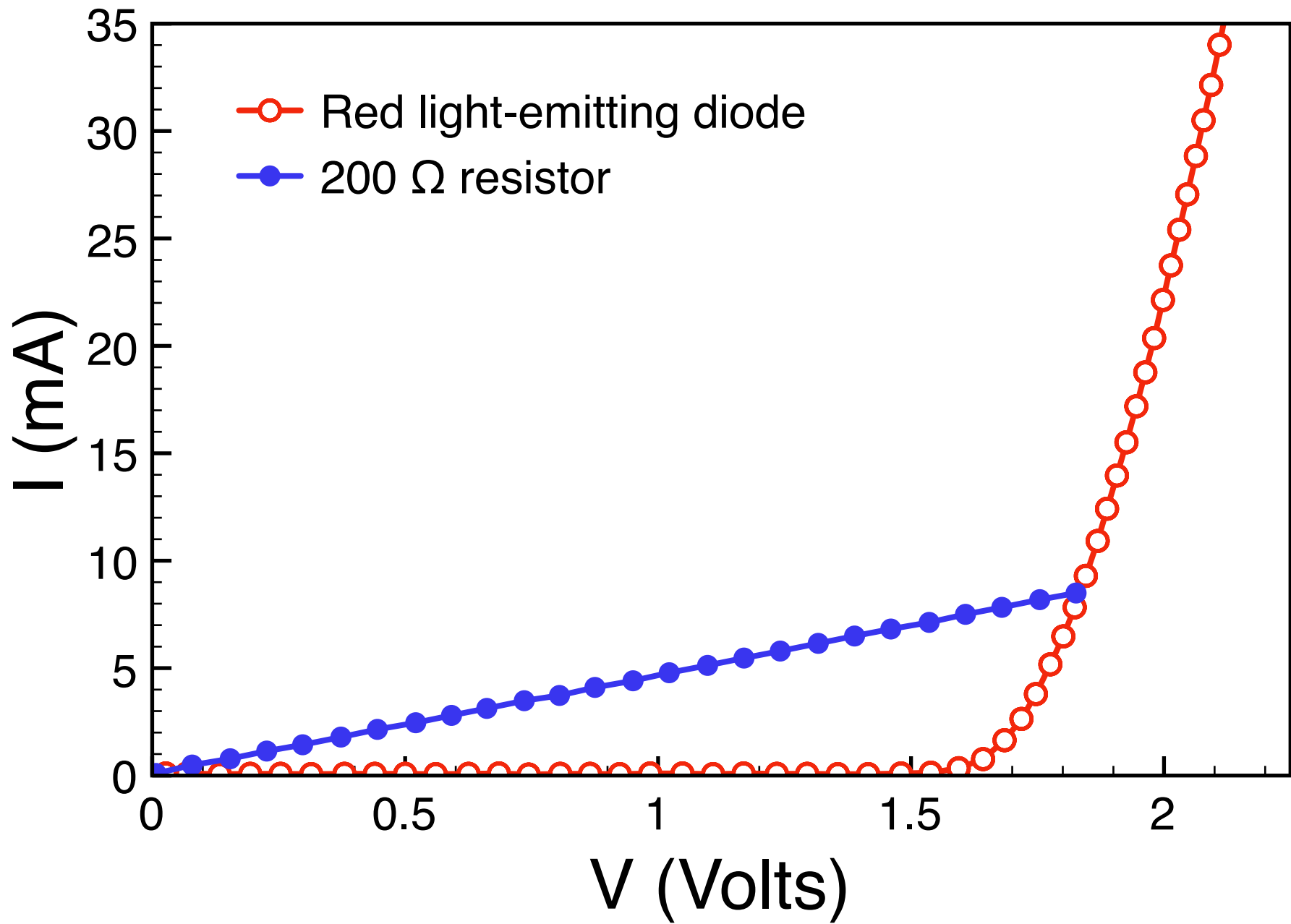


with the time left ...

let's get a jump on dc circuits

real battery = ideal battery + R



=

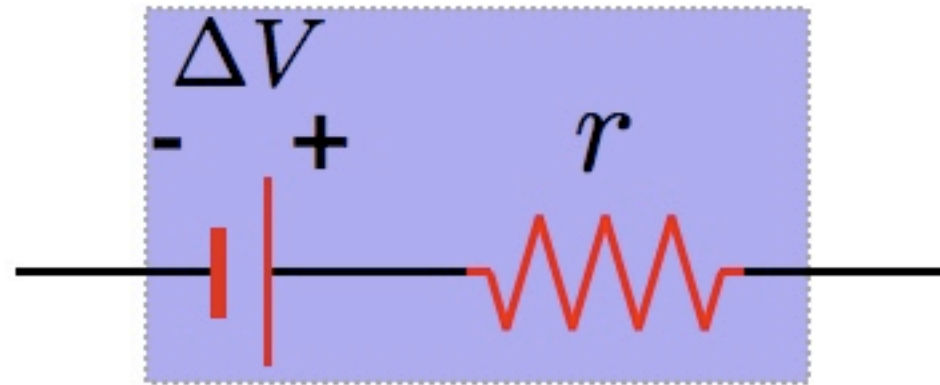


actual circuit has a parasitic r


a)




b)

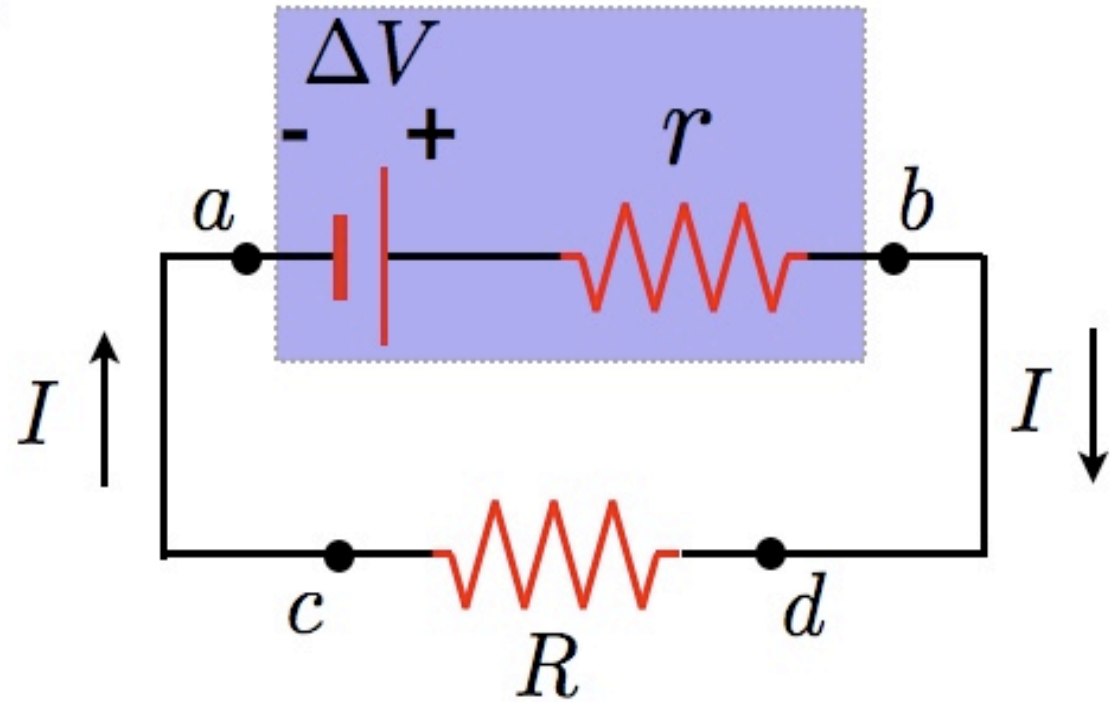

real current sources

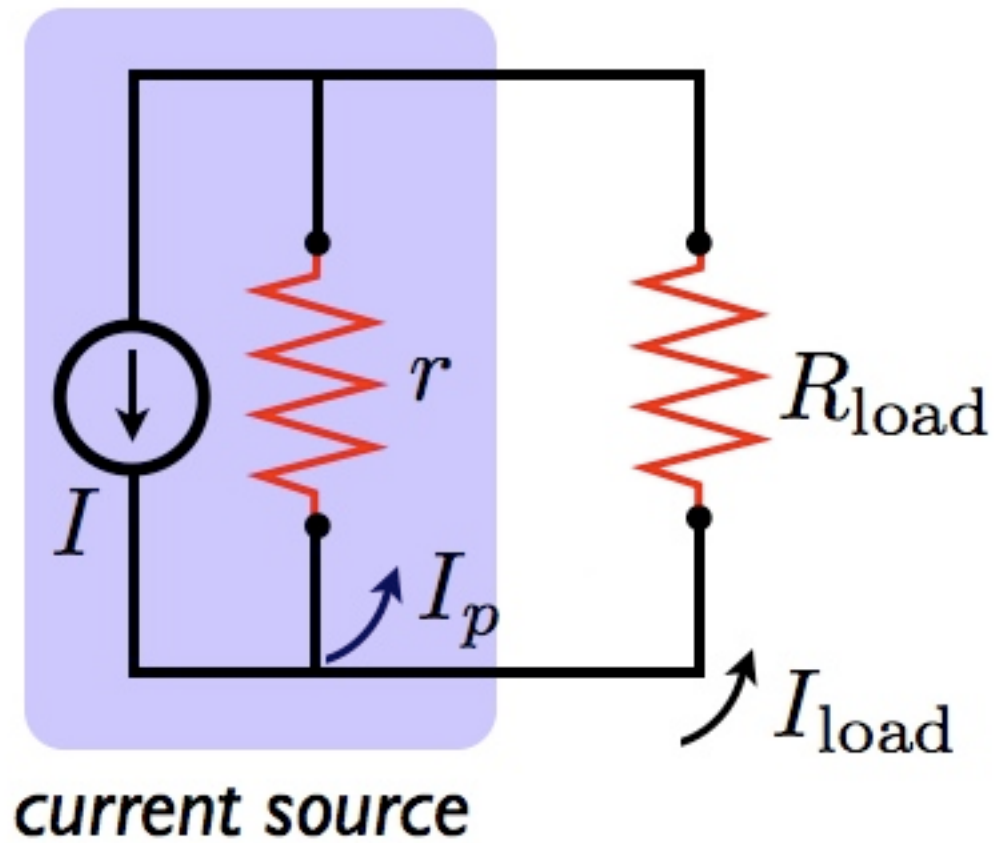

series resistors: conservation of energy

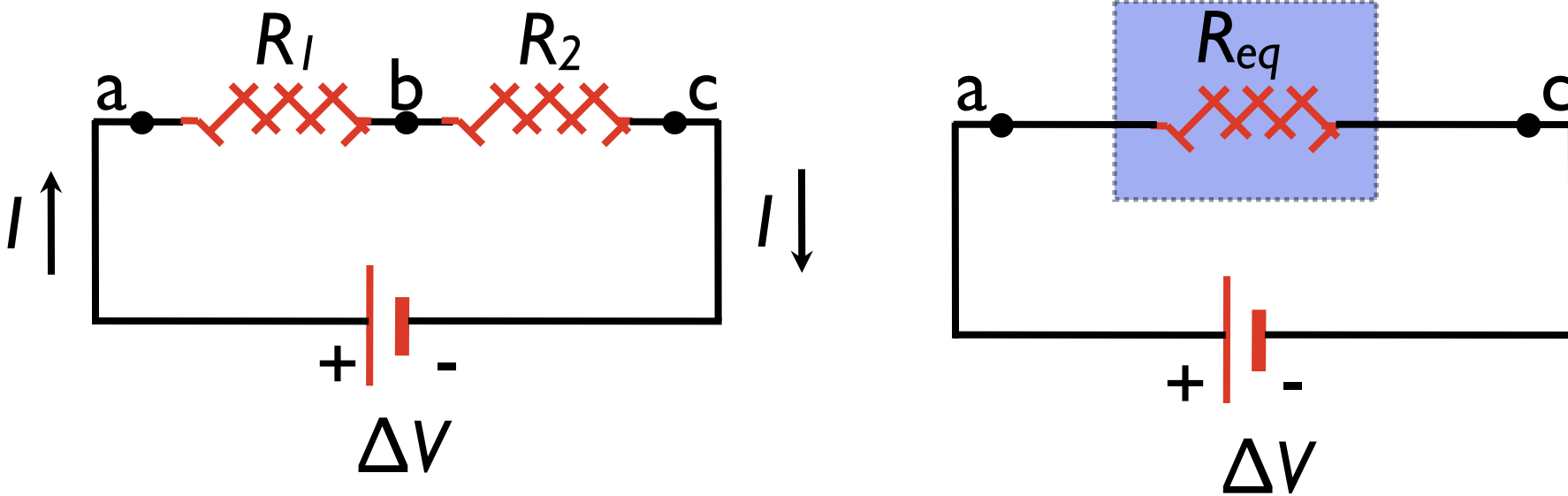

Two Resistors in Series:


$$R_{eq} = R_1 + R_2$$

Three or More Resistors in Series:


$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

The current through resistors in series is the same.

voltage divider

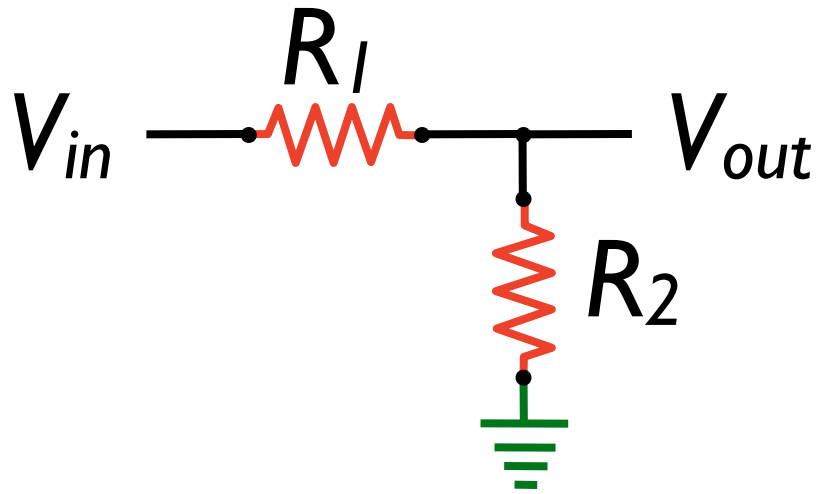

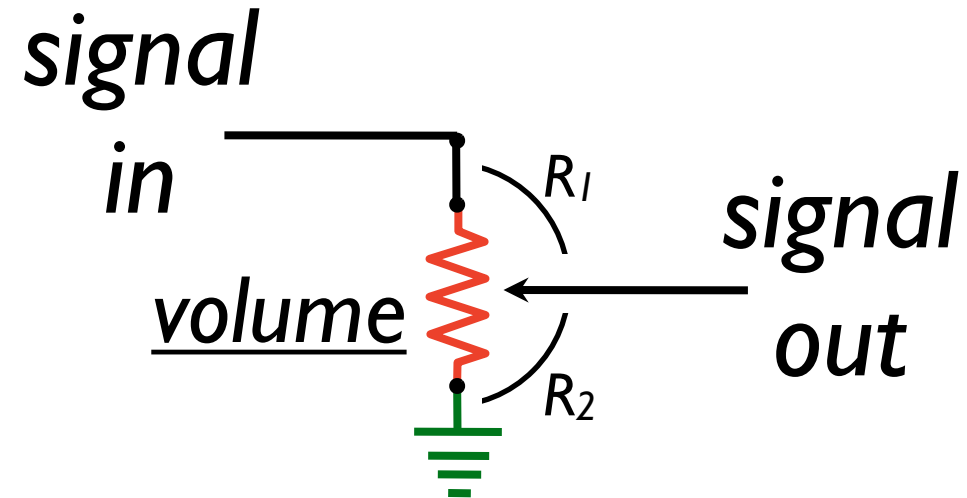
$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$




parallel resistors: conservation of charge

$$\Delta V_1 = \Delta V_2 = \Delta V$$

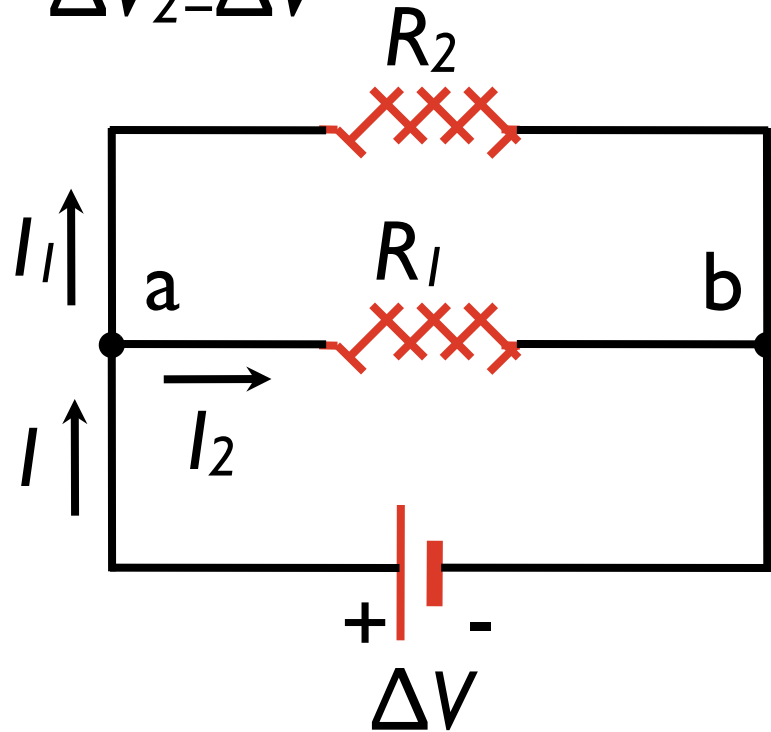
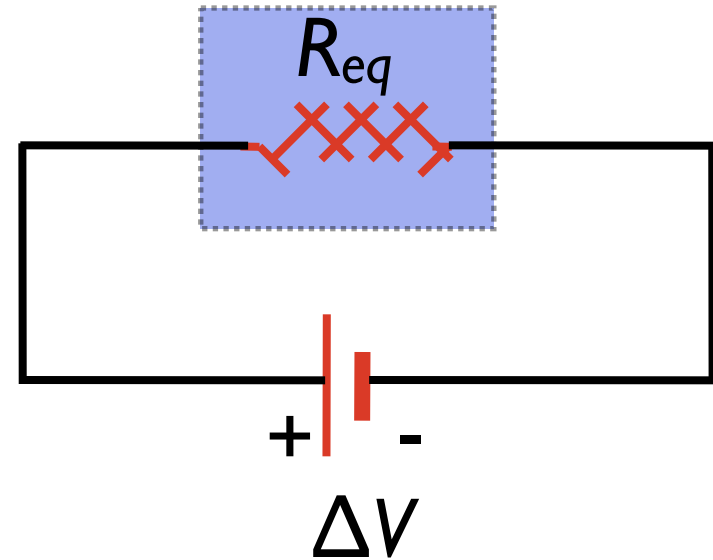
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Two Resistors in Parallel:





$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Three or More Resistors in Parallel:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

current divider


more complex arrangements

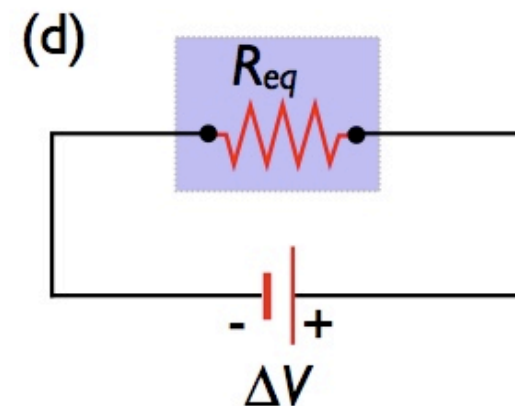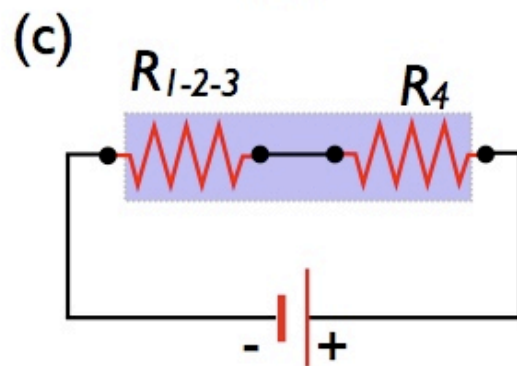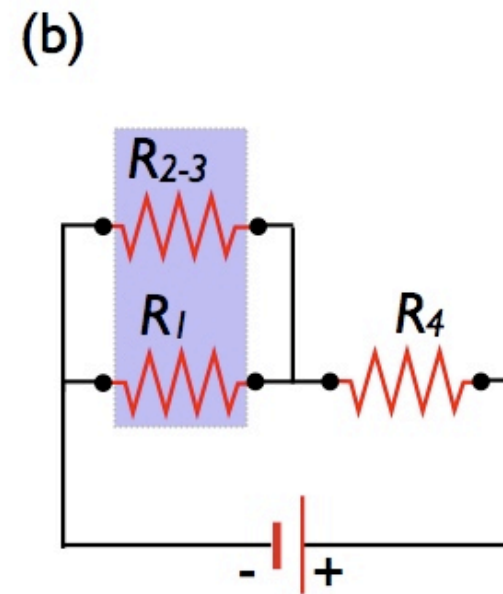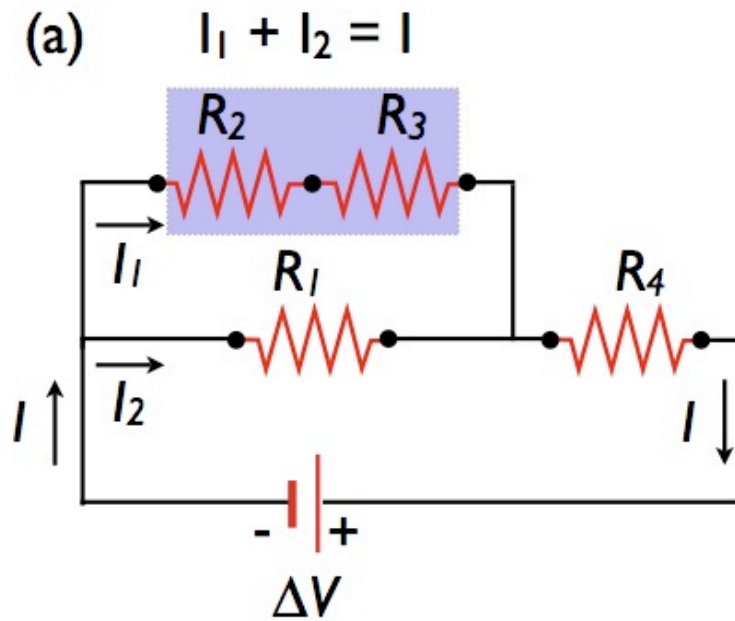

measuring voltage

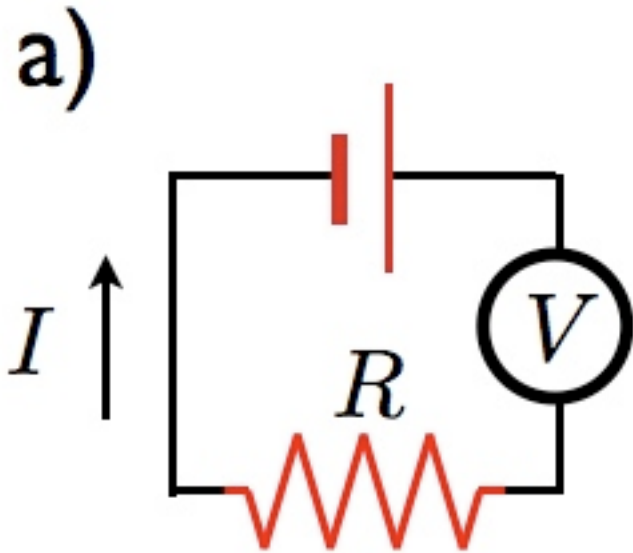


! INCORRECT !

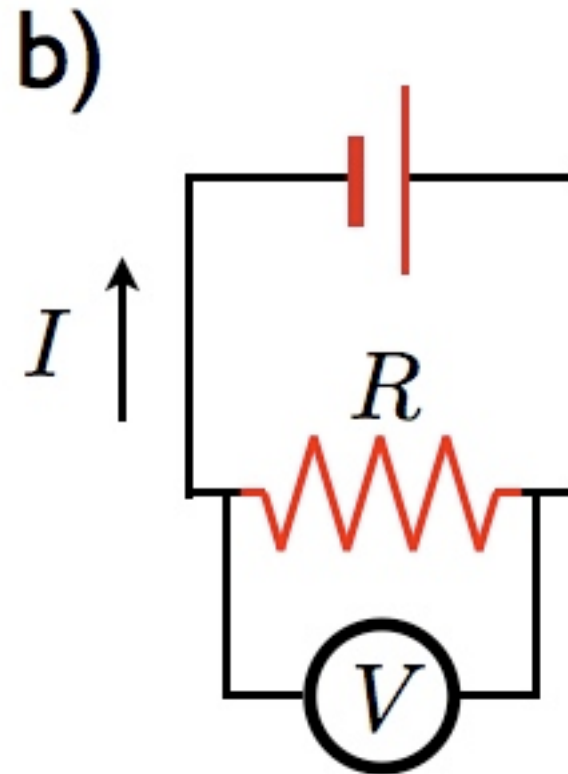


CORRECT

real voltmeters

(a)

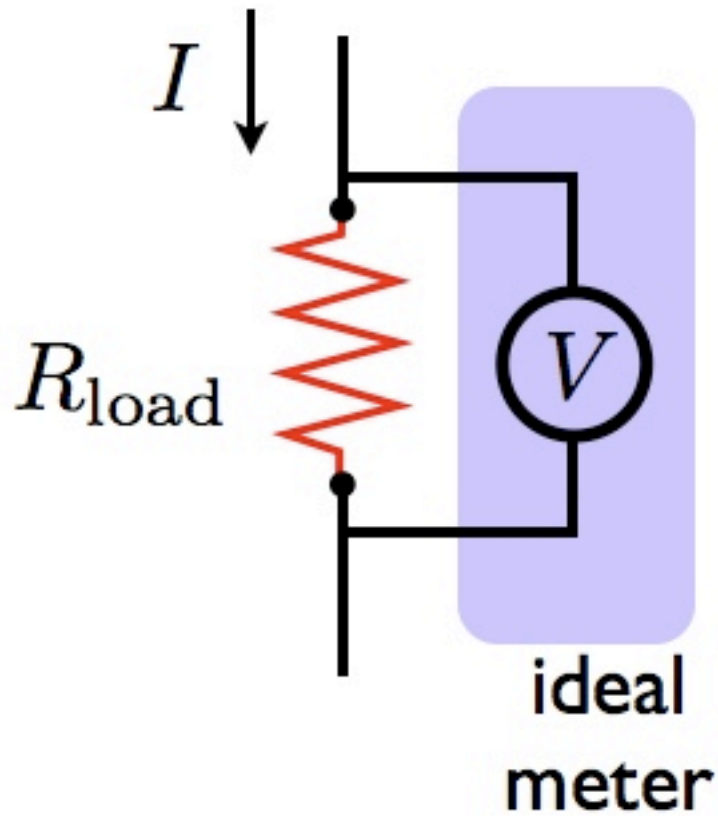


(b)

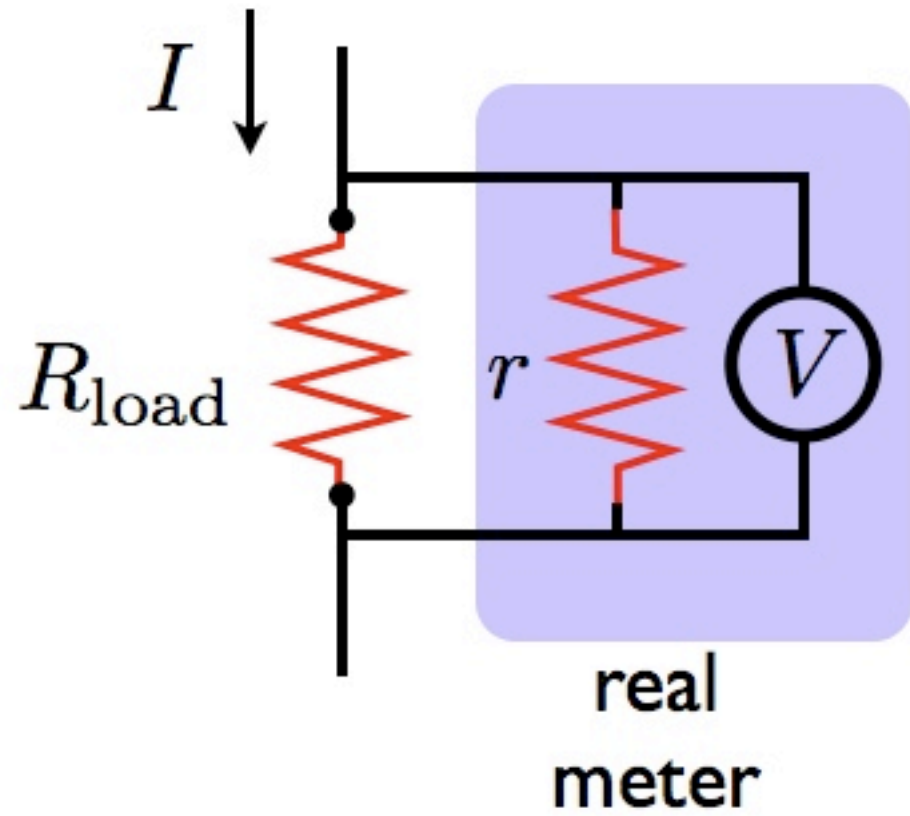


measuring current

a)

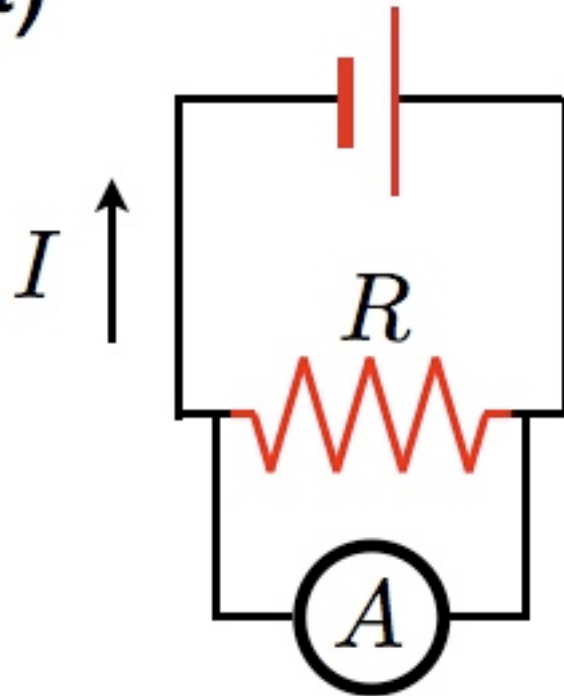


! INCORRECT !

b)

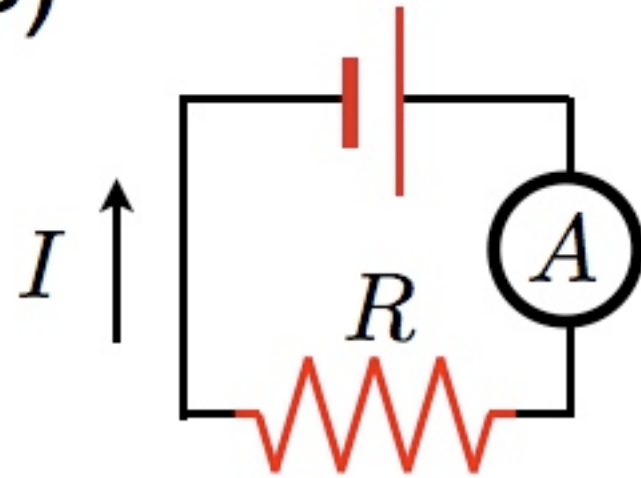


CORRECT

a simple ammeter

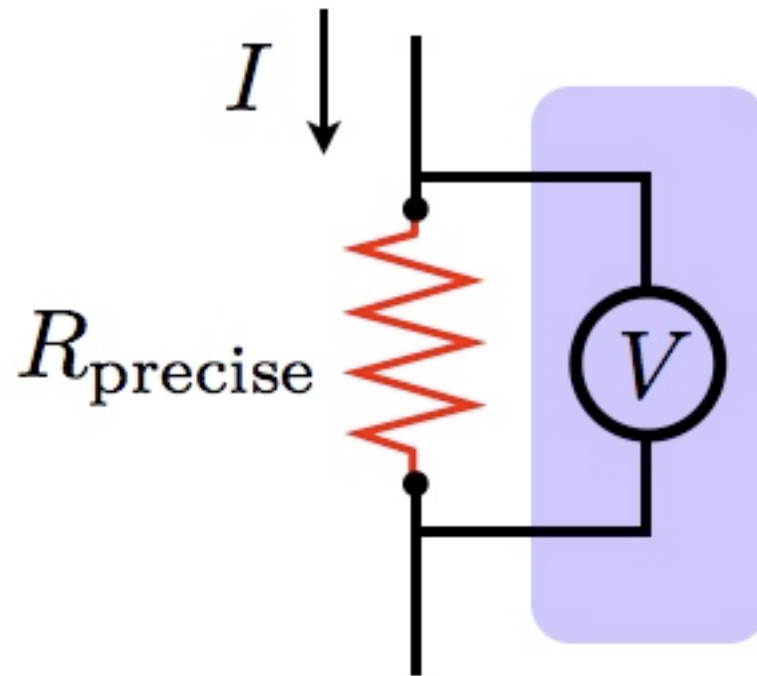

Thévenin equivalents

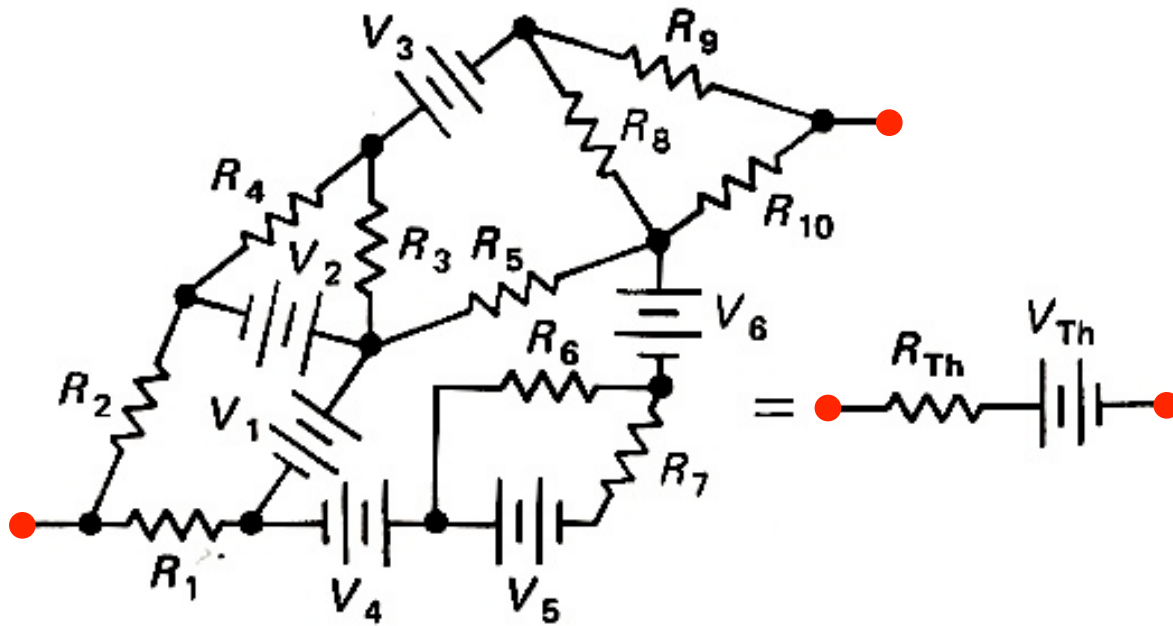


$$V_{th} = V \text{ (open circuit)}$$

$$R_{th} = \frac{V \text{ (open circuit)}}{I \text{ (closed circuit)}}$$



any weird combinations of R's and V's
is equivalent
to a
SINGLE R and V

(or a single I source
in parallel with R)

so what?

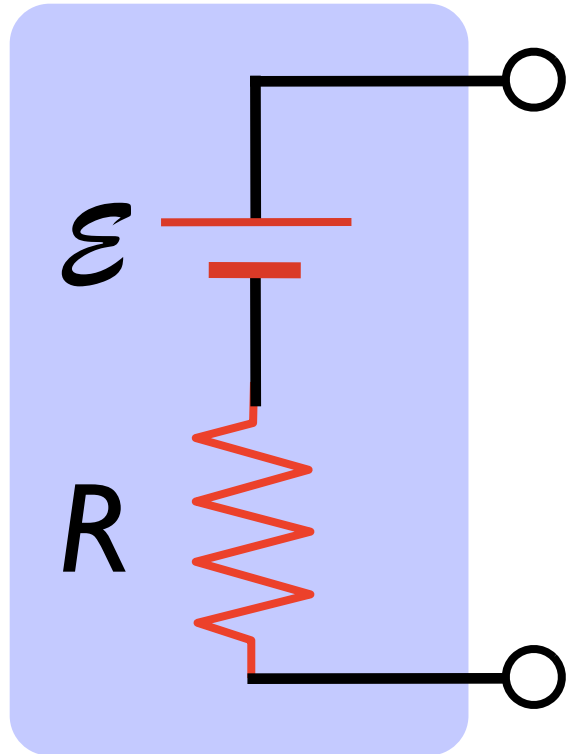


real sources =
ideal sources + R

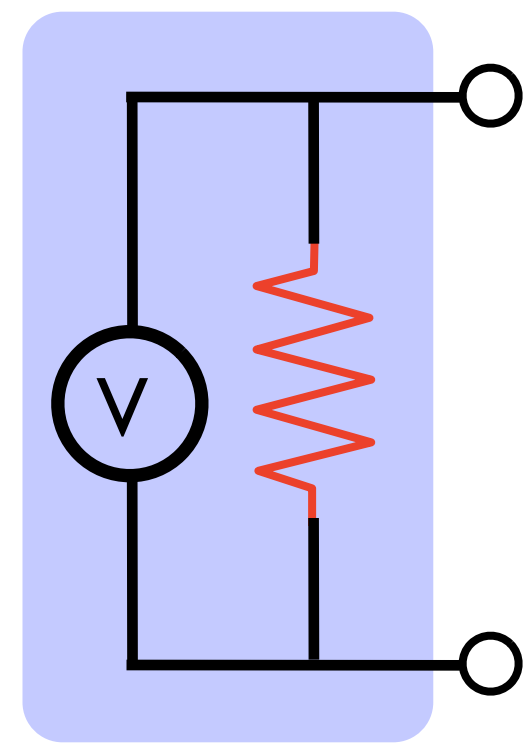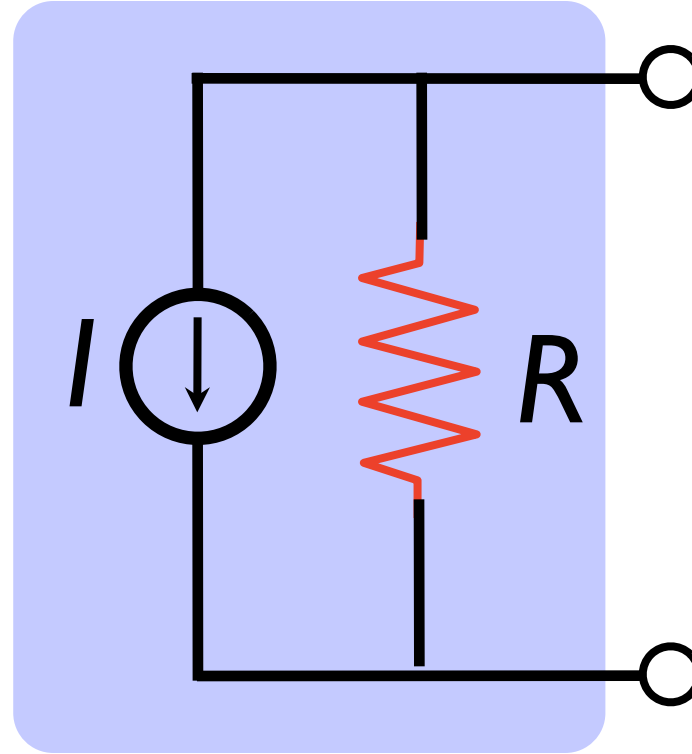

real meter =
ideal meter with R

V source loading

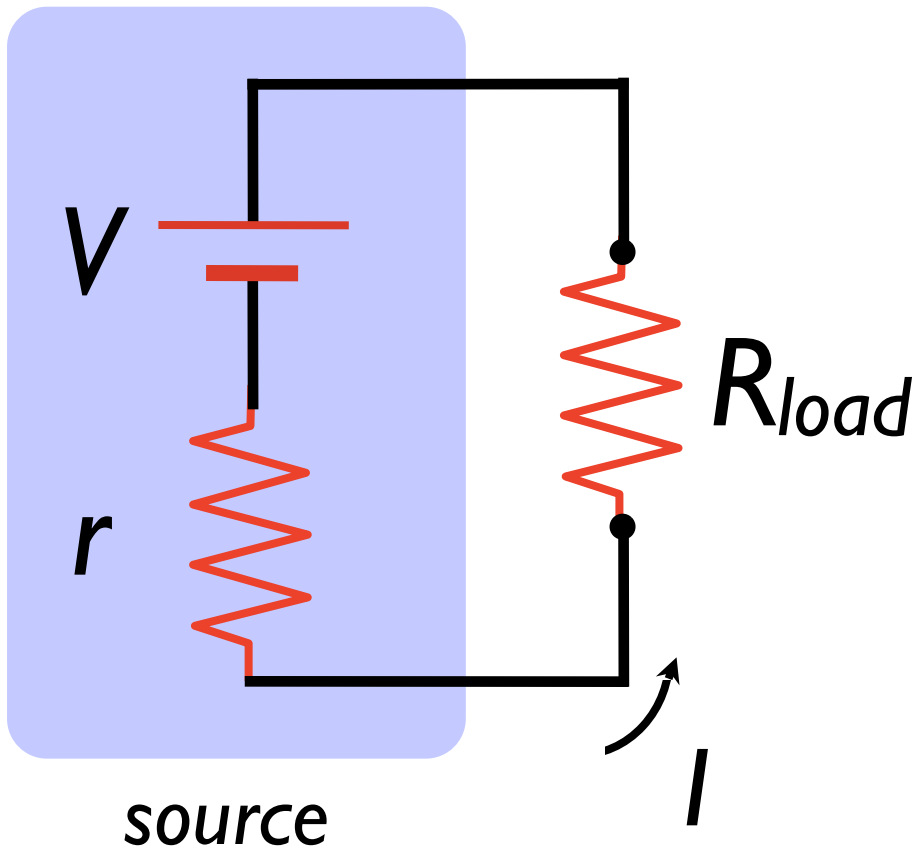

$$\Delta V_{load} = V - Ir$$

for $r \ll R_{load}$,


$$\Delta V_{load} \approx V$$

V source wants R **high**

like a battery

one easy solution:
large resistor in parallel with load

I source loading

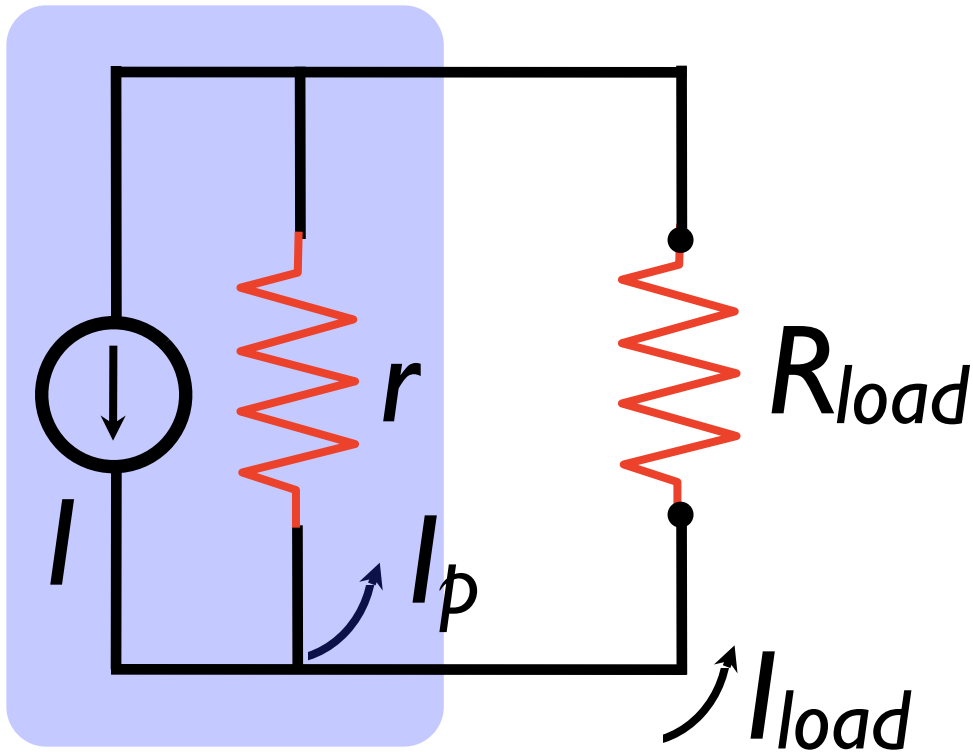

$$I_{load} = I \frac{r}{r+R}$$



for $R_{load} \ll r$,

$$I_{load} \approx I$$

source

I source wants R **low**
sourcing currents at high R_{load} is hard

measuring the meter

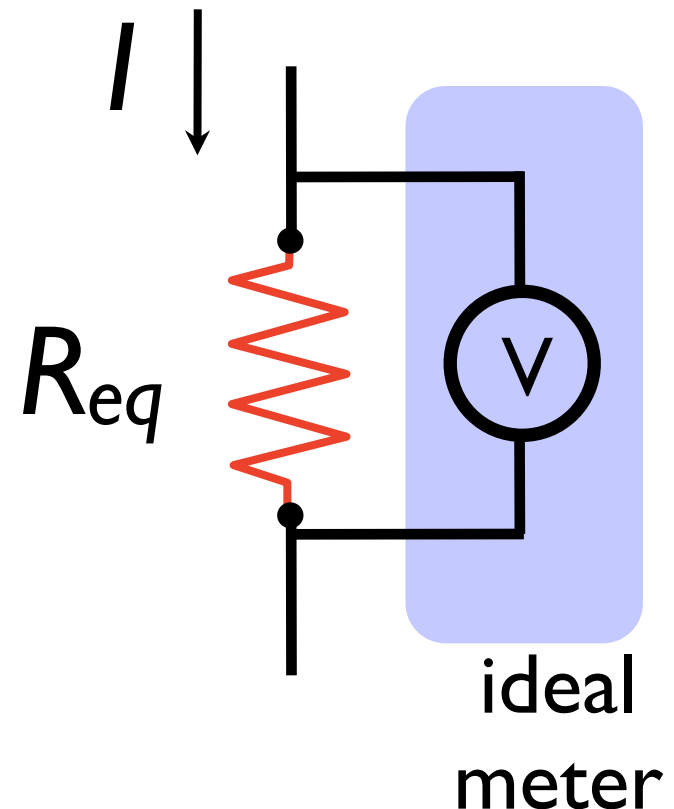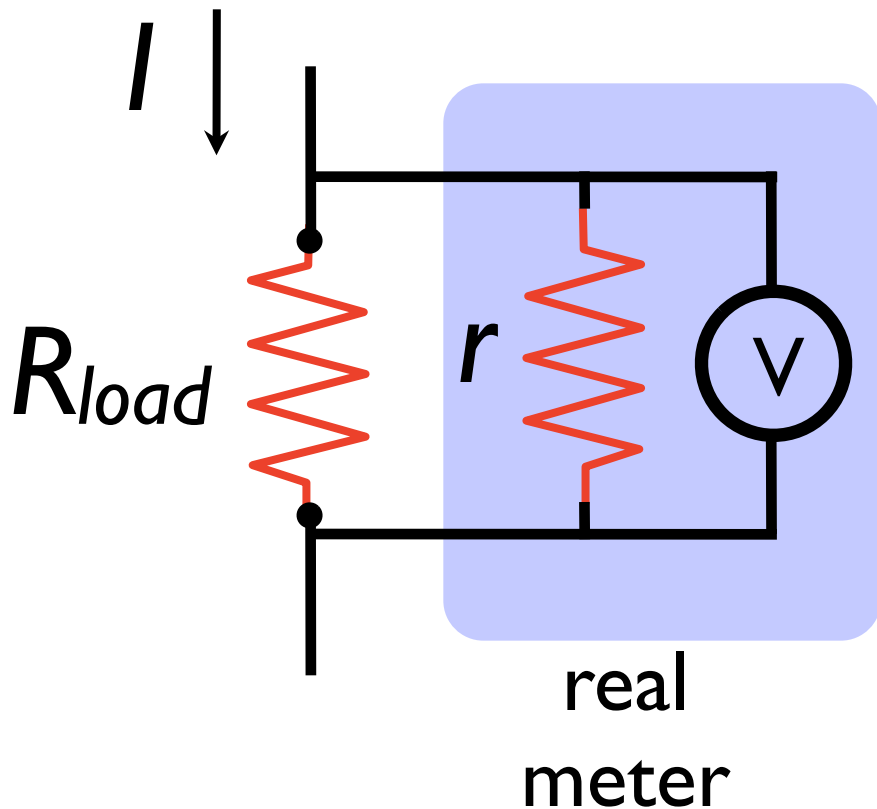

$$\Delta V_{load} = IR_{eq} = \frac{R}{1+R/r} I$$


$$R_{load} \ll r, \Delta V_{load} \approx IR$$

summary

voltmeter wants R **low!**
can use a buffer/follower

I source wants R **low**
transformer pre-amp
consider sourcing V

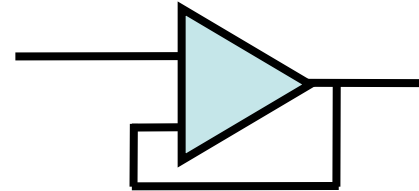
V source wants R **high**
large series + parallel resistors
present large R



Sourcing current


This is what a hand meter does.

Why is it no good?

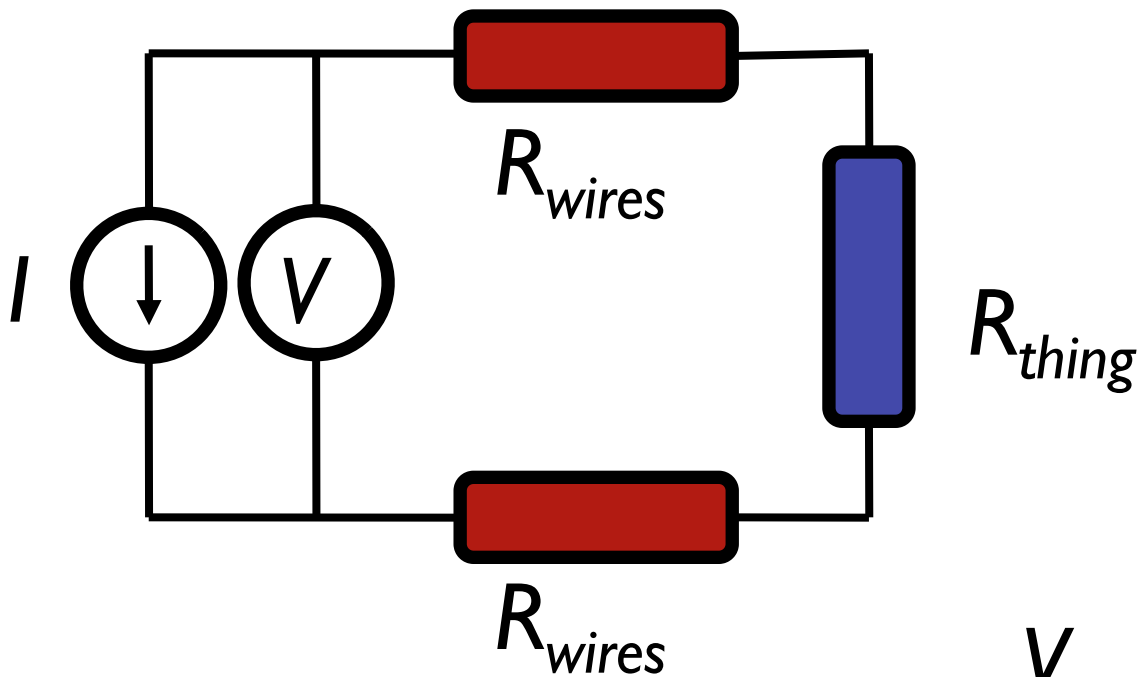

$$V_{meter} = I(R_{thing} + 2R_{wires})$$


Sourcing current, properly

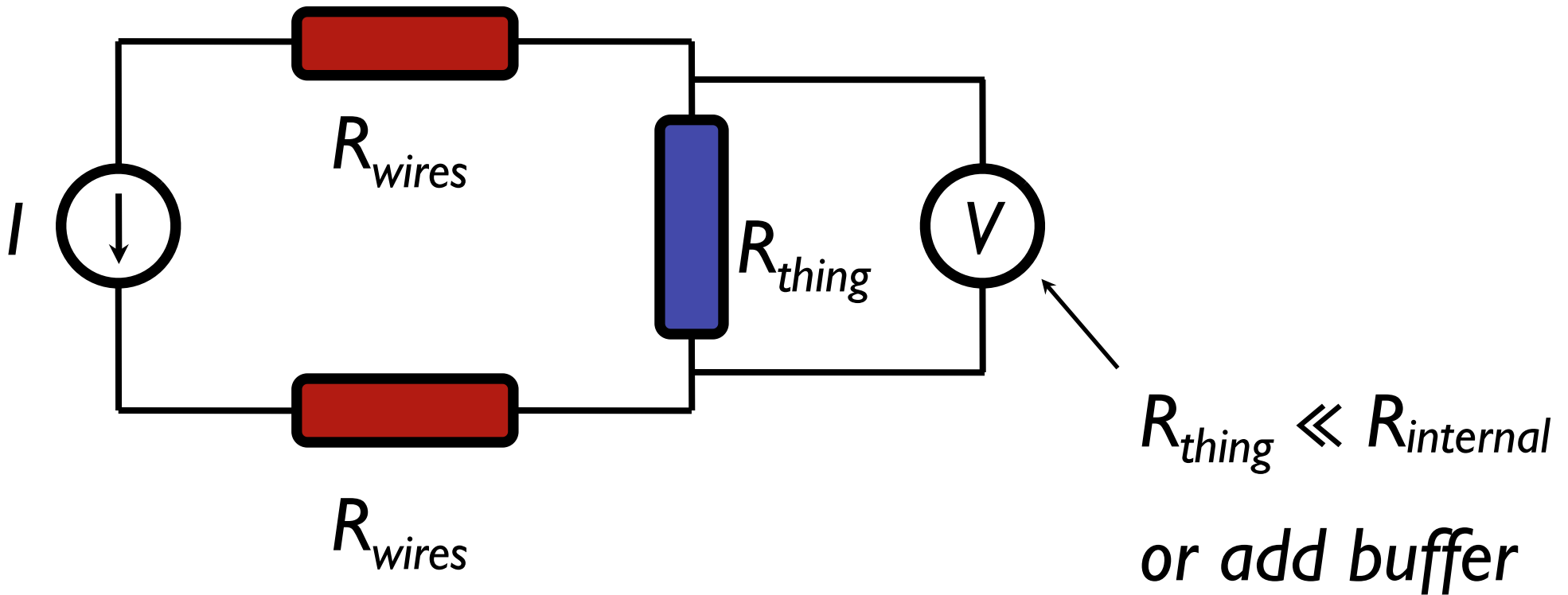

No problem.
You just need four wires.


What is still wrong?

Sourcing voltage

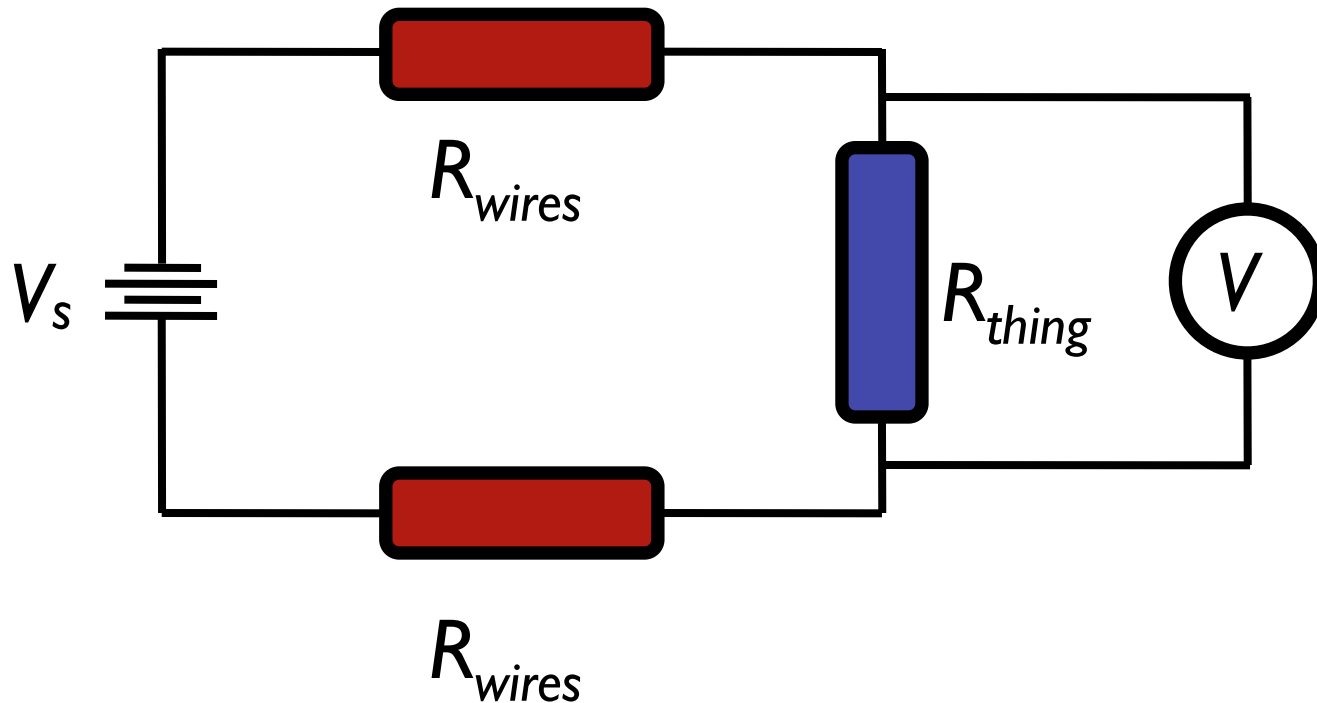



Still have to measure voltage on device
the wires still use up some of V
What about current?

Sourcing voltage II

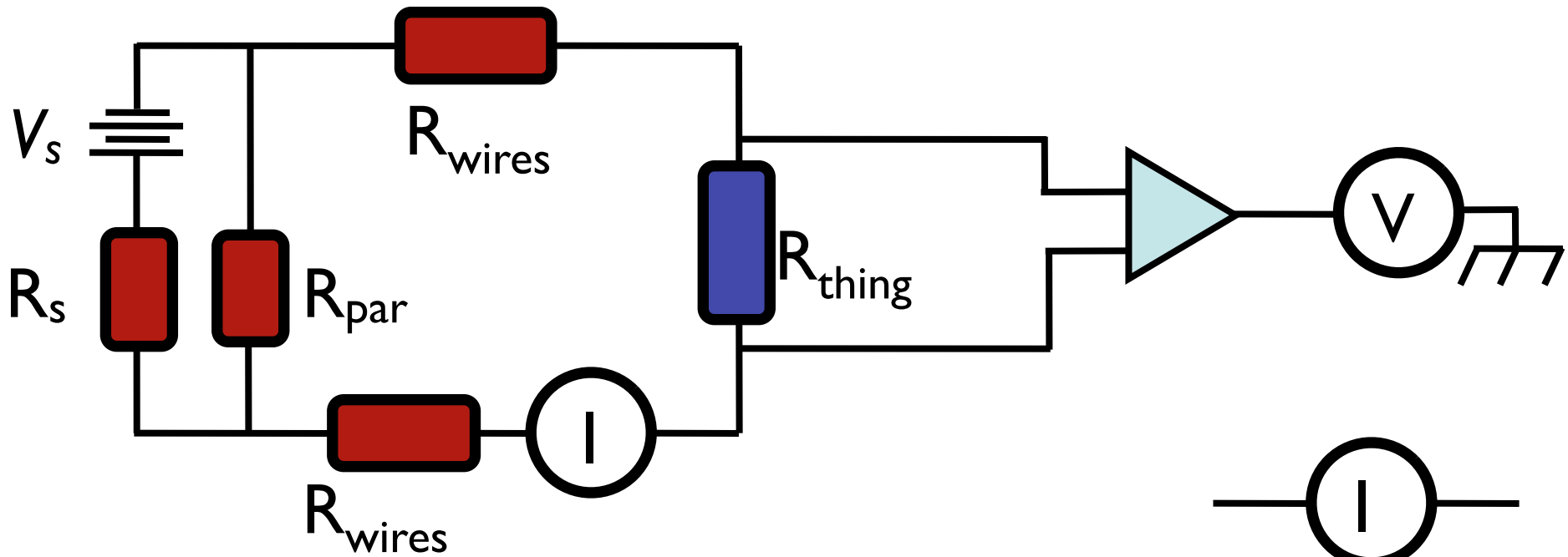

$$R = \Delta V / I$$

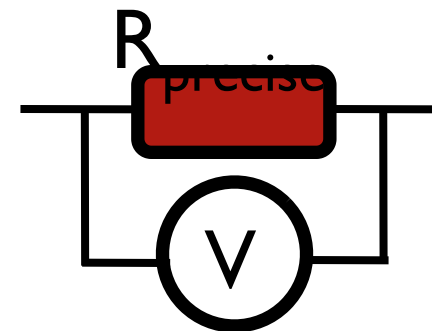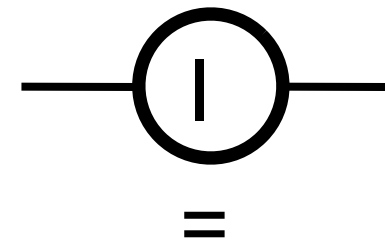Note we need 4 wires again
current meter - not hard
still problems?




source/meter resistances

voltmeter wants R low
but V source wants R high

need buffer/amp on V meter
resistor in parallel with source

if V source is problem, R is too low
consider sourcing I

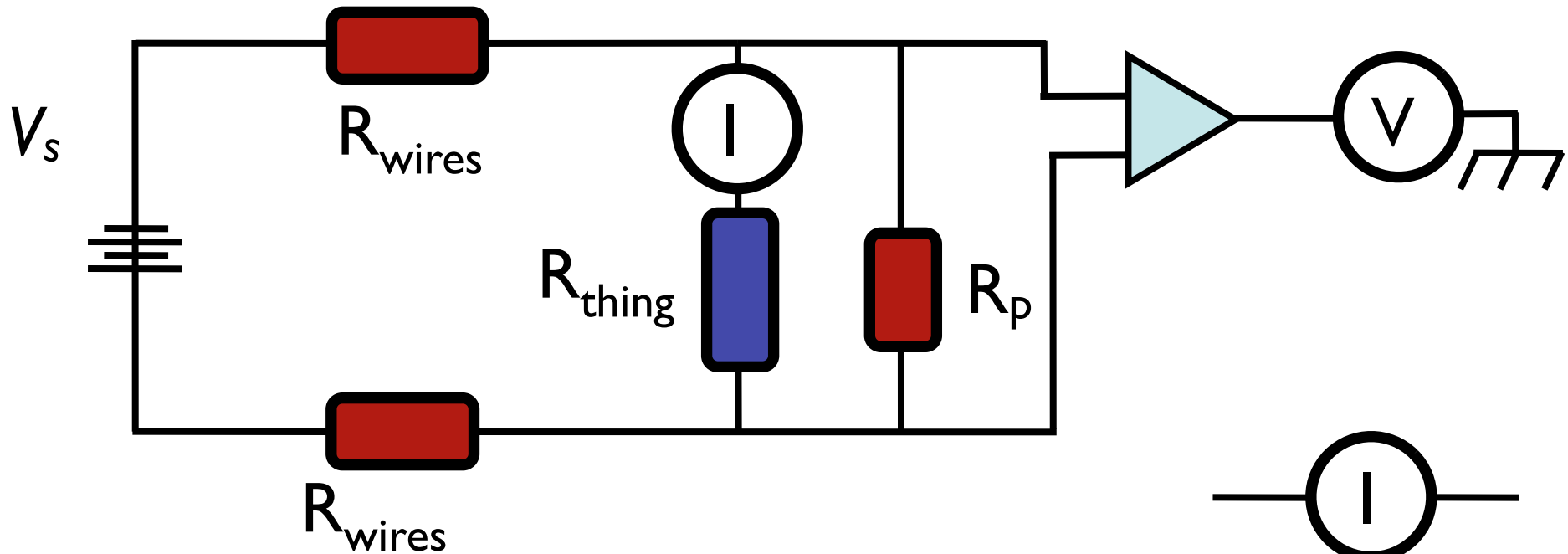what if I want to measure a **really** high R ?




source *voltage*


R_p has same voltage as R_{thing}

R_s has same current

have done $> 10^{10}$ Ohm

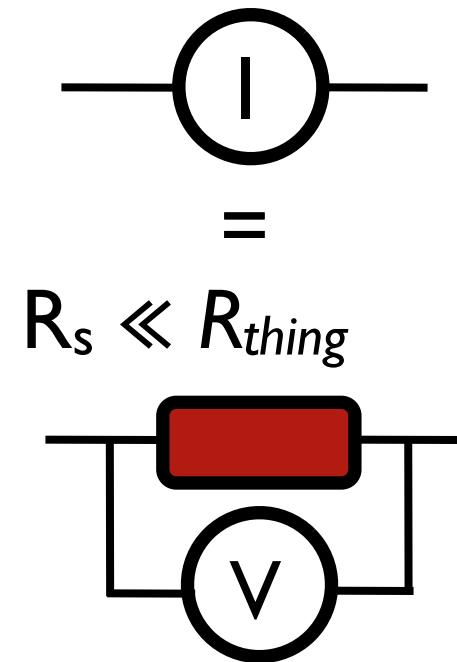


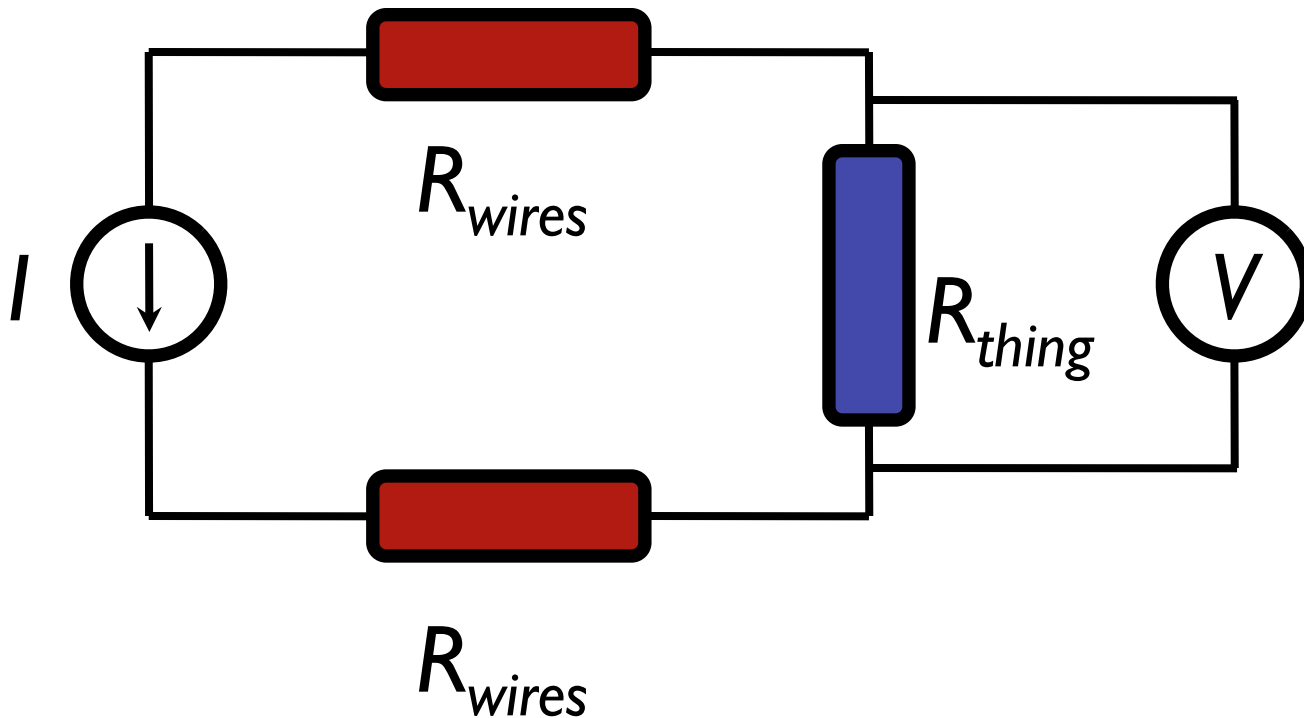what if I want to measure a **really** low R?




this works just fine ...
so long as your V meter is good
v. good amp / part of a bridge

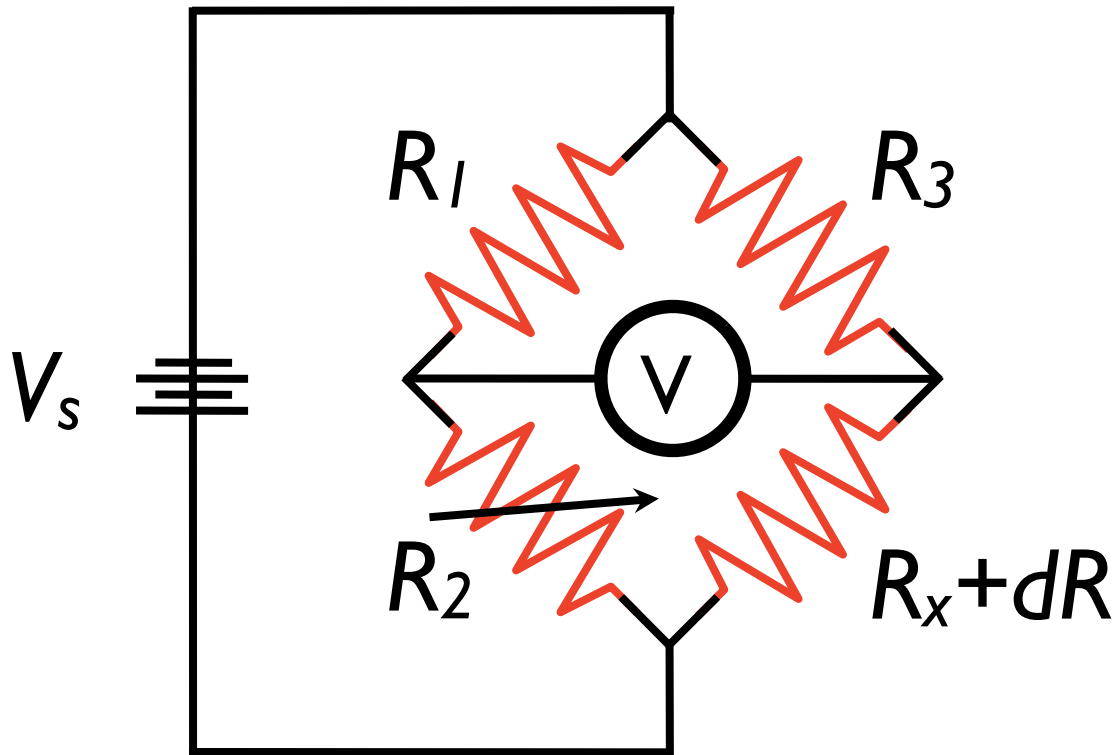what if I want to measure a small change in R?



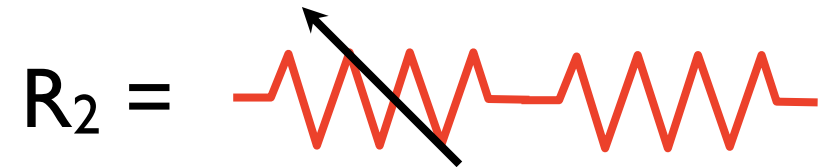balance bridge to $V=0$
 detect small changes from null



make R_1-R_3 about the same
 trimming resistor on $R_2 = dR$

$$V = \left(\frac{R_x}{R_3 + R_x} - \frac{R_2}{R_1 + R_2} \right) V_s$$

$$R_x = \frac{R_3 R_2}{R_1}$$

