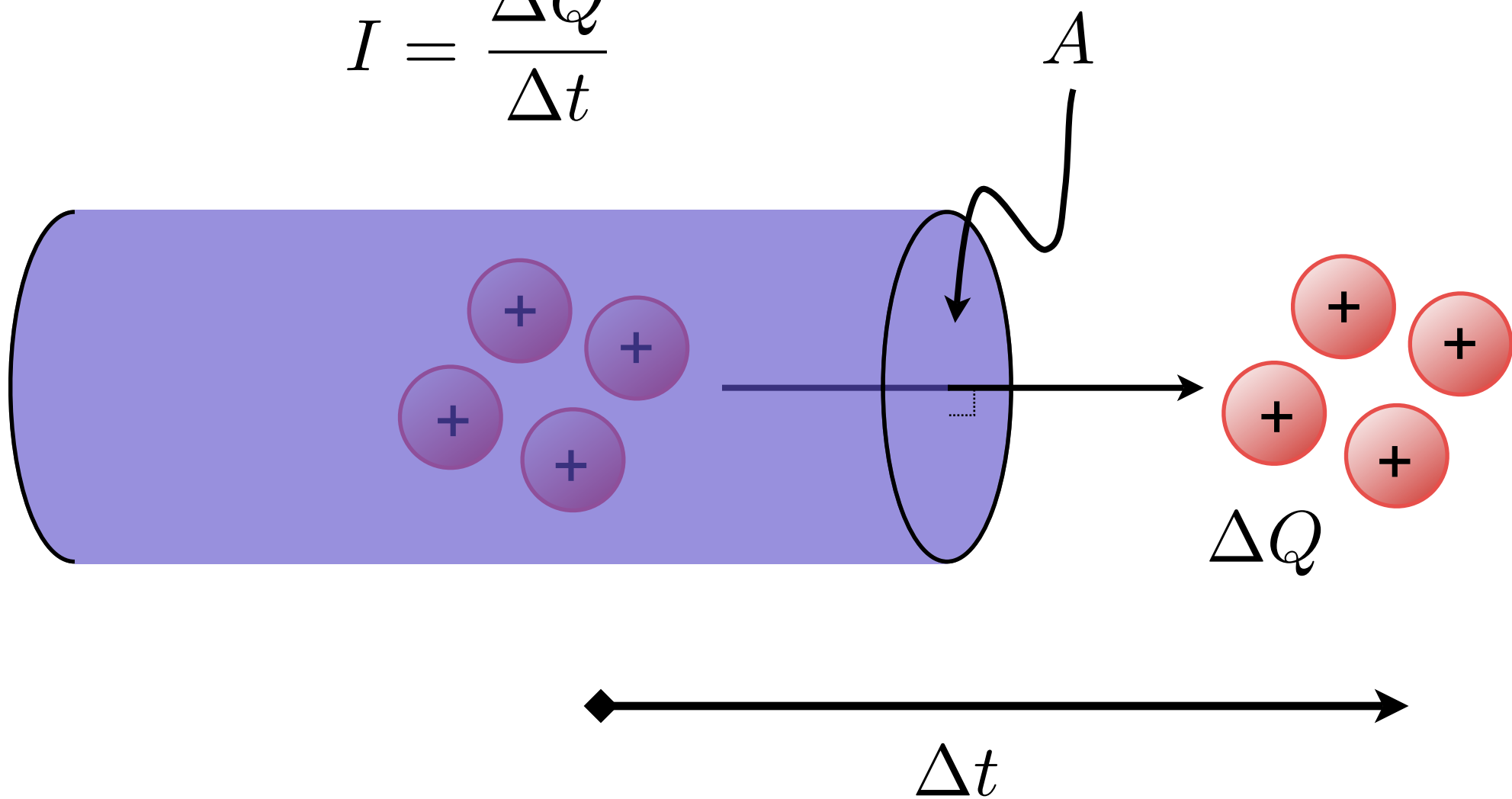



today: dc circuits

mostly current &
resistance


$$I = \frac{\Delta Q}{\Delta t}$$




$+x$

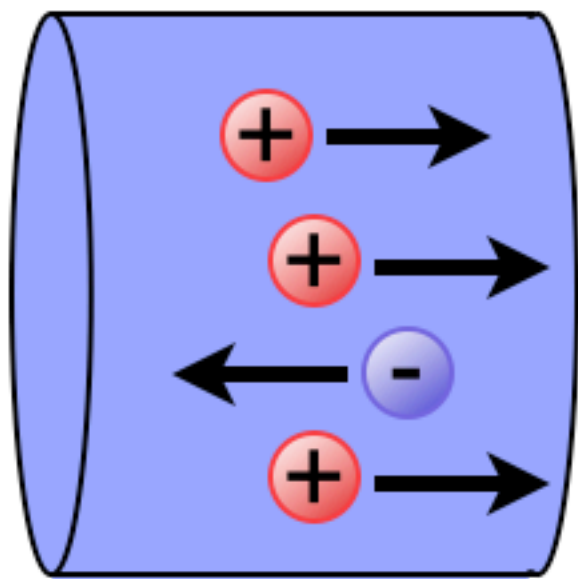

A

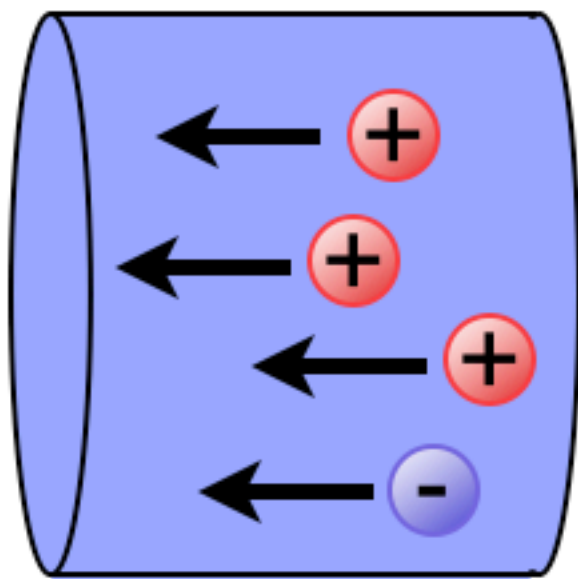

B

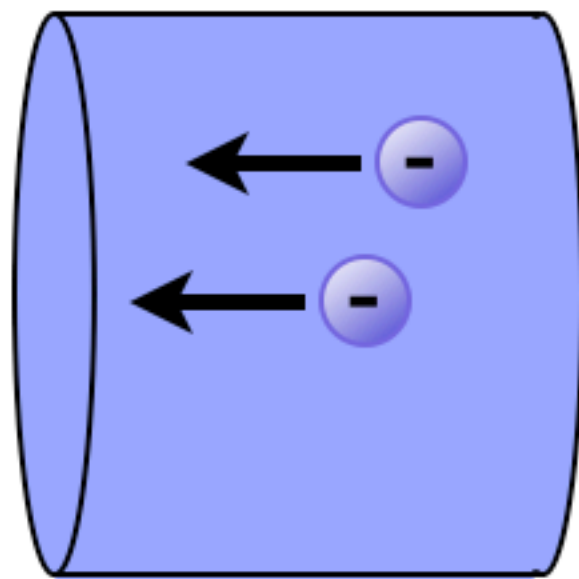

C

BENJAMIN FRANKLIN?

I BRING A MESSAGE
FROM THE FUTURE!
I DON'T HAVE MUCH TIME.

YES?

WHAT IS IT?


THE CONVENTION YOU'RE SETTING
FOR ELECTRIC CHARGE IS BACKWARD.
THE ONE LEFT ON GLASS BY SILK
SHOULD BE THE *NEGATIVE* CHARGE.




WE WERE GOING TO USE THE TIME MACHINE TO
PREVENT THE ROBOT APOCALYPSE, BUT THE
GUY WHO BUILT IT WAS AN ELECTRICAL ENGINEER.

not so funny now.

just wait ...

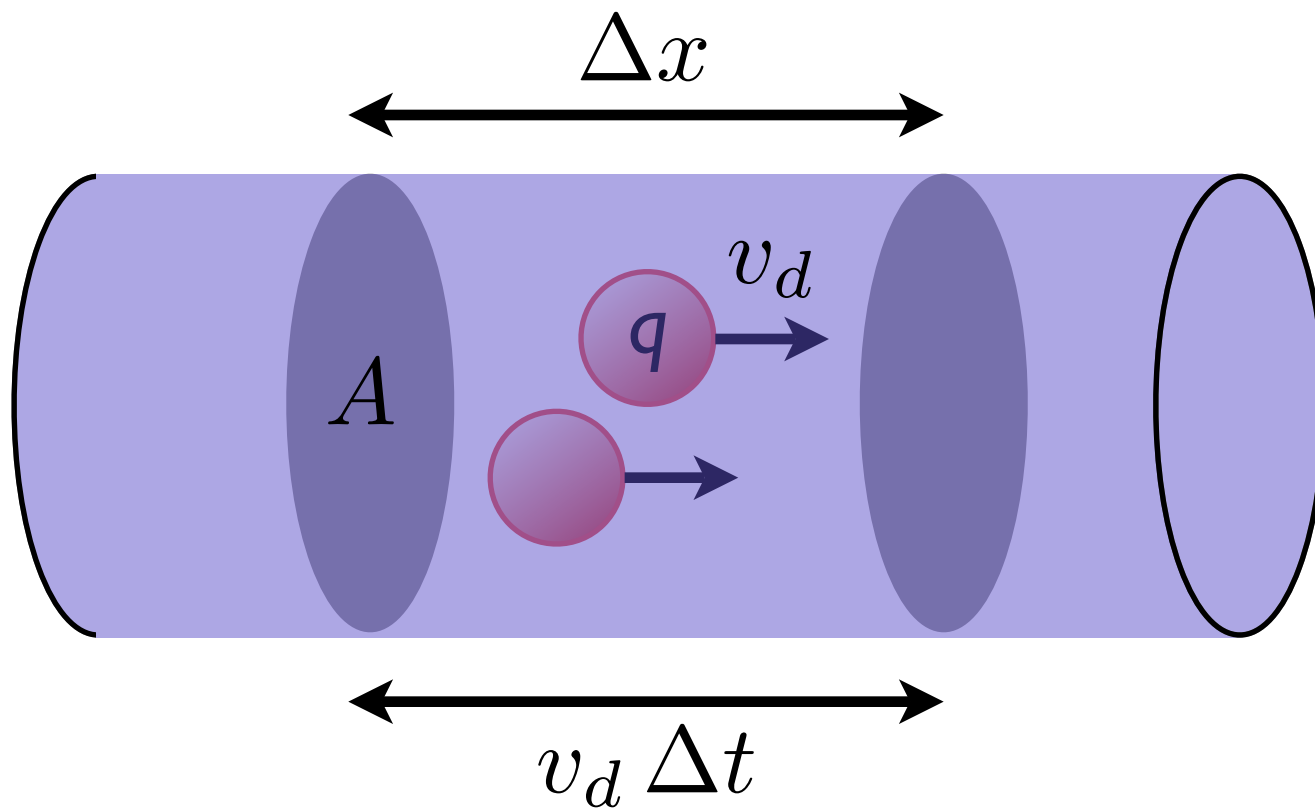

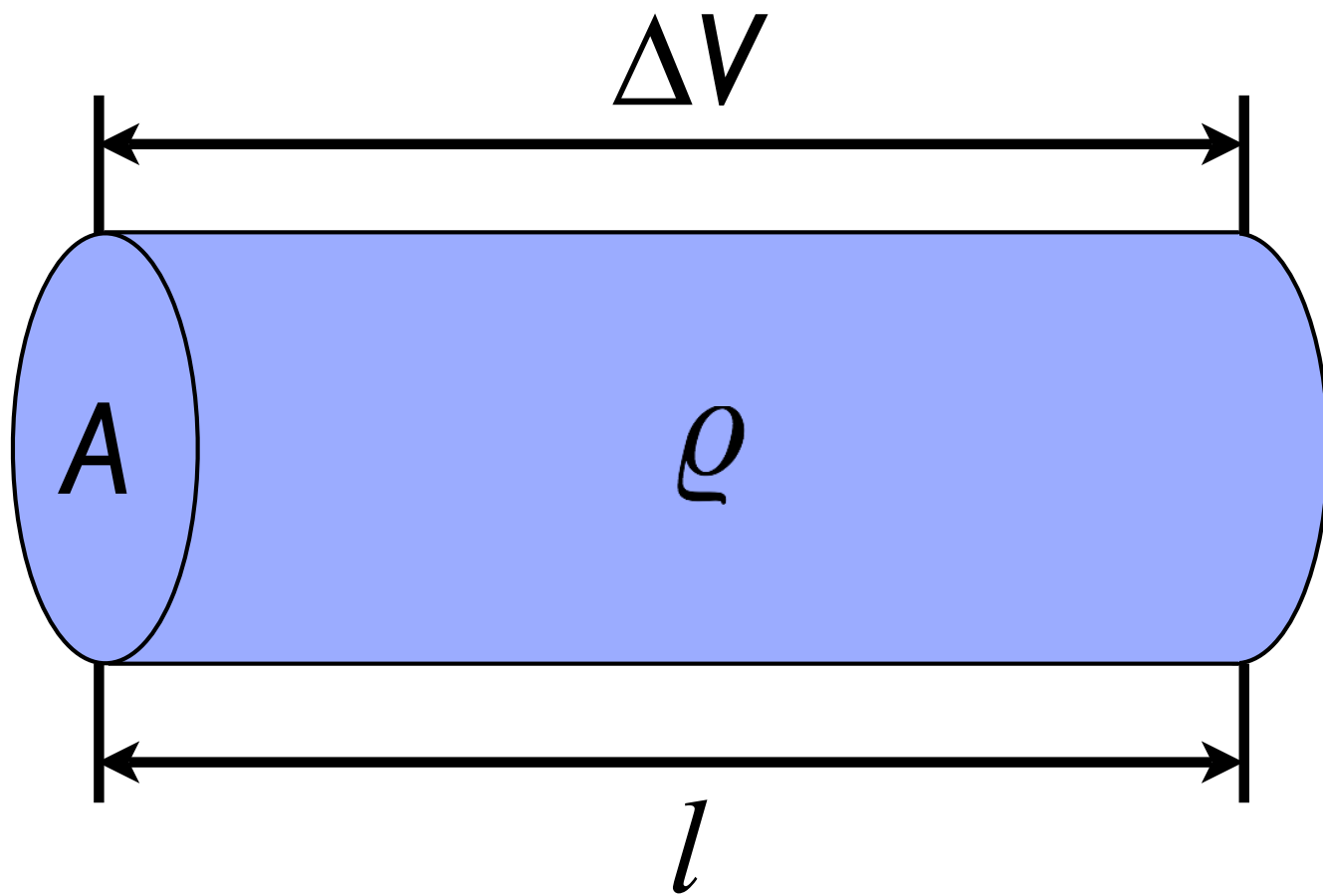


$$R = \frac{\rho l}{A} = \frac{\Delta V}{I}$$


$$I = \text{Cause}/\text{Resistance}$$

I is the current, or flow rate,
describes different scenes:


(a) Heat flow
through
a wall

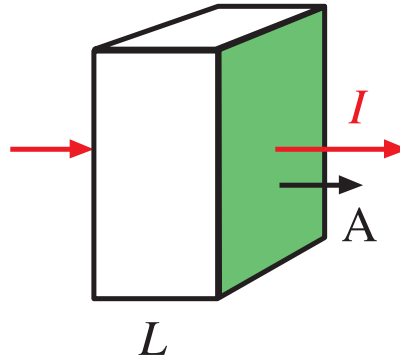

(b) Charge
flow
through
a wire

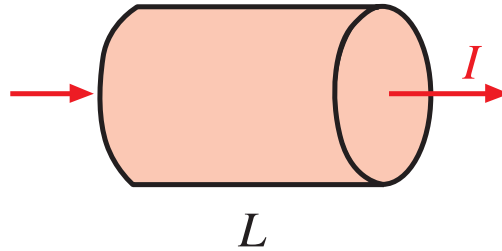

(c) Fluid
flow
through
a pipe

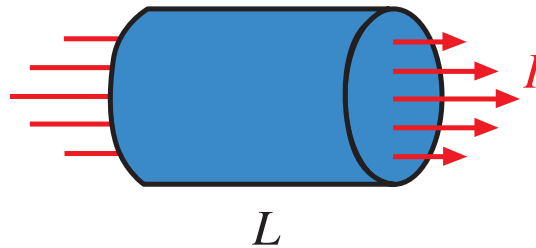



Resistance R
has the same form in most cases,

$$R = \rho L/A$$


Transport what?	Heat	Electric charges	Displacement of a molecule in a fluid	Volume of fluid
Current form (items/second)	$I = -\Delta T/R$	$I = -\Delta V/R$	$v_{av} \equiv I = -\Delta P/R$	$I = -\Delta P/R$
Current units	J/s or W	C/s or amperes	m/s	m³/s
Resistance form	$R = \rho L/A$	$R = \rho L/A$	$R = \rho L/A$	$R = \rho L/A^2$
Detail of ρ (resistivity)	$\rho = 1/\text{heat conductivity}$	$\rho = \text{electrical resistivity}$	$\rho = 6\eta\pi$	$\rho = 8\eta\pi$

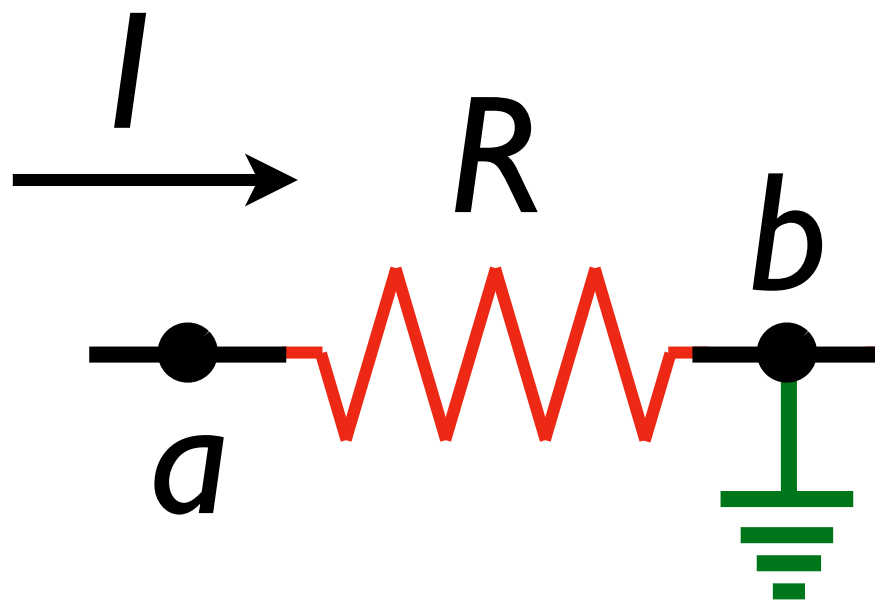battery = pump
 voltage = pressure
 current = flow
 resistor = constriction
 capacitor = diaphragm / flexible reservoir
 diode = check valve
 inductor = paddle wheel




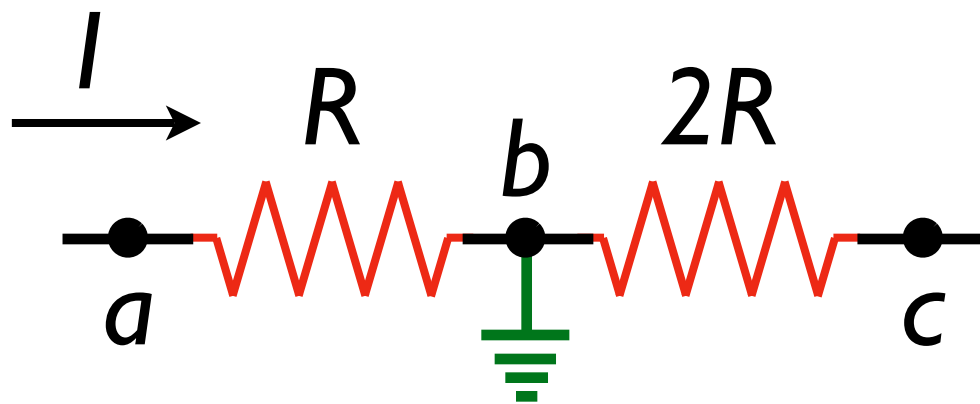


(a)

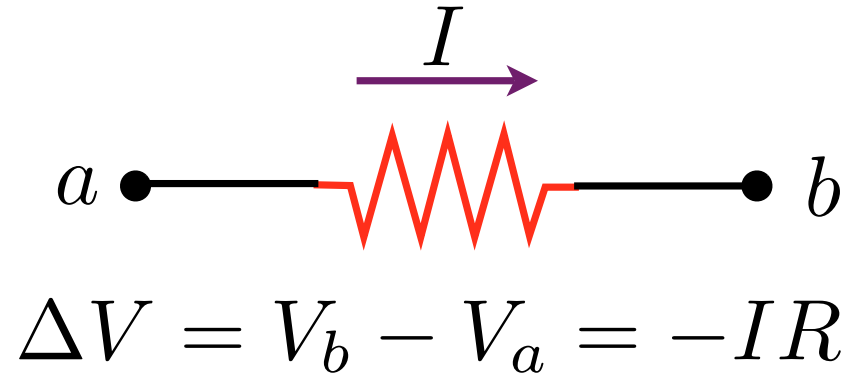

(b)

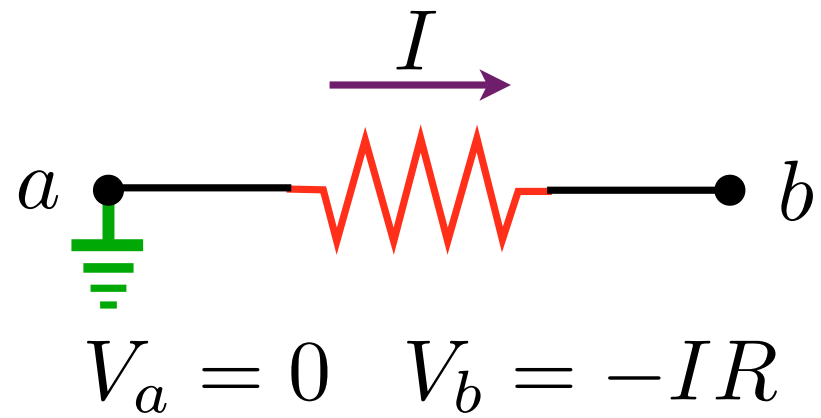


(c)

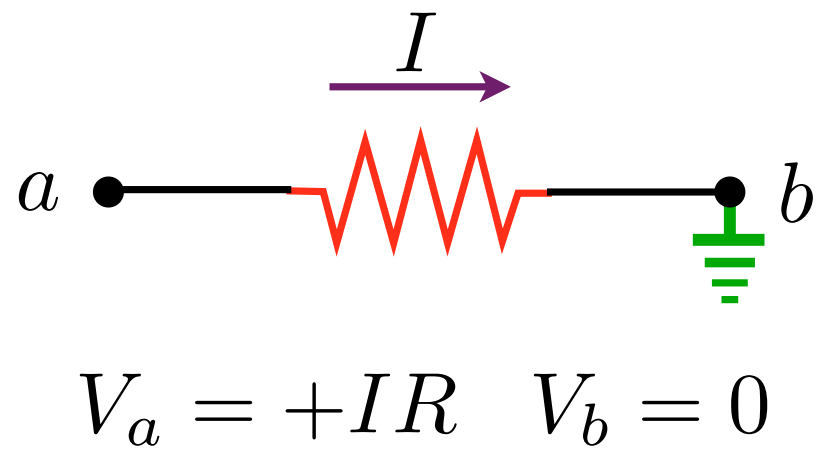

real V source = ideal V source + R




=

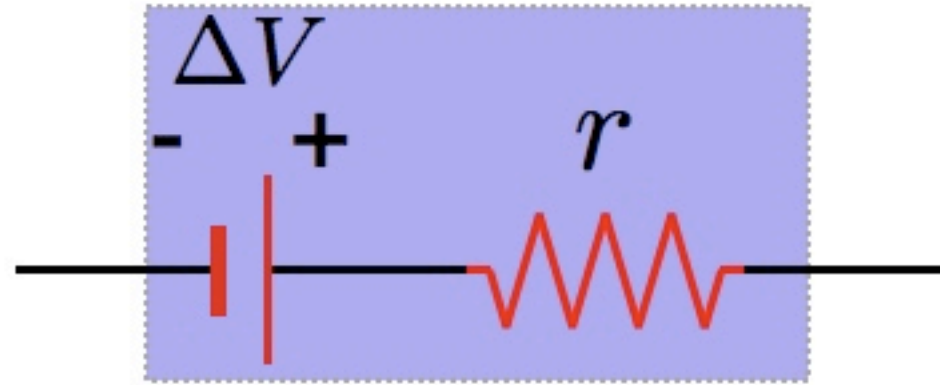

actual circuit has a parasitic r




b)

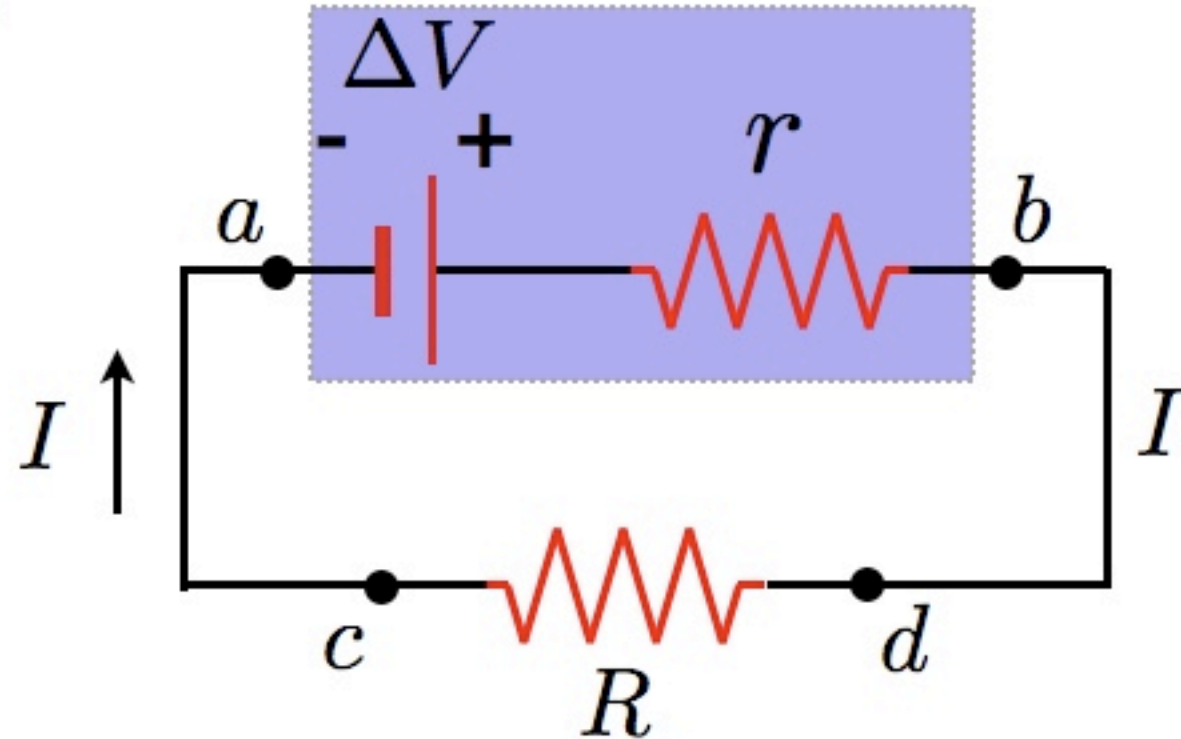


R in series with output
("steals" V)

real current sources

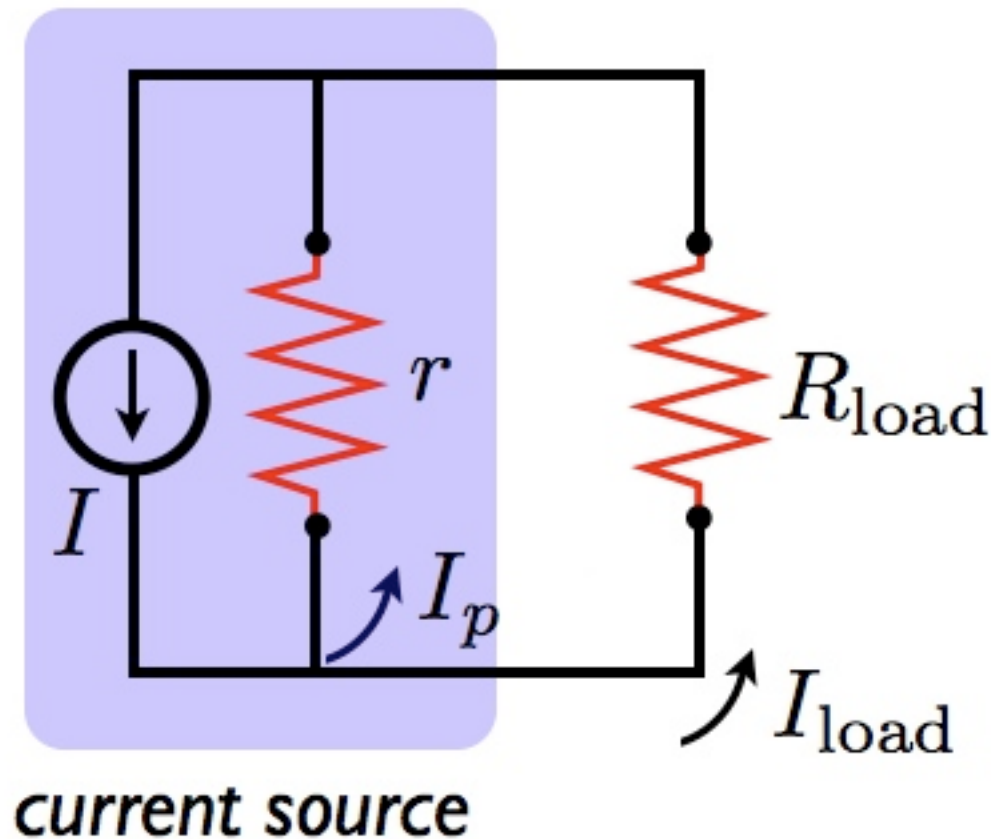

R in parallel with output
("steals" I)

series resistors: conservation of energy

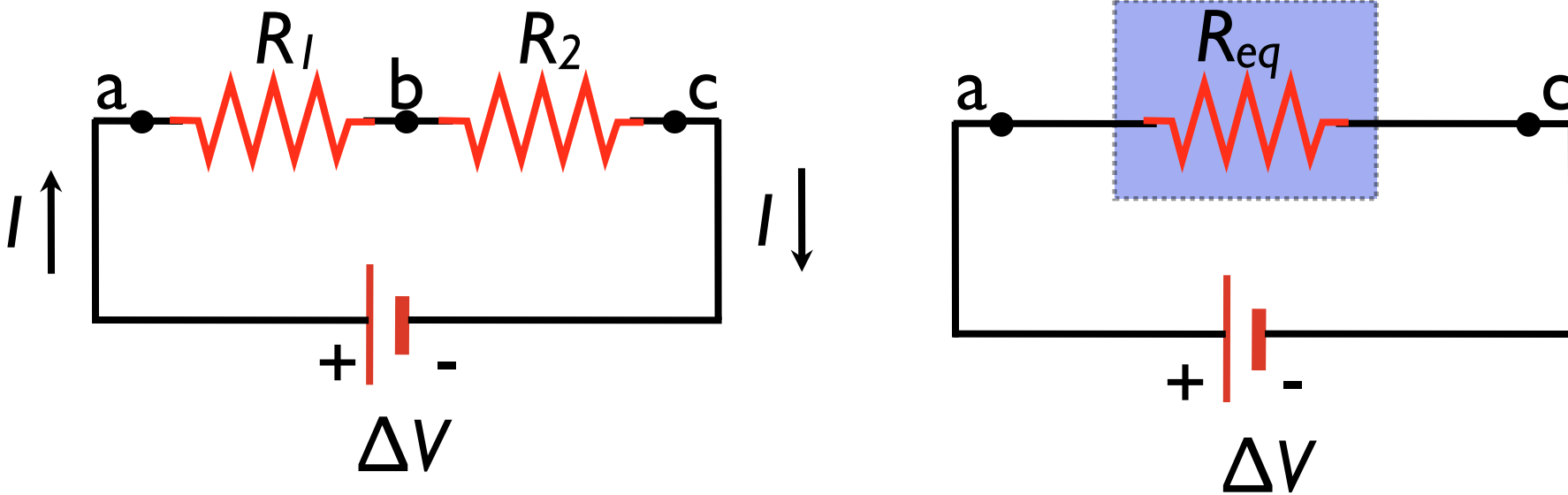

Two Resistors in Series:


$$R_{eq} = R_1 + R_2$$

Three or More Resistors in Series:


$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

The current through resistors in series is the same.

voltage divider

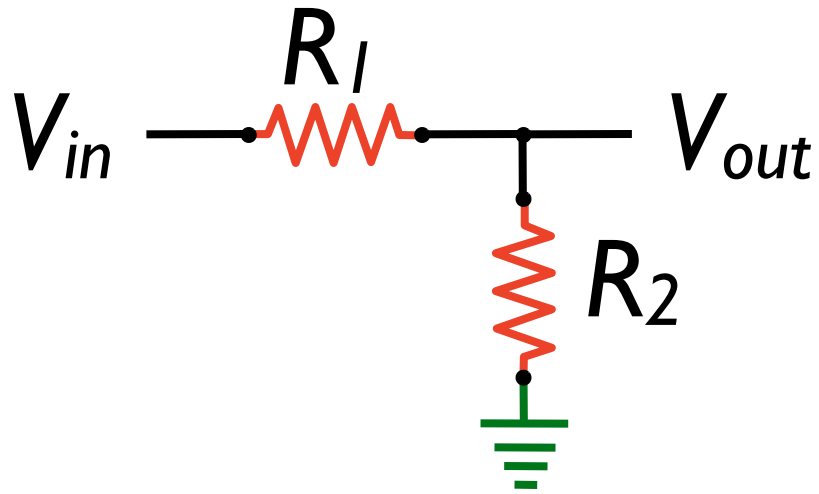

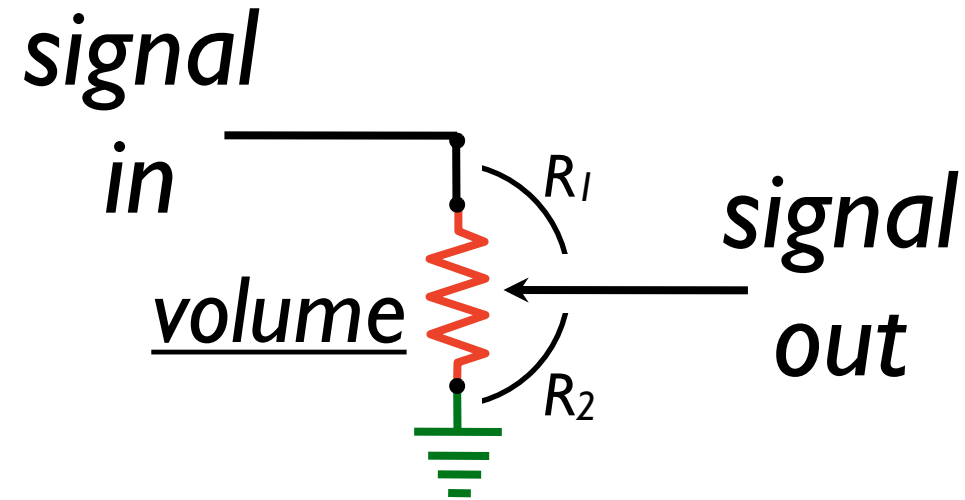
$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$




parallel resistors: conservation of charge

$$\Delta V_1 = \Delta V_2 = \Delta V$$

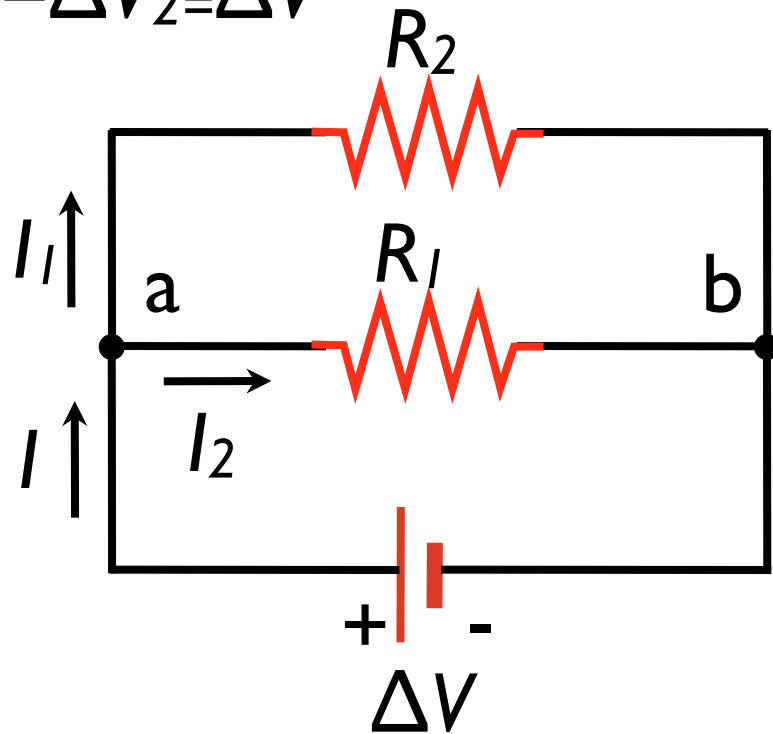
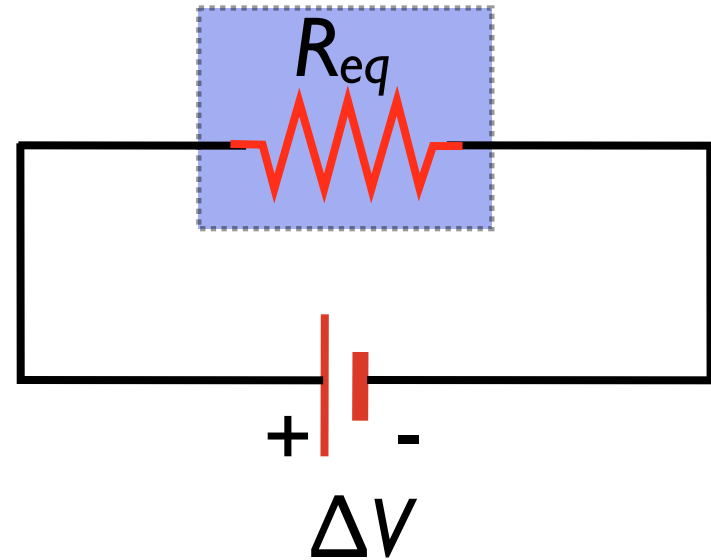
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Two Resistors in Parallel:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Three or More Resistors in Parallel:





$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

current divider


rank the currents

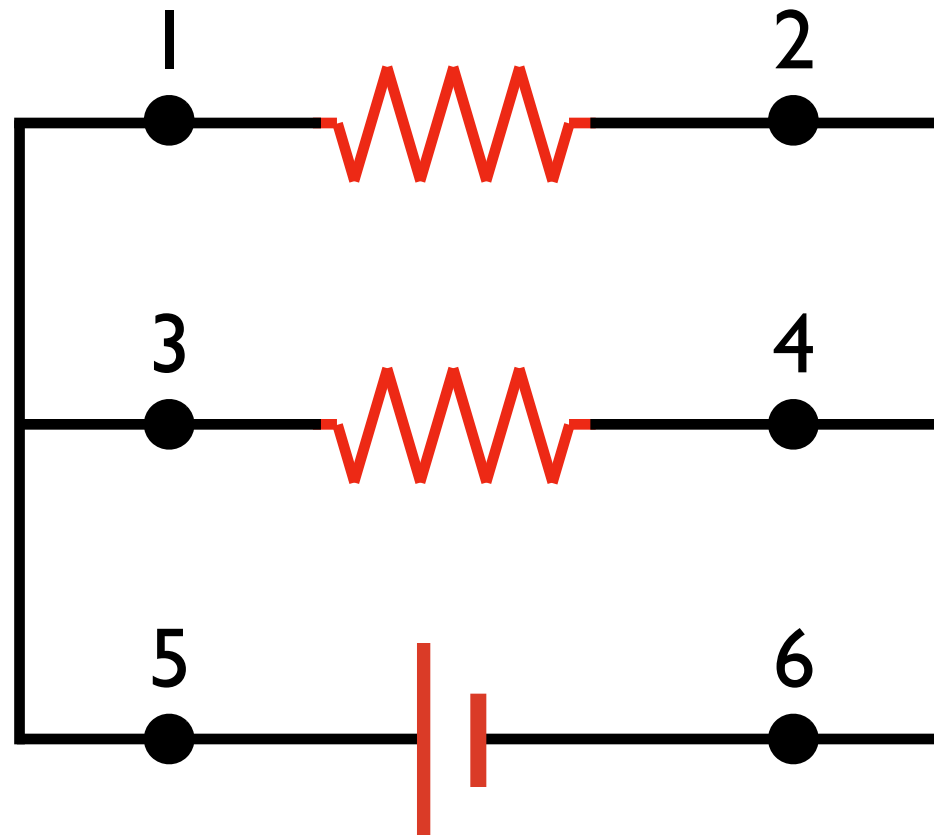


more complex arrangements

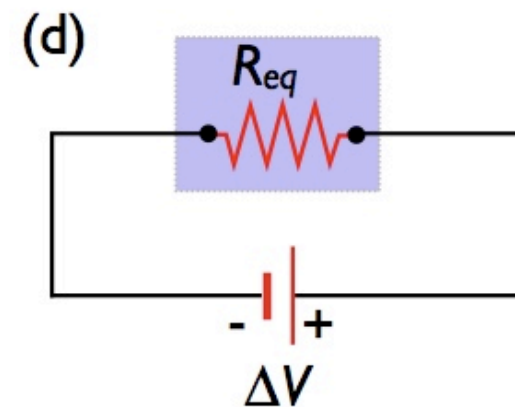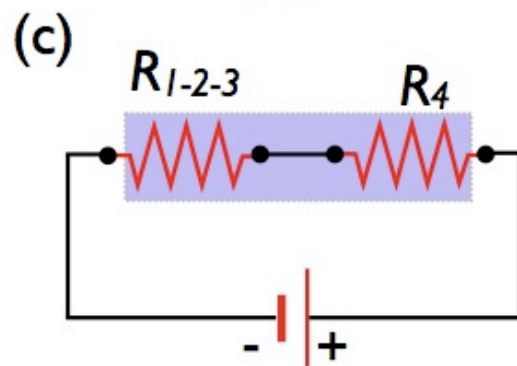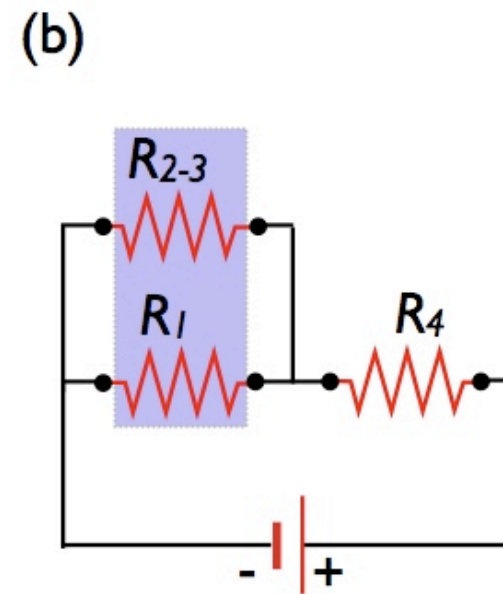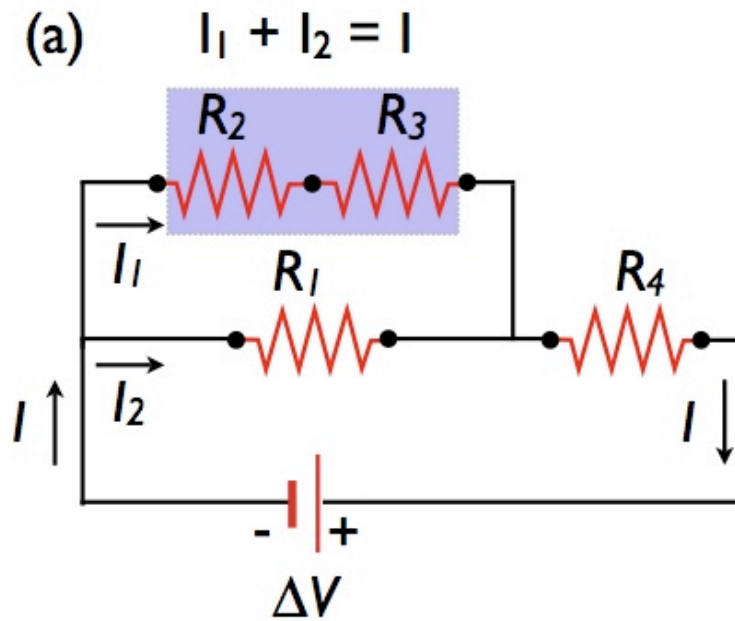

measuring voltage

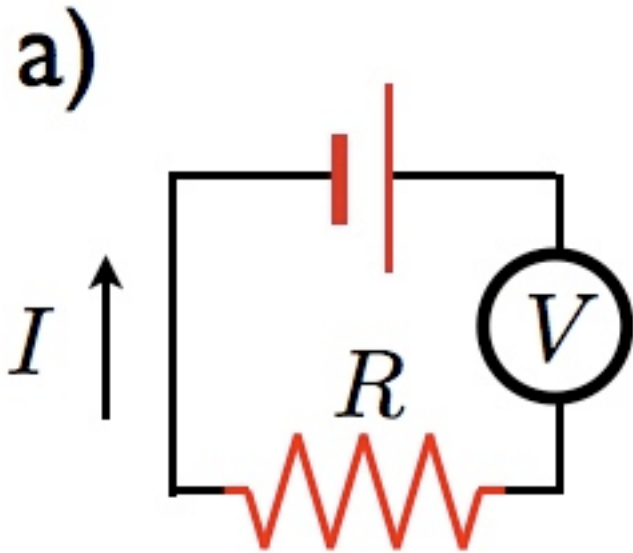


! INCORRECT !

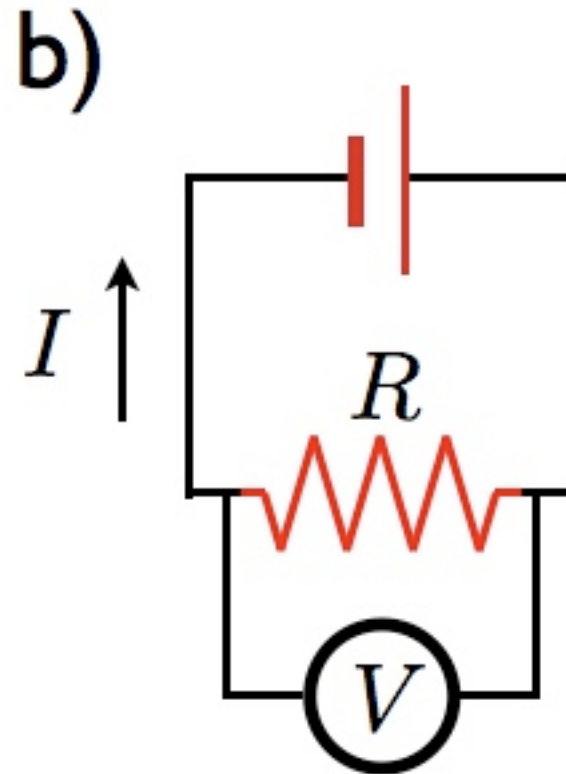


CORRECT

real voltmeters

(a)

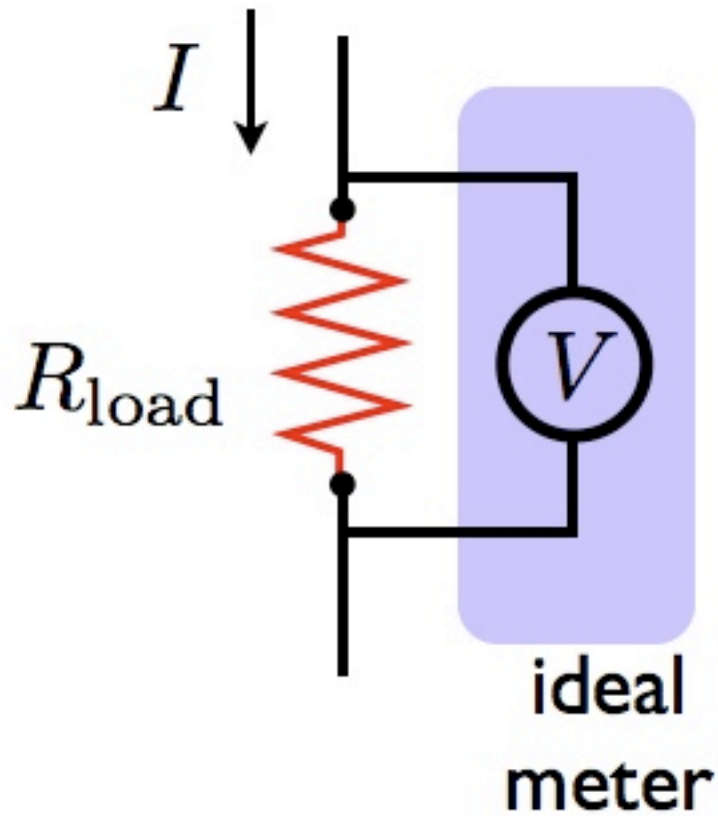


(b)

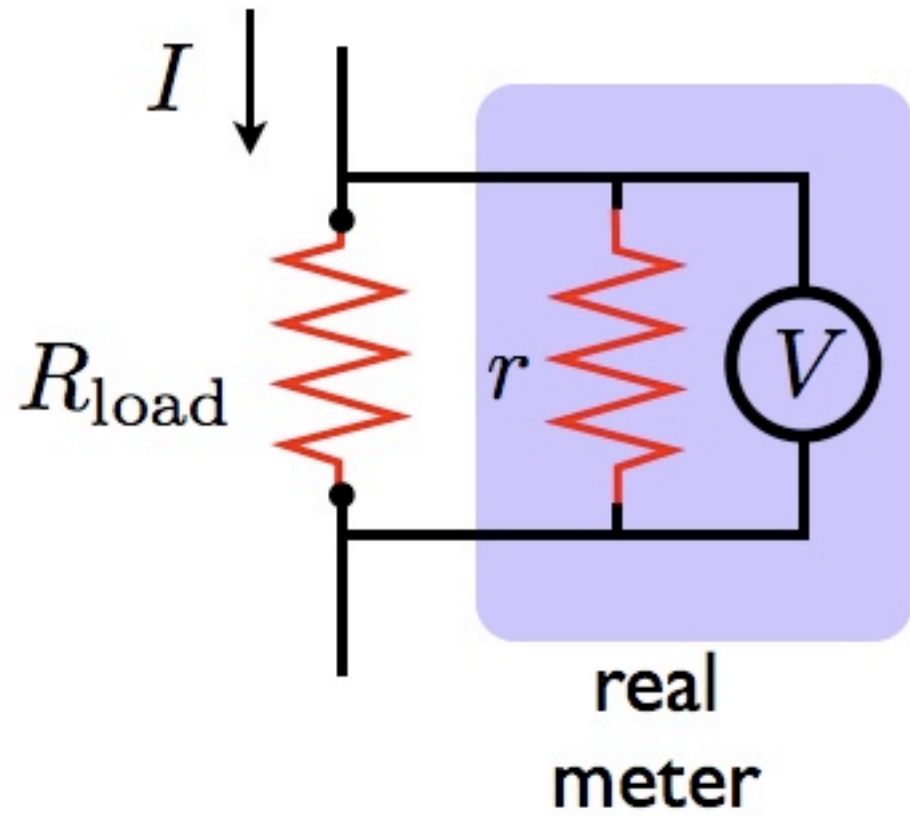


measuring current

a)

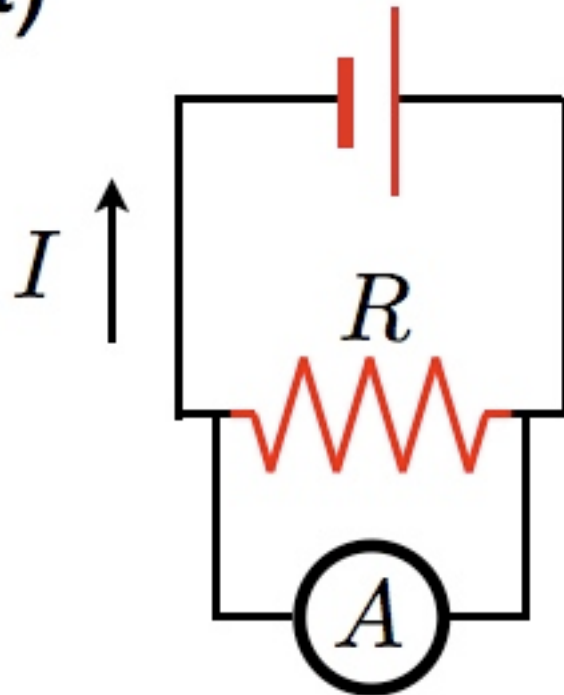


! INCORRECT !

b)

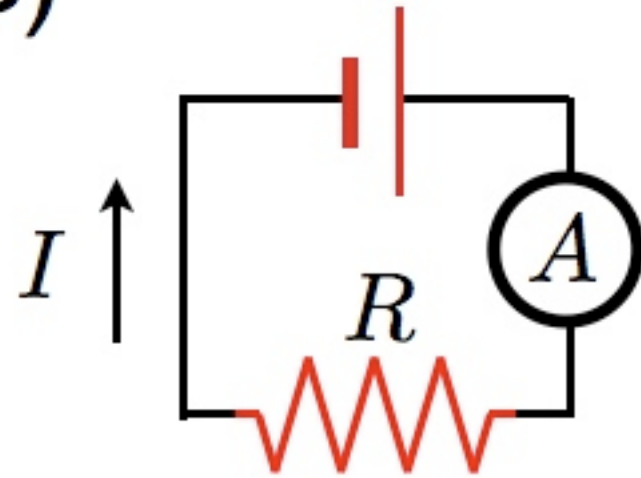

CORRECT

a simple ammeter

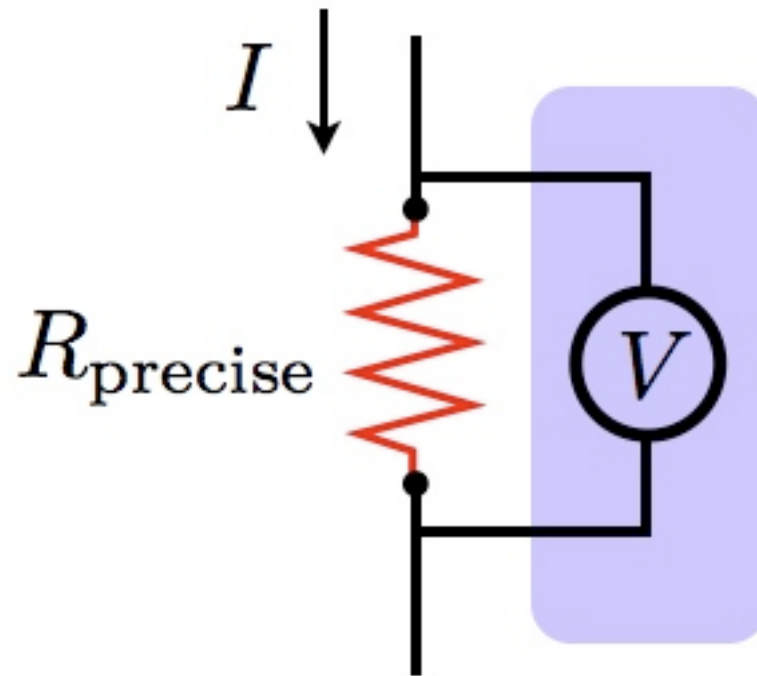


dc Circuits, part II

same thing, just more of it

Thévenin equivalents

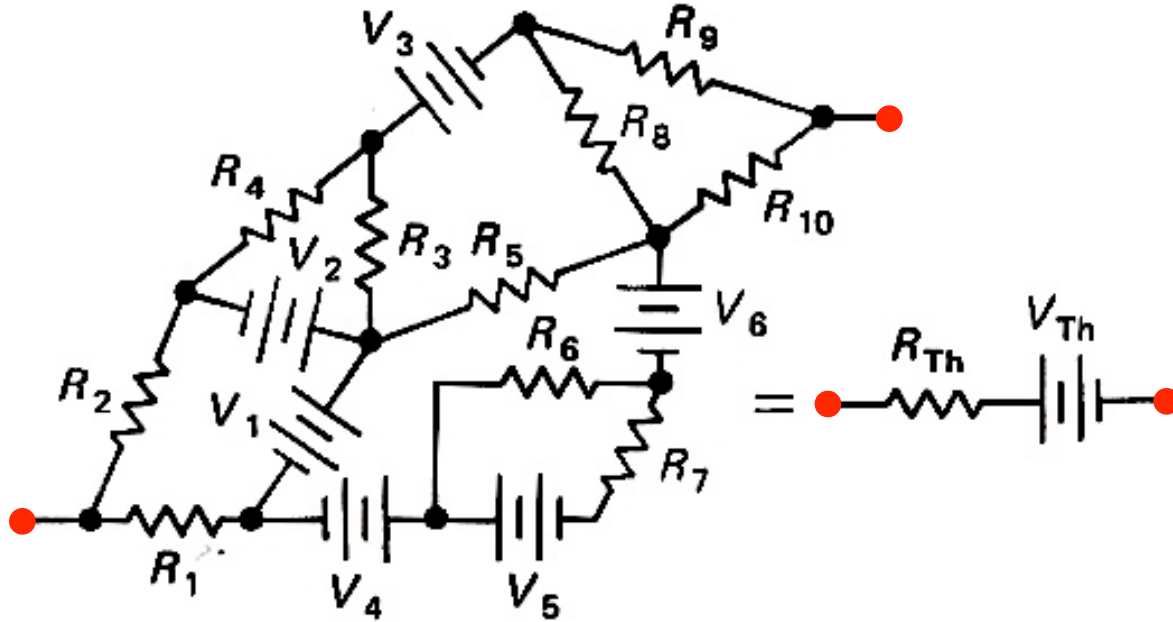This image: Horowitz & Hill, *The art of electronics*



$$V_{th} = V \text{ (open circuit)}$$


$$R_{th} = \frac{V \text{ (open circuit)}}{I \text{ (closed circuit)}}$$

any combination of R's and V's
is equivalent to a SINGLE R and V

disconnect from red dots = open circuit voltage
short red dots, current *there* is closed-circuit current.

(Norton equivalent: a single I source in parallel with R)

series resistors: conservation of energy

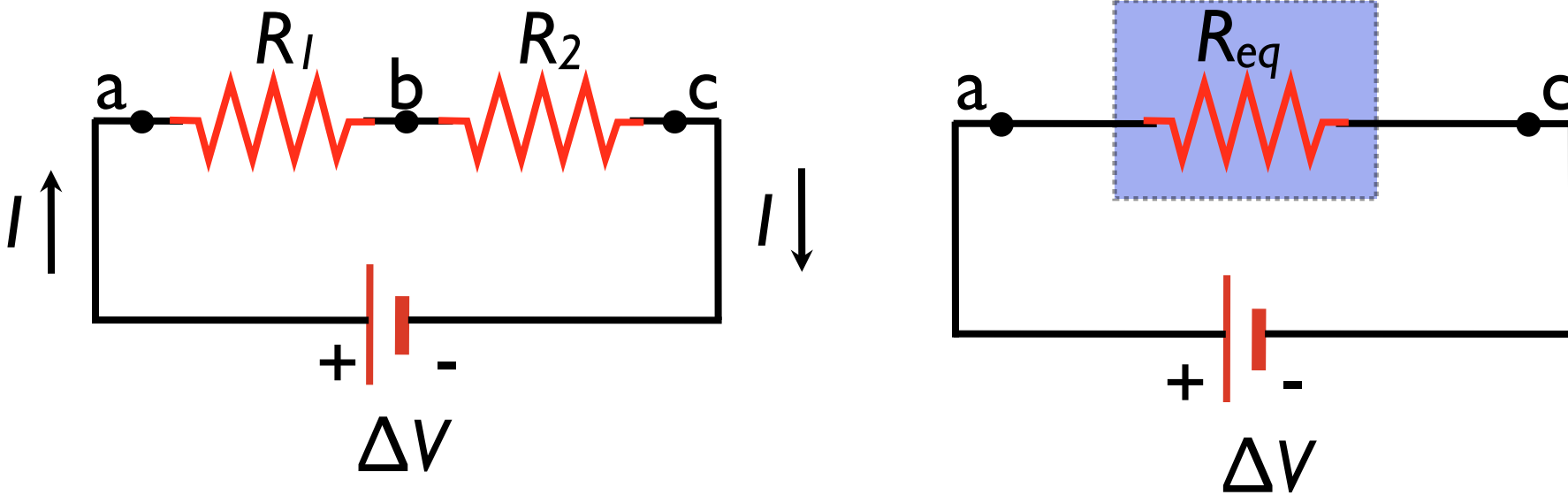

Two Resistors in Series:

$$R_{eq} = R_1 + R_2$$

Three or More Resistors in Series:


$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

The current through resistors in series is the same.


source voltage =
sum of voltages
on resistors

parallel resistors: conservation of charge

$$\Delta V_1 = \Delta V_2 = \Delta V$$

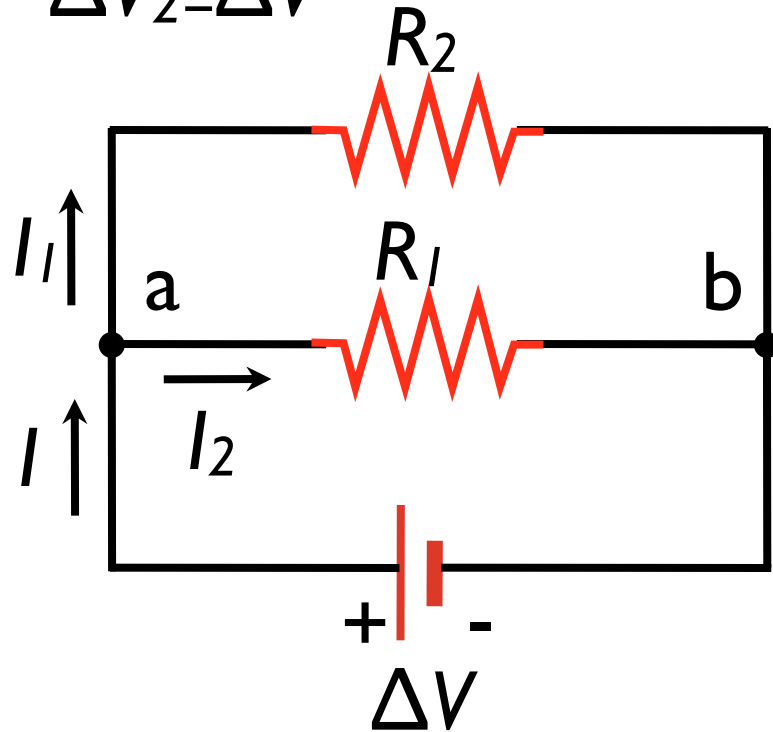
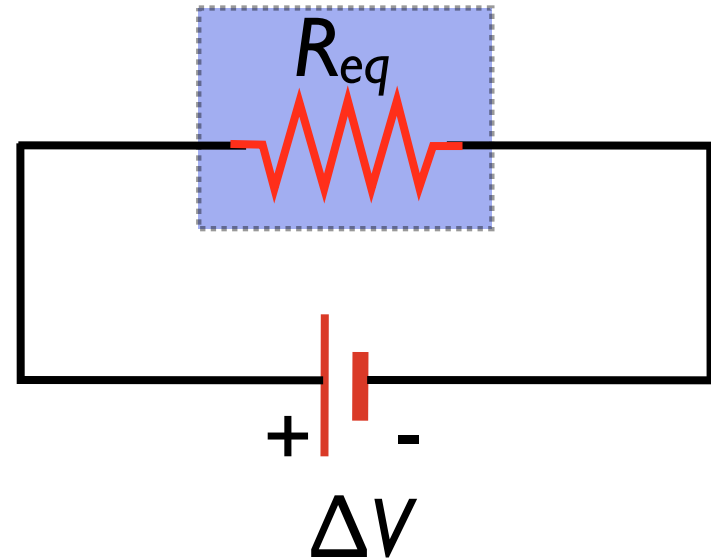
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Two Resistors in Parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Three or More Resistors in Parallel:


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

source current =
sum of currents
in resistors



current divider

so what?

real sources =
ideal sources + R

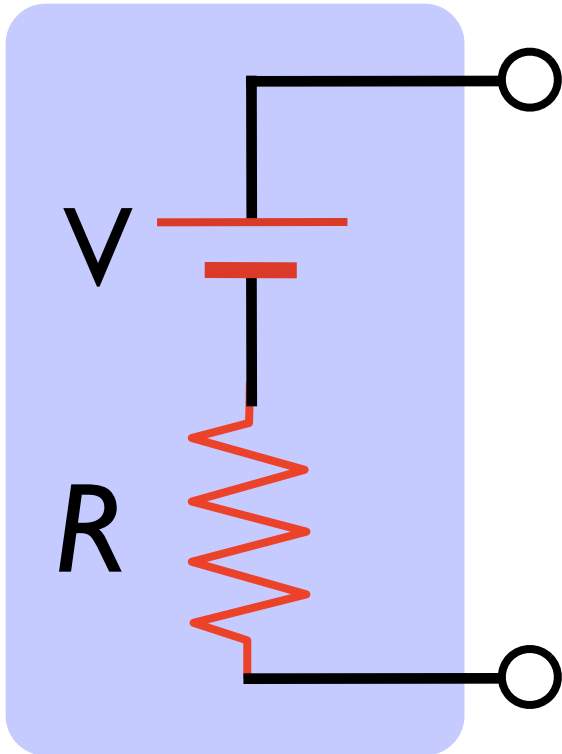


real meter =
ideal meter with R

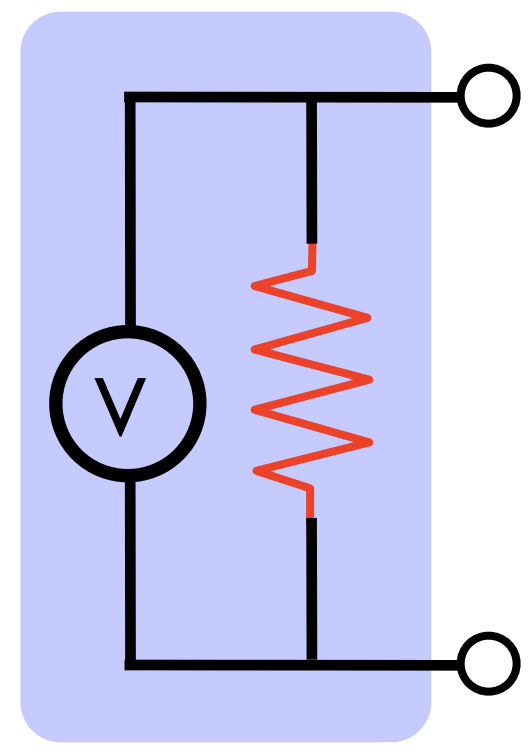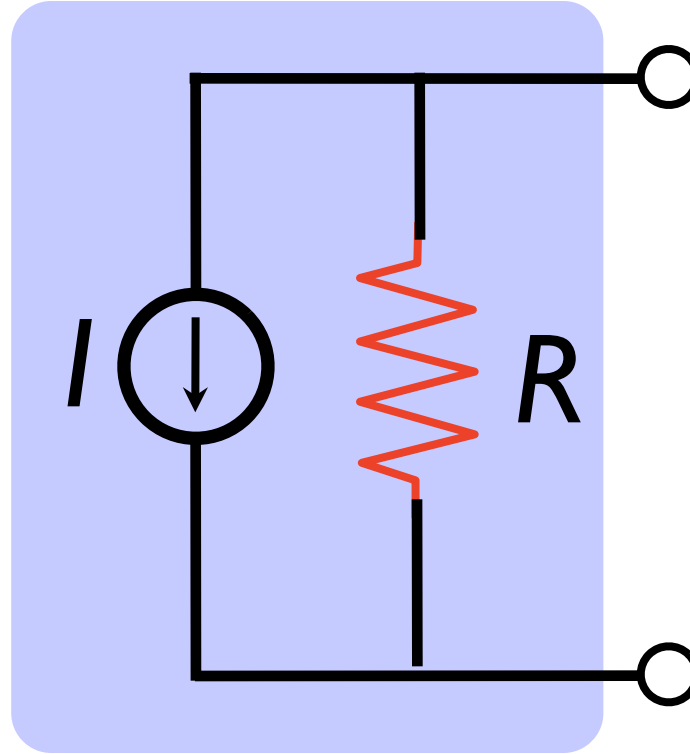

what about
ammeter?

V source loading

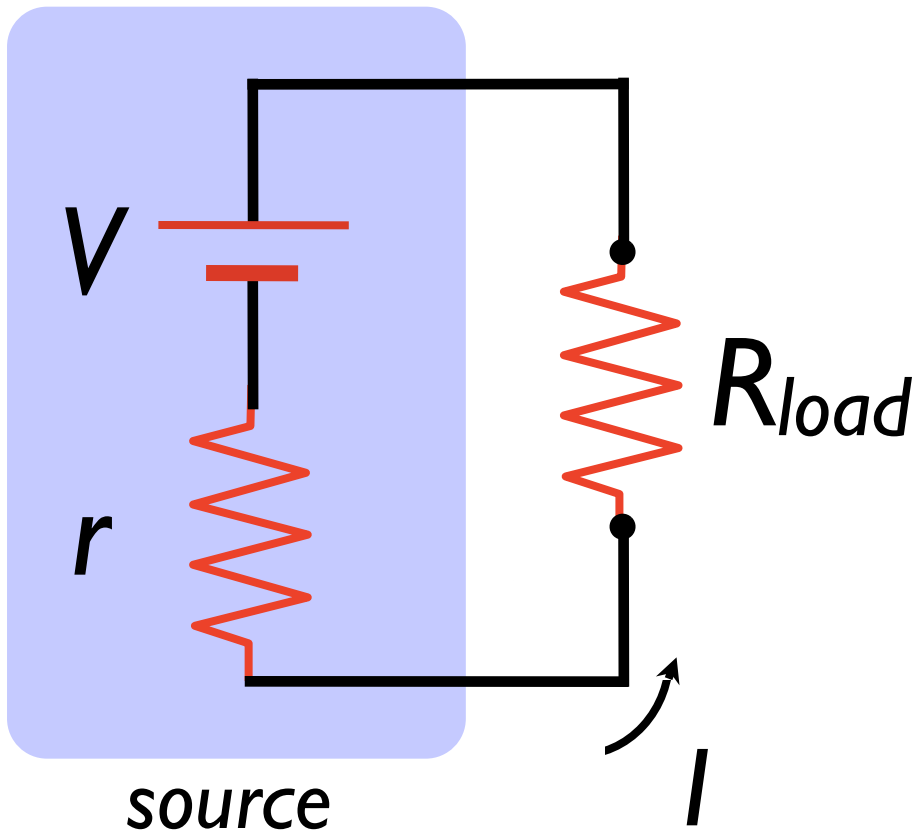

$$\Delta V_{load} = V - Ir$$

for $r \ll R_{load}$,


$$\Delta V_{load} \approx V$$

V source wants R **high**

*extra series
resistance*

one solution:
large resistor in parallel with load

I source loading

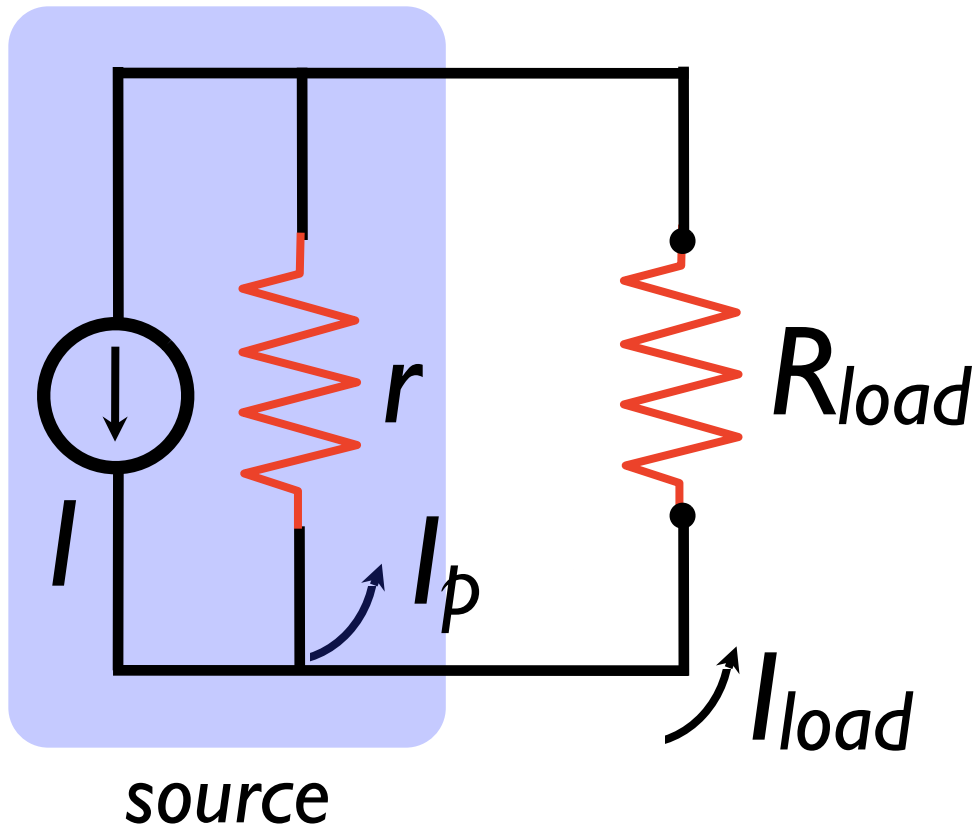

$$I_{load} = I \frac{r}{r+R}$$



for $R_{load} \ll r$,

$$I_{load} \approx I$$

extra parallel
resistance

I source wants R **low**
sourcing currents at high R_{load} is hard

measuring the meter

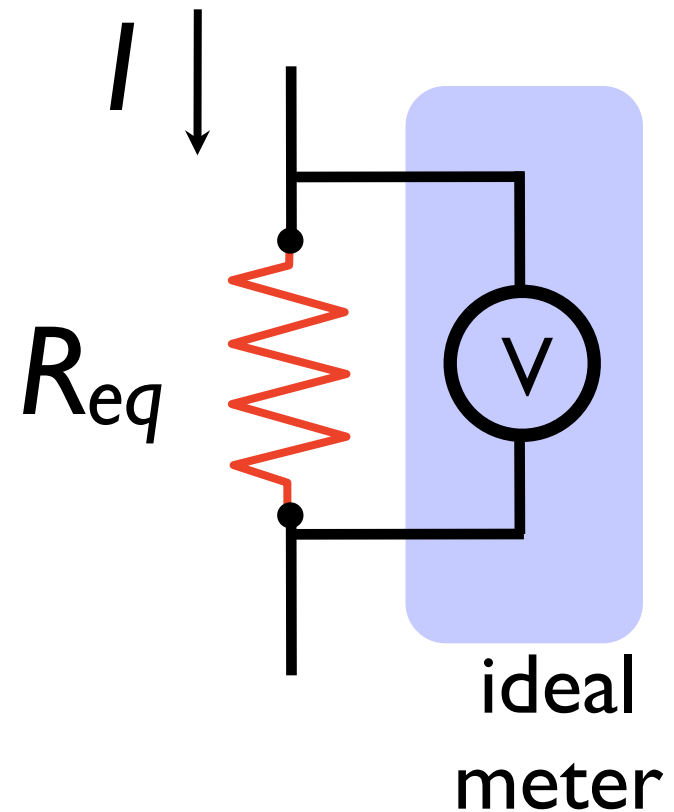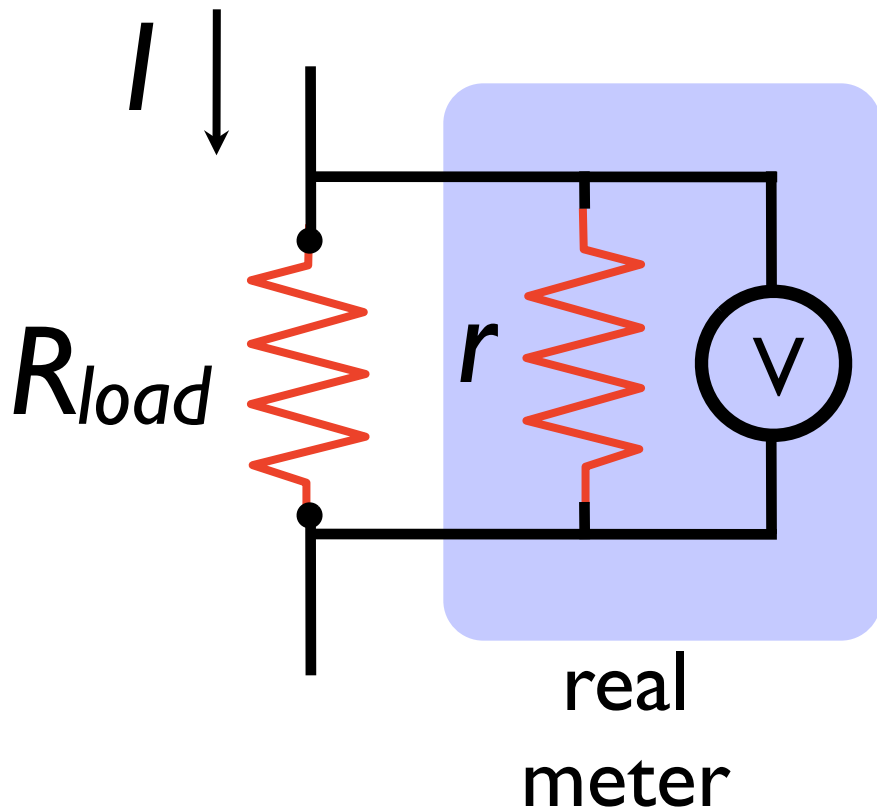

$$\Delta V_{load} = IR_{eq} = \frac{R}{1+R/r} I$$

$$R_{load} \ll r, \Delta V_{load} \approx IR$$

summary

voltmeter wants R **low!**

can use a buffer/follower ... later

I source wants R **low**

transformer pre-amp

consider sourcing V

V source wants R **high**


large series + parallel resistors

present large R

Sourcing current


This is what a hand meter does.

Why is it no good?

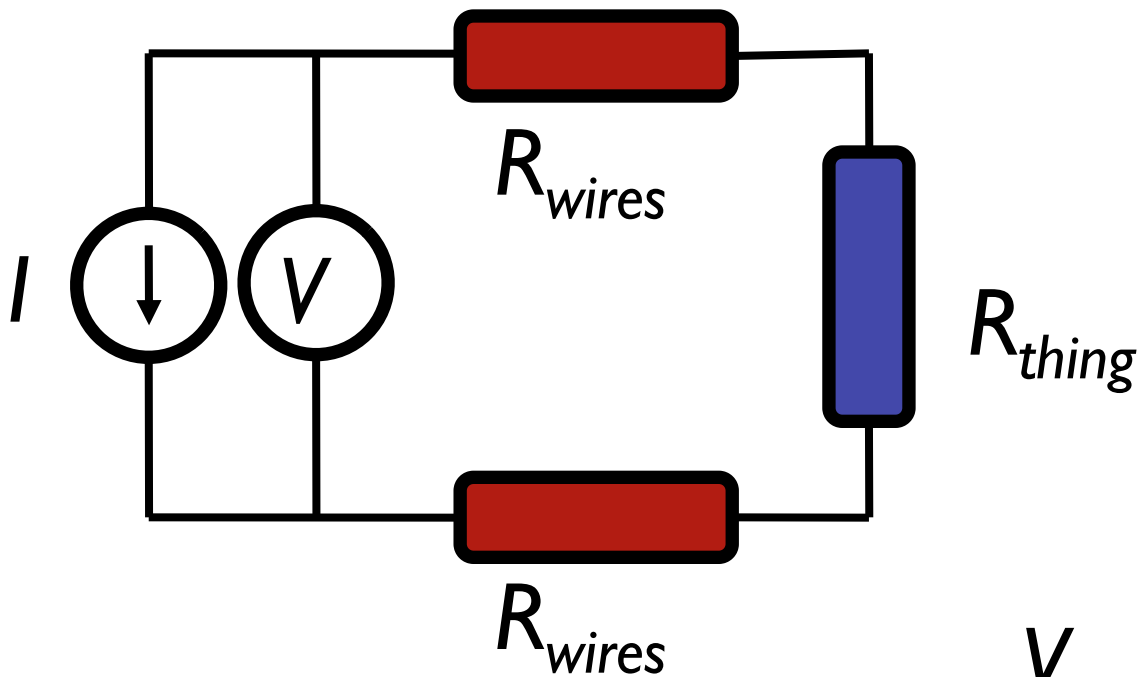


$$V_{meter} = I(R_{thing} + 2R_{wires})$$

Sourcing current, properly

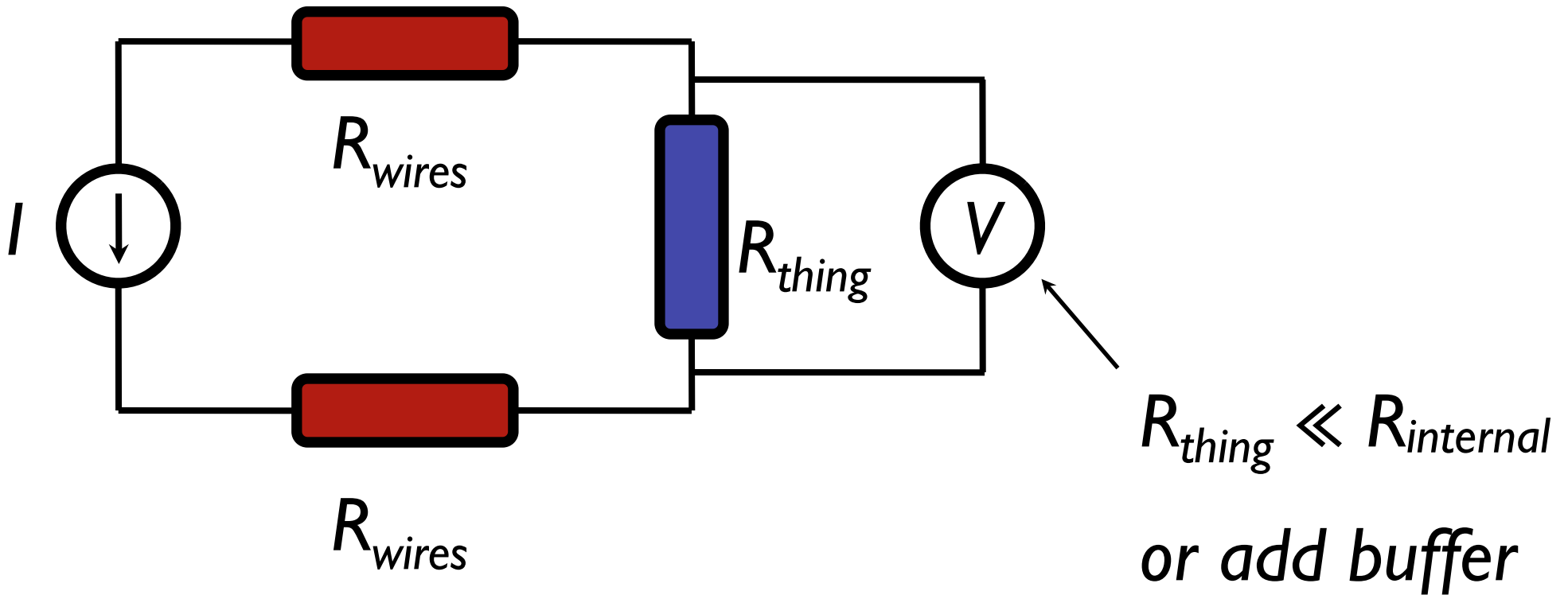


No problem.
You just need four wires.

Sourcing voltage

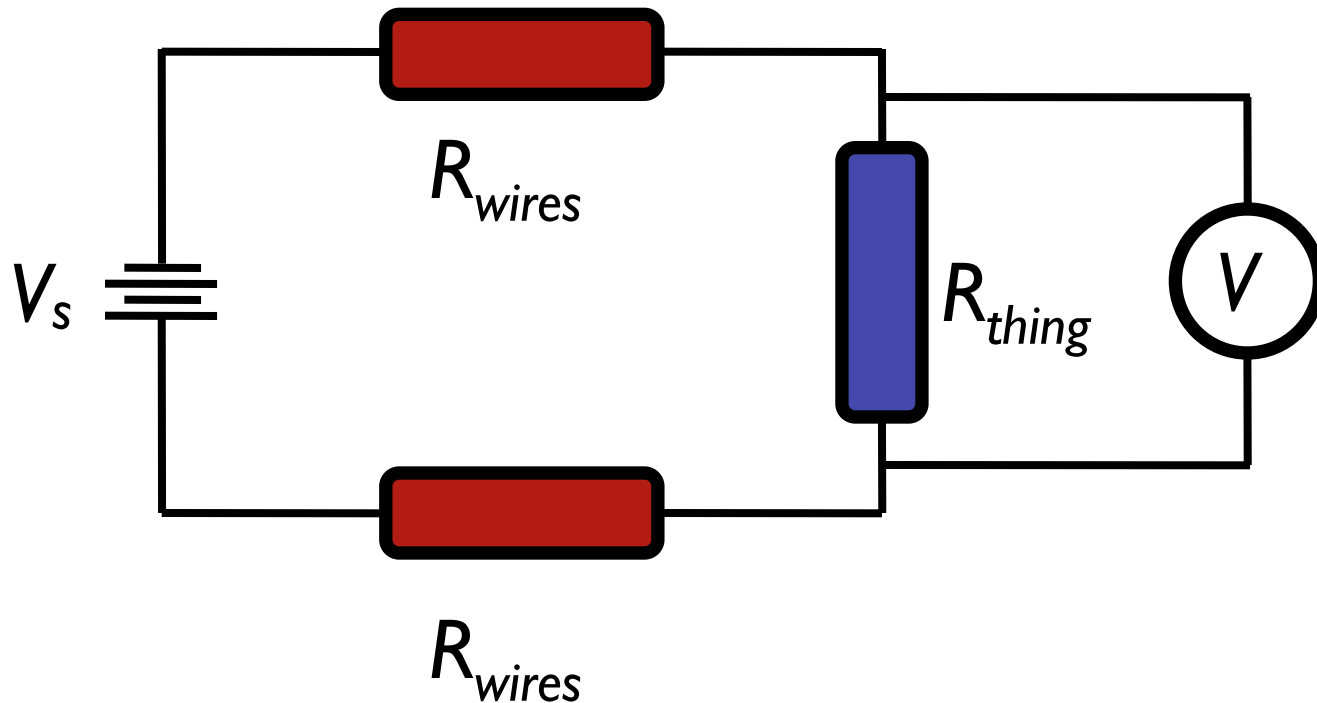


Still have to measure voltage on device
the wires still use up some of V
What about current?

Sourcing voltage better

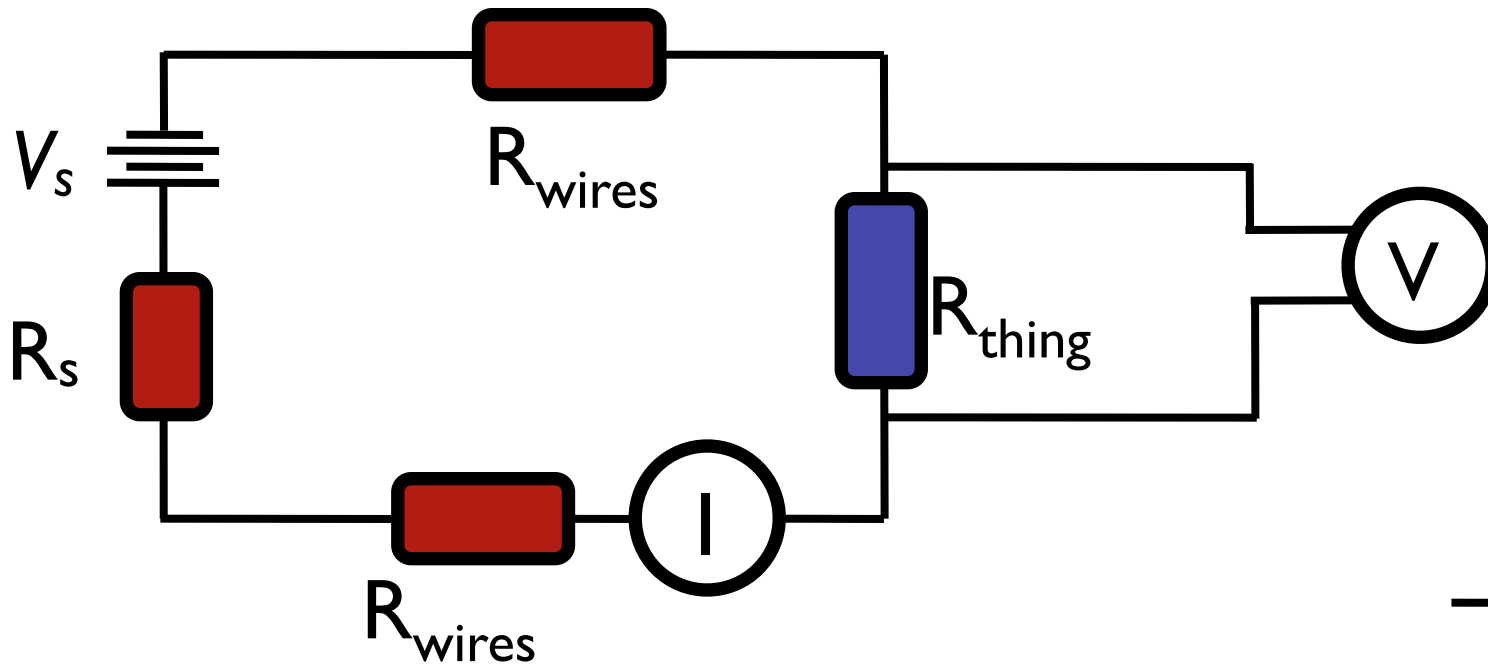

$$R = \Delta V / I$$

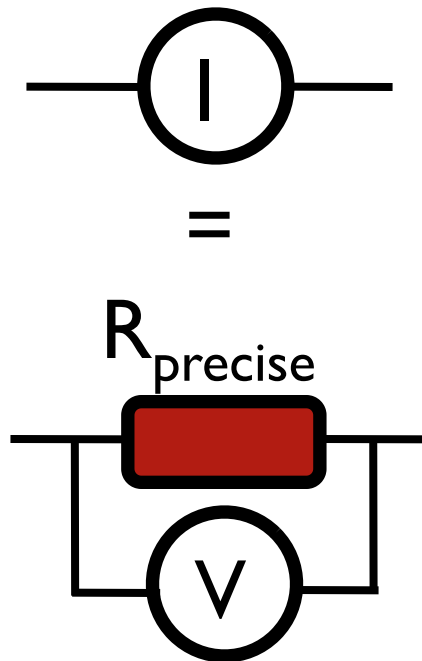Note we need 4 wires again
current meter - not hard
still problems?




source/meter resistances

voltmeter wants R low
but V source wants R high

need buffer/amp on V meter
resistor in parallel with source

if V source is problem, R is too low
consider sourcing I

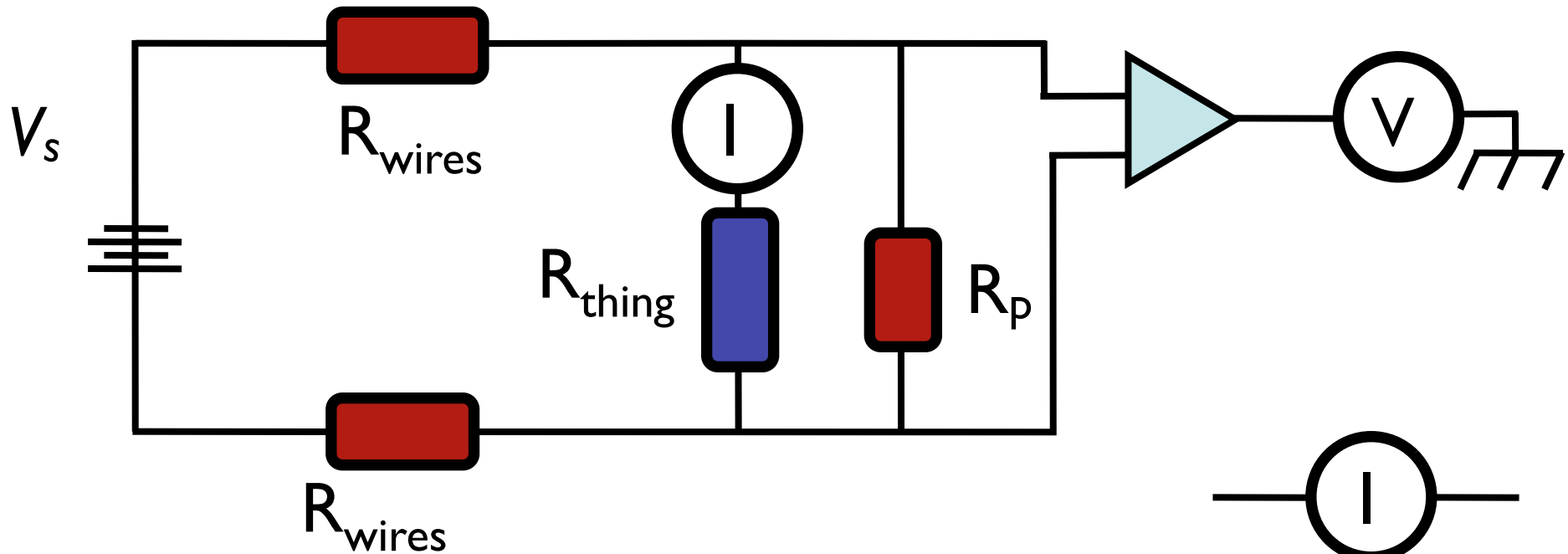what if I want to measure a **really** high R?




source voltage


R_p has same voltage as R_{thing}

R_s has same current

have done $> 10^{10}$ Ohm

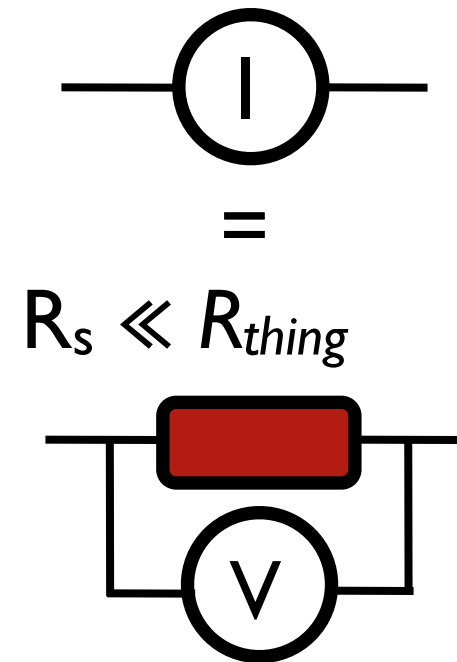


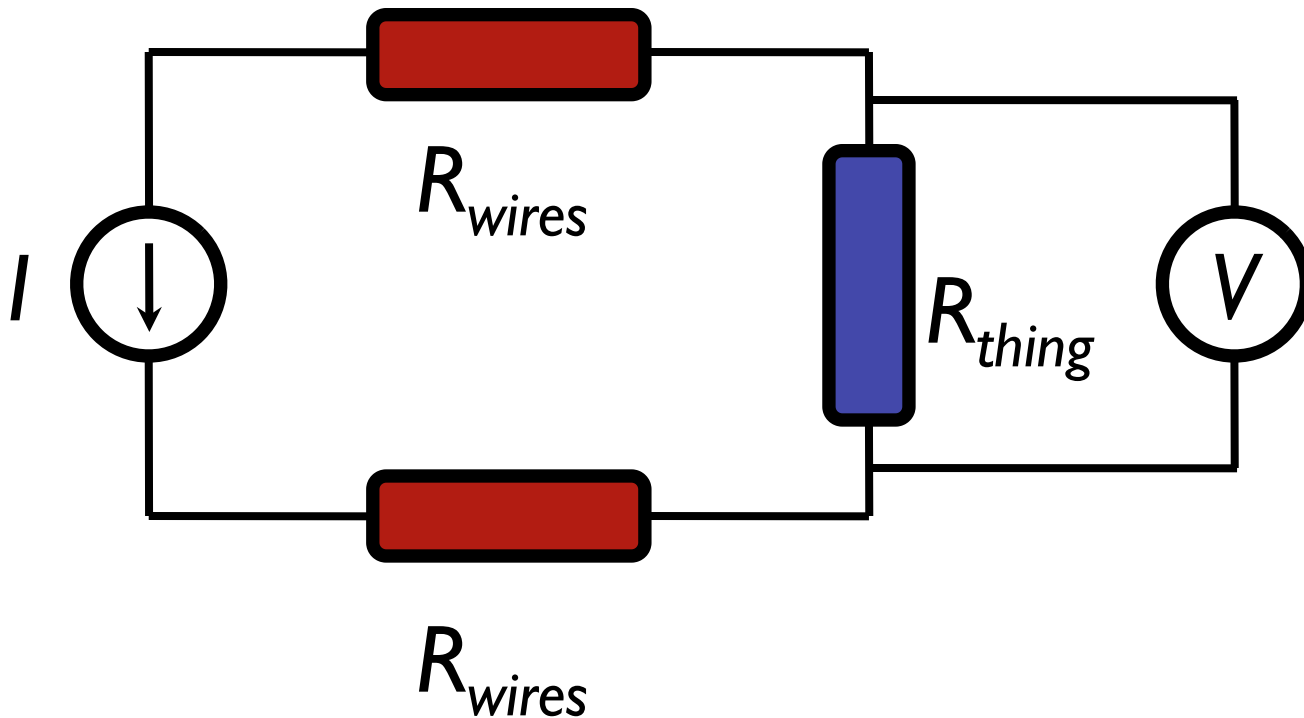
what if I want to measure a **really** low R?







this works just fine ...


so long as your V meter is good or you can tolerate large I
v. good amp / part of a bridge

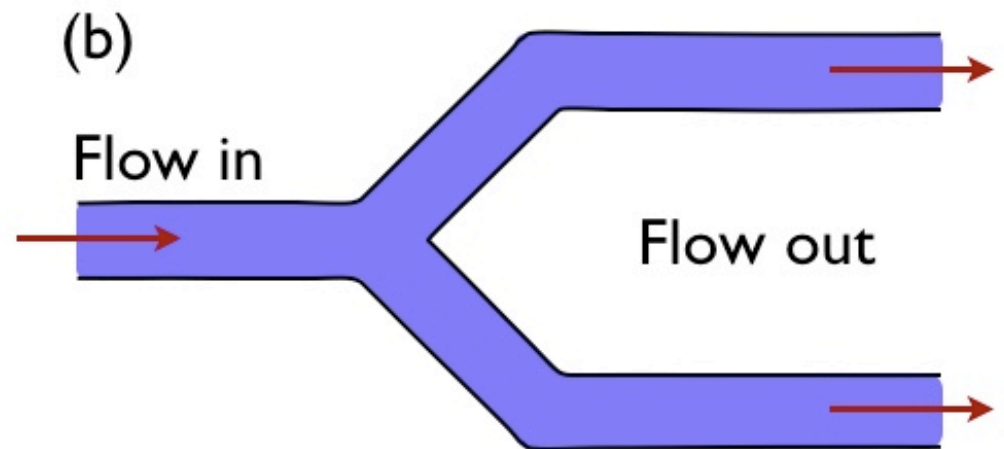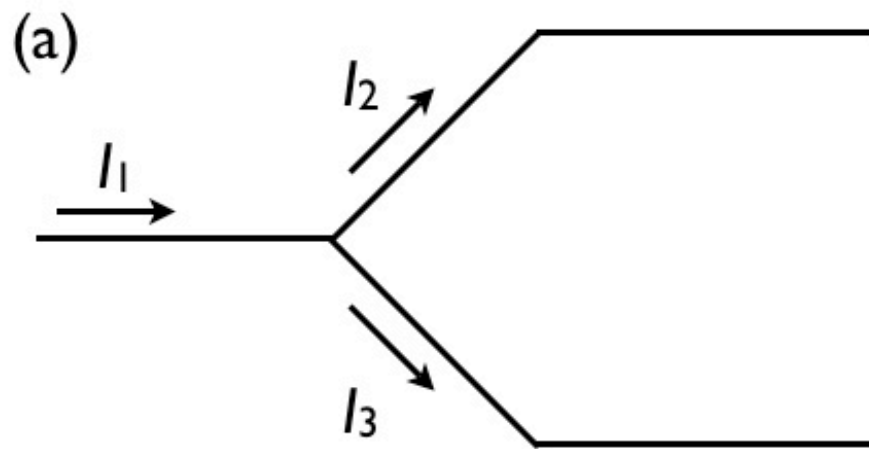Rules for analyzing more complicated circuits




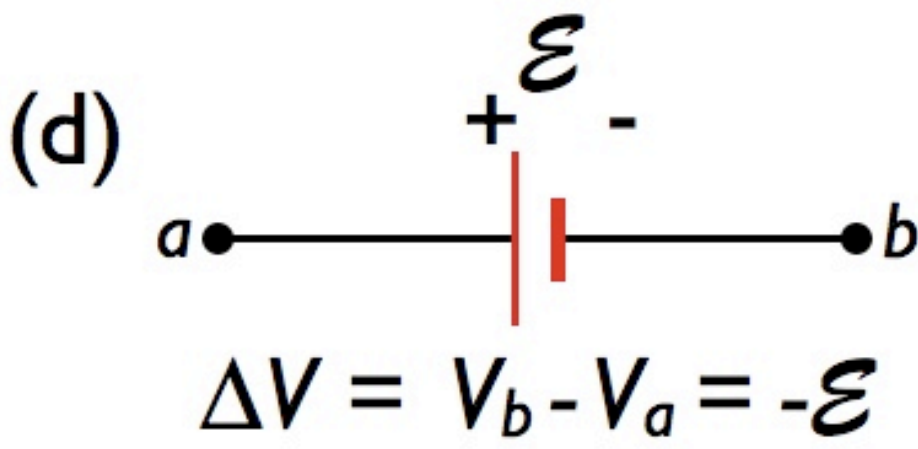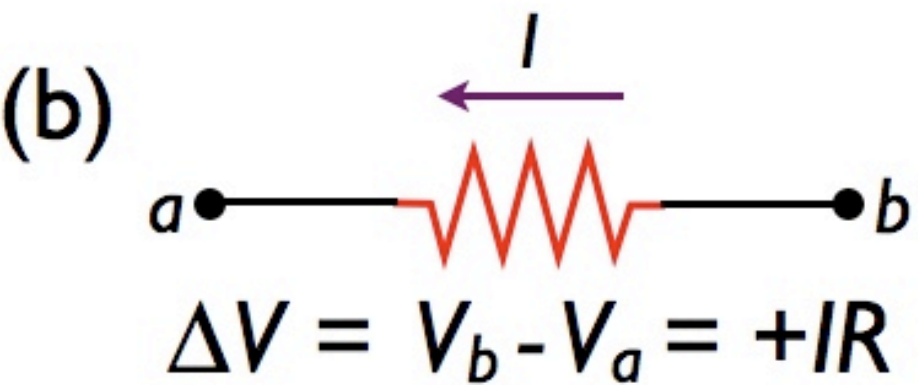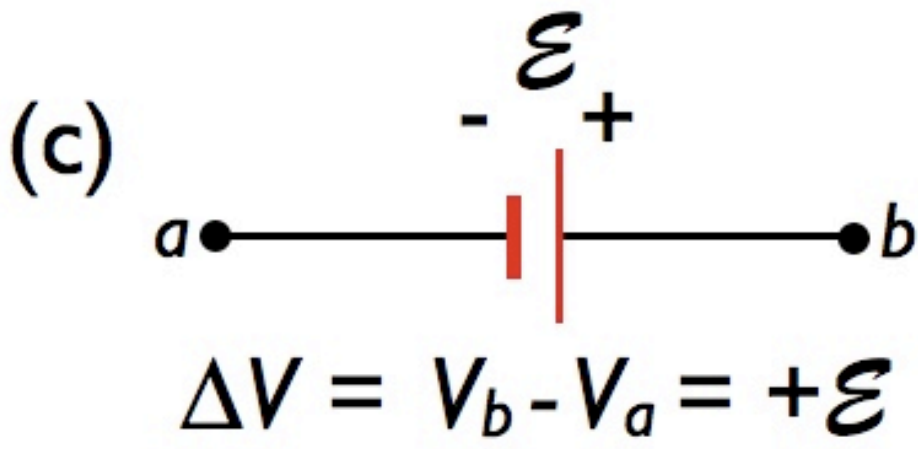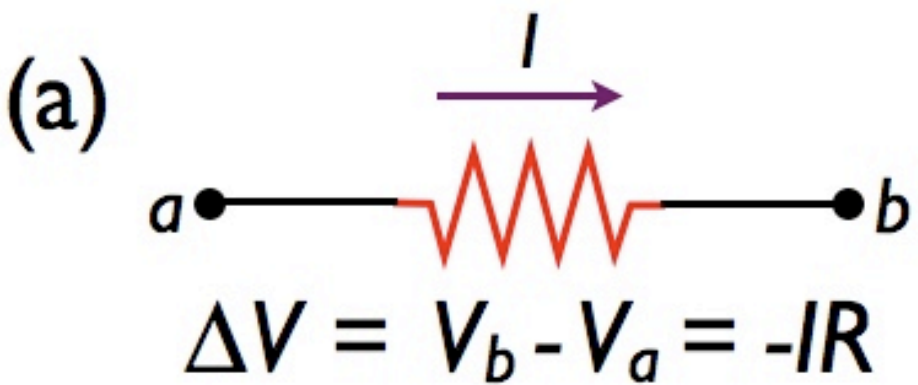

(a)

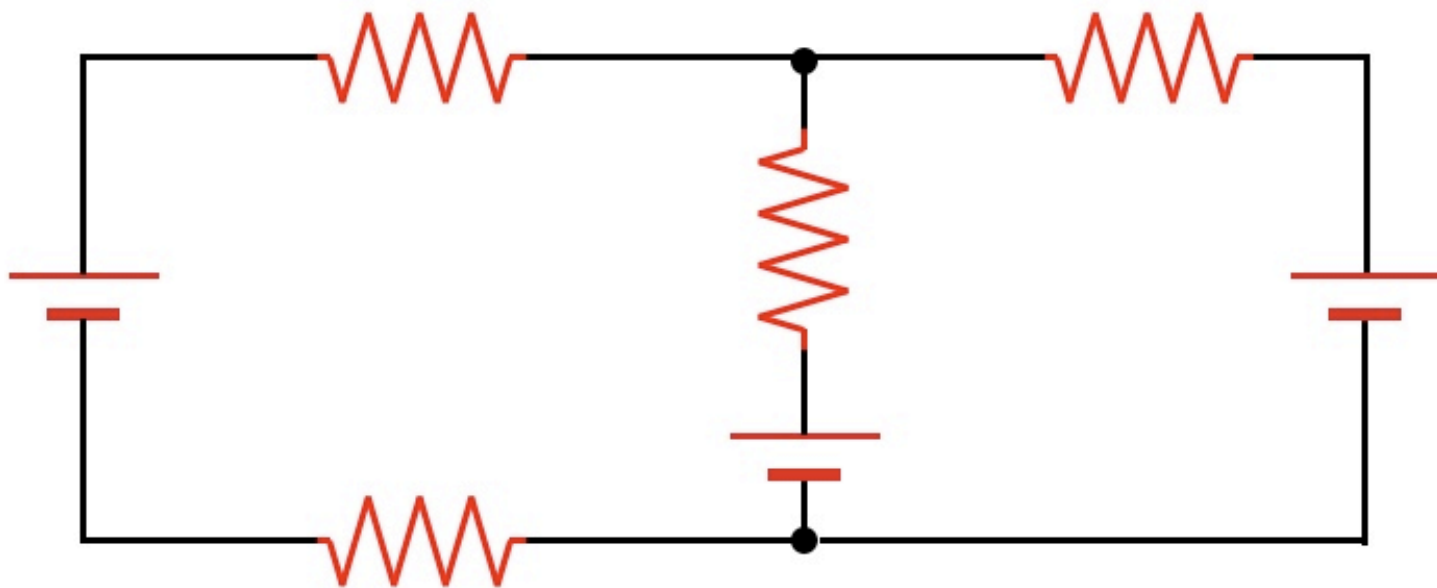

(b)

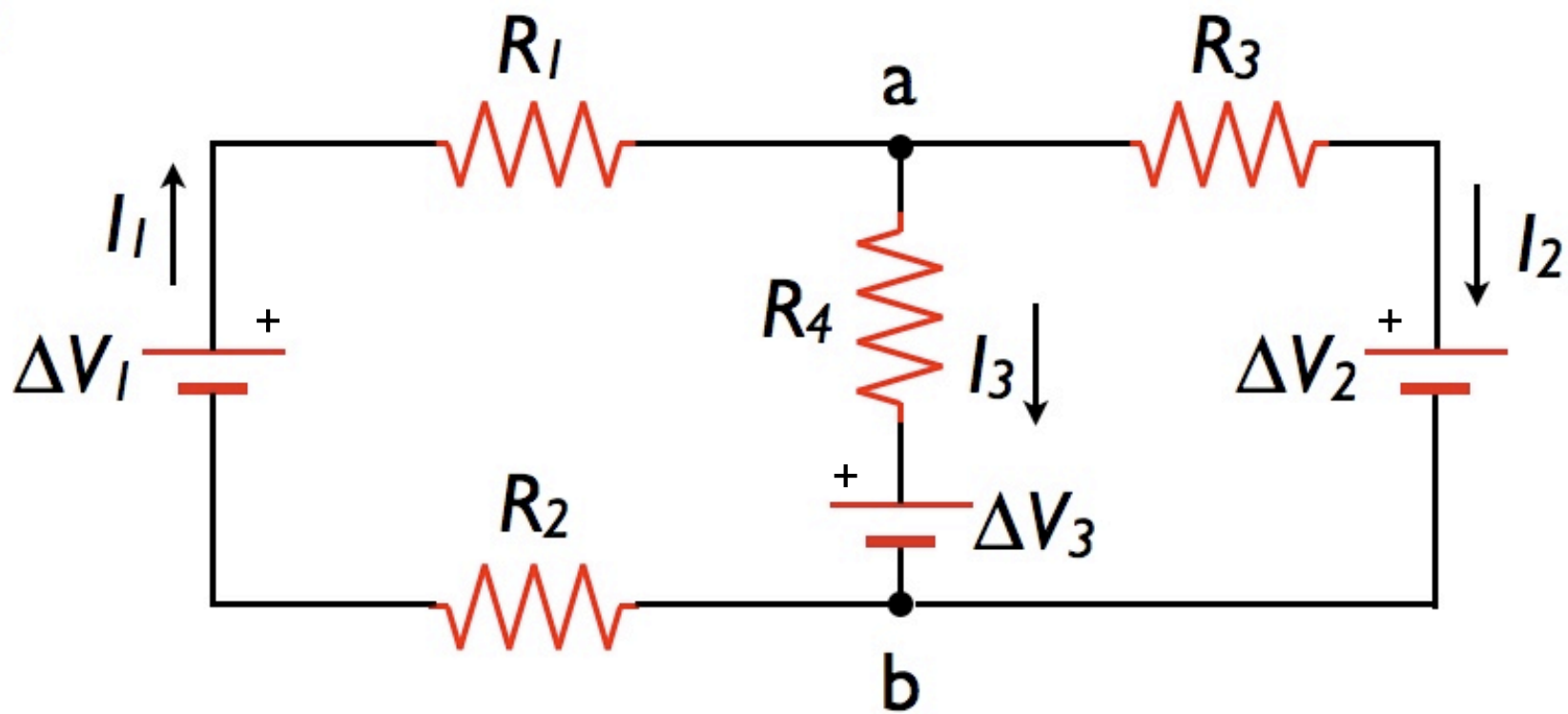


capacitors

Definition of Capacitance: the capacitance C is the ratio of the charge stored on one conductor (or the other) to the potential difference between the conductors:

$$C \equiv \frac{|Q|}{|\Delta V|} \quad (4.12)$$

frequency-dependent resistor
 I and V are 90° out of phase
can't dissipate power, ideally
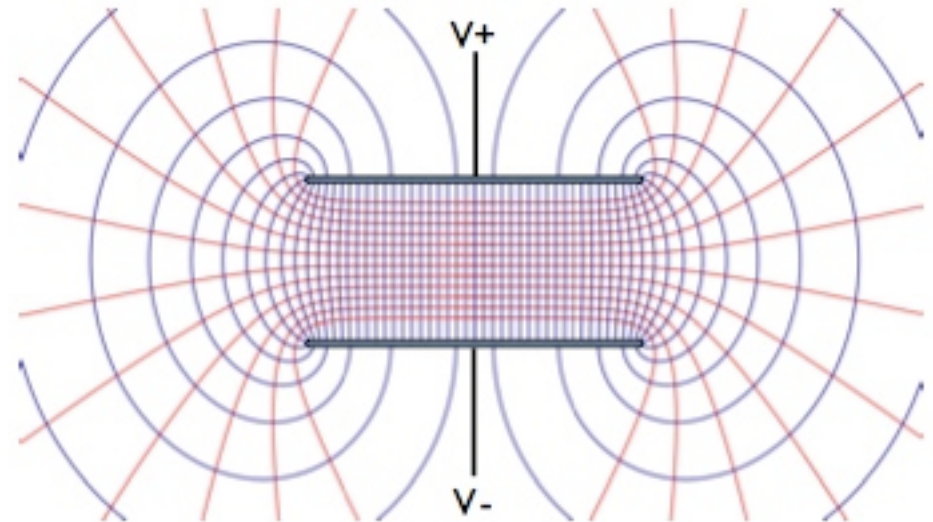
$$I = \frac{dQ}{dt} = \frac{d(CV)}{dt} \rightarrow C \frac{dV}{dt}$$



Capacitance of a parallel plate capacitor:

$$C = \epsilon_0 \frac{A}{d}$$

where d is the spacing between the plates, and A is the area of the plates.


combinations of capacitors

Two Capacitors in Parallel:

$$C_{\text{eq}} = C_1 + C_2$$

Three or More Capacitors in Parallel:
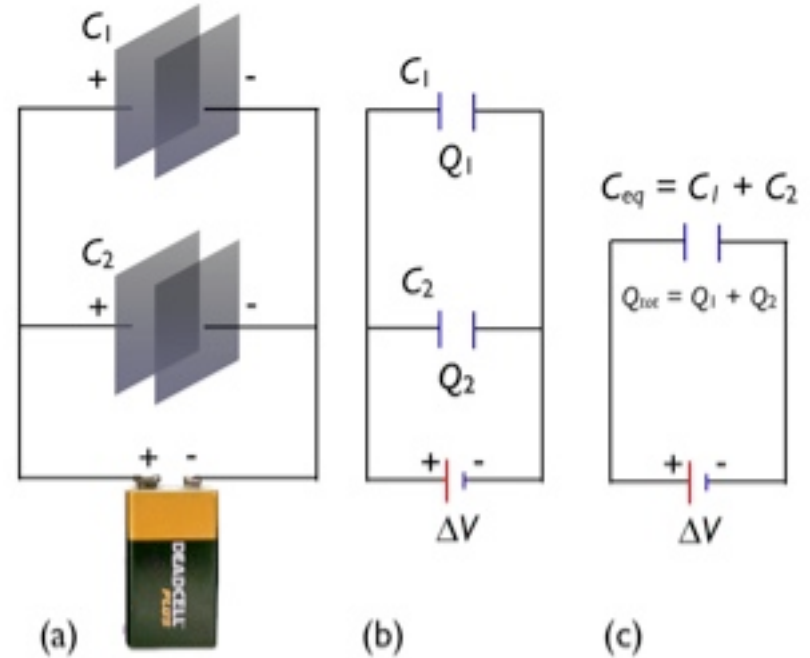
$$C_{\text{eq}} = C_1 + C_2 + C_3 + \dots$$




Two Capacitors in Series:


$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2}$$

Three or More Capacitors in Series:
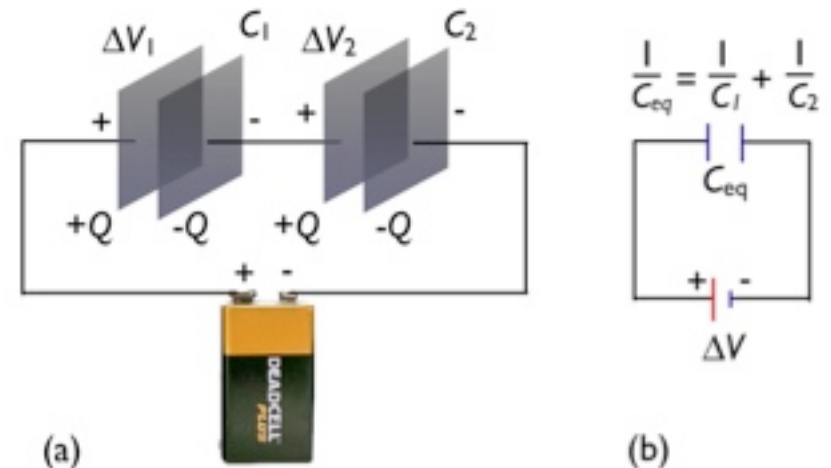
$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots$$



capacitors with stuff inside

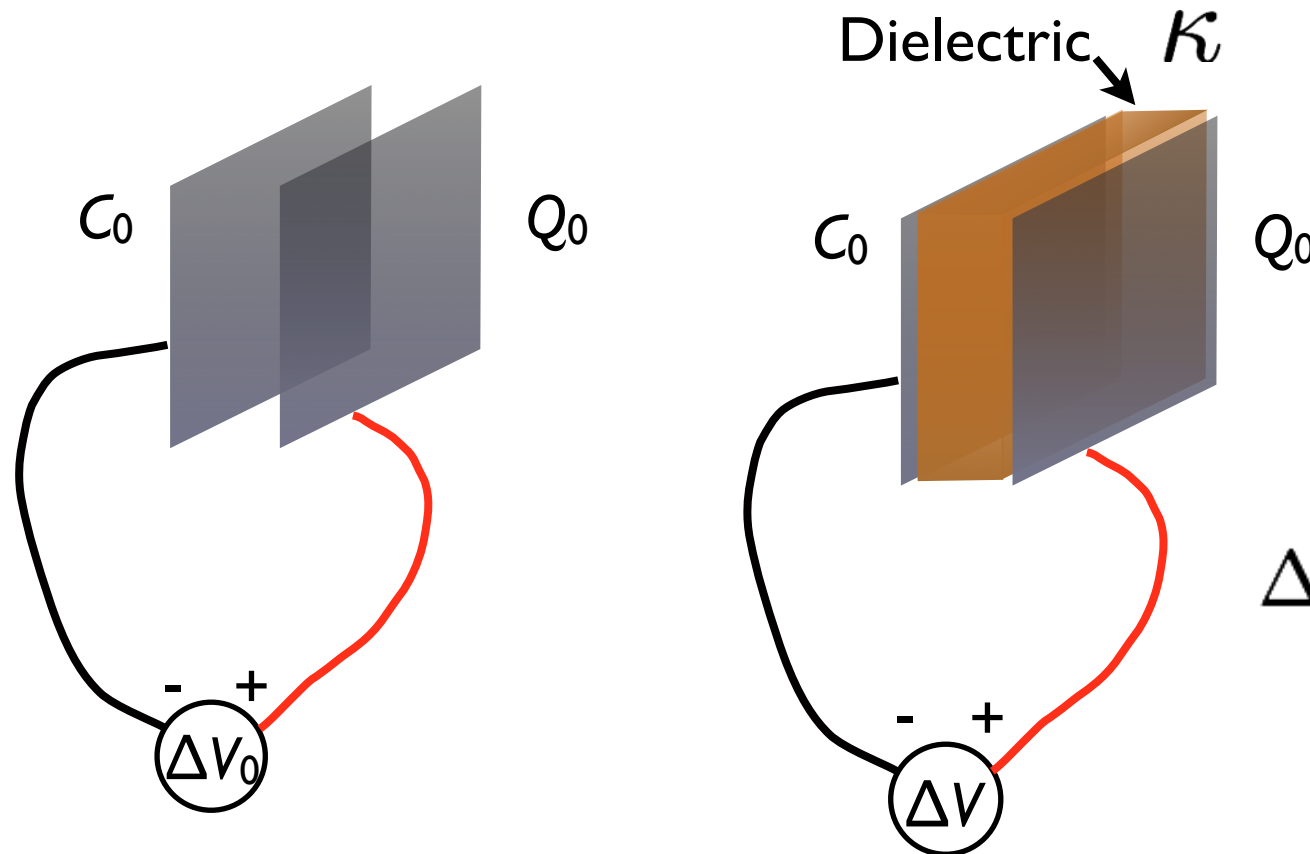



$$\Delta V = \frac{\Delta V_0}{\kappa} = \frac{\Delta V_0}{\epsilon_r}$$
$$C = \frac{Q_0}{\Delta V} = \frac{\kappa Q_0}{\Delta V_0}$$

Parallel plate capacitor with a dielectric between the plates:

$$C = \kappa \epsilon_0 \frac{A}{d} = \epsilon_r \epsilon_0 \frac{A}{d} \quad (4.29)$$

the dielectric *increases* the capacitance by a factor κ , the dielectric constant. The dielectric constant is also written ϵ_r sometimes.

rc circuits

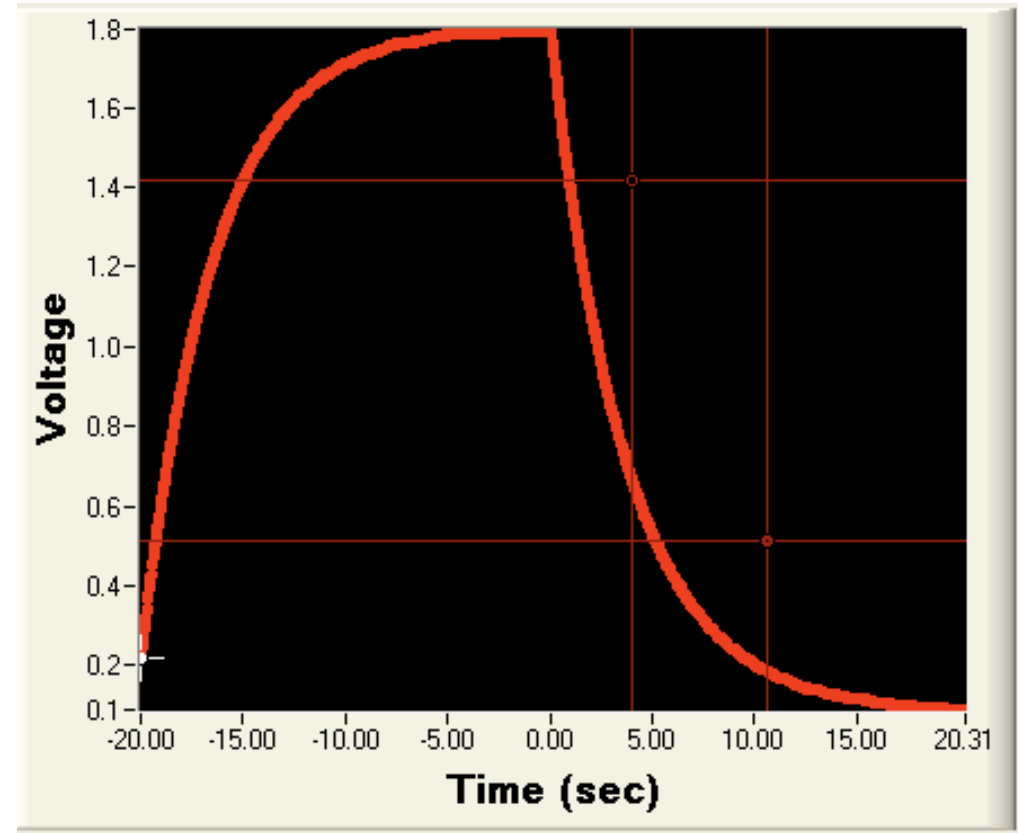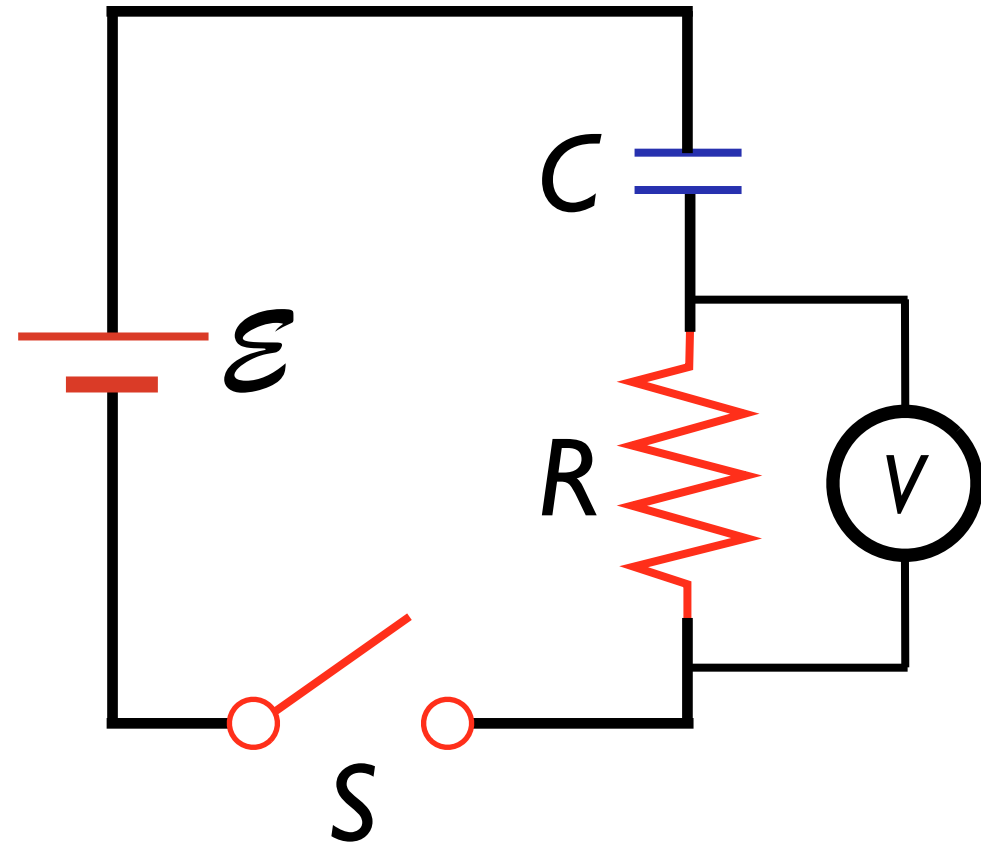

$$V \propto e^{-\tau/RC}$$


Time constant τ of an RC circuit:

$$\tau = RC$$

(6.27)

This gives τ in seconds [s] when R is in Ohms [Ω] and C is in farads [F].

RC differentiator

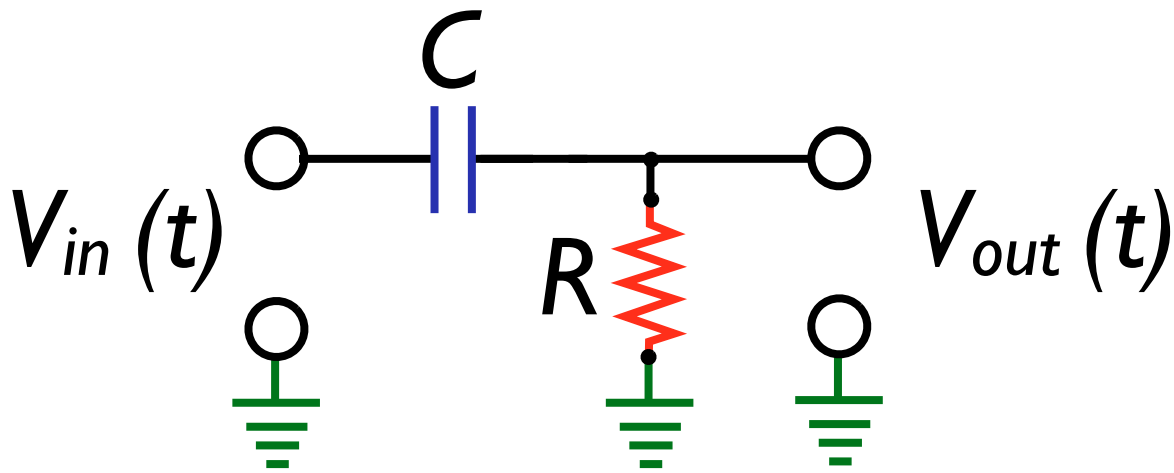


$$I = C \frac{d}{dt} (V_{in} - V) = \frac{V}{R}$$

for small RC ,

$$C \frac{dV_{in}}{dt} \approx \frac{V}{R}$$

$$V(t) \approx RC \frac{d}{dt} V_{in}(t)$$

RC integrator

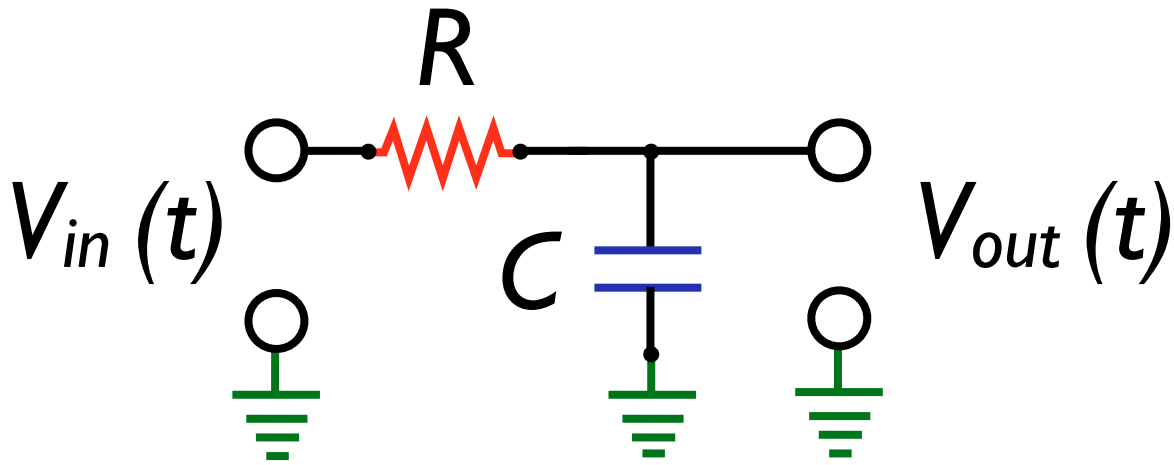

$$I = C \frac{dV}{dt} = \frac{V_{in} - V}{R}$$

for large RC ($V \ll V_{in}$)

$$C \frac{dV}{dt} \approx \frac{V_{in}}{R}$$

$$V(t) = \frac{1}{RC} \int^t V_{in}(t) dt + \text{const}$$


so what?

filtering of signals

unintentional capacitive coupling
see from waveform shape

more later


ac resistive circuits

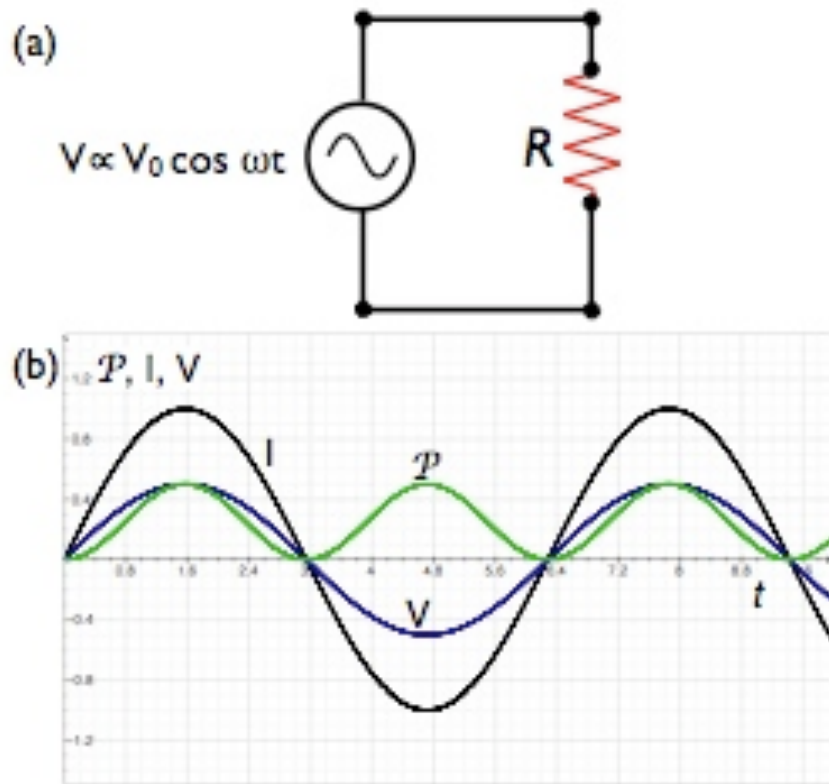


nothing earth-shattering happens
except P is lower than you expect

ac capacitive circuits

(a)

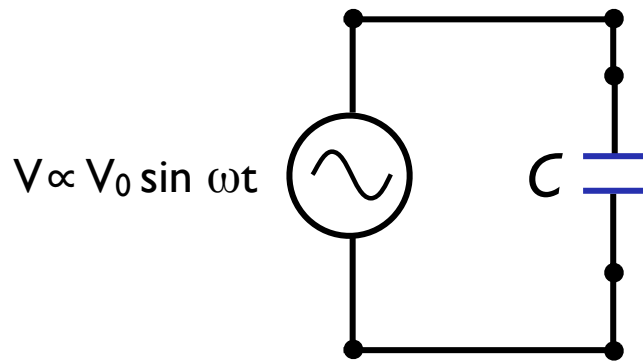

(b)

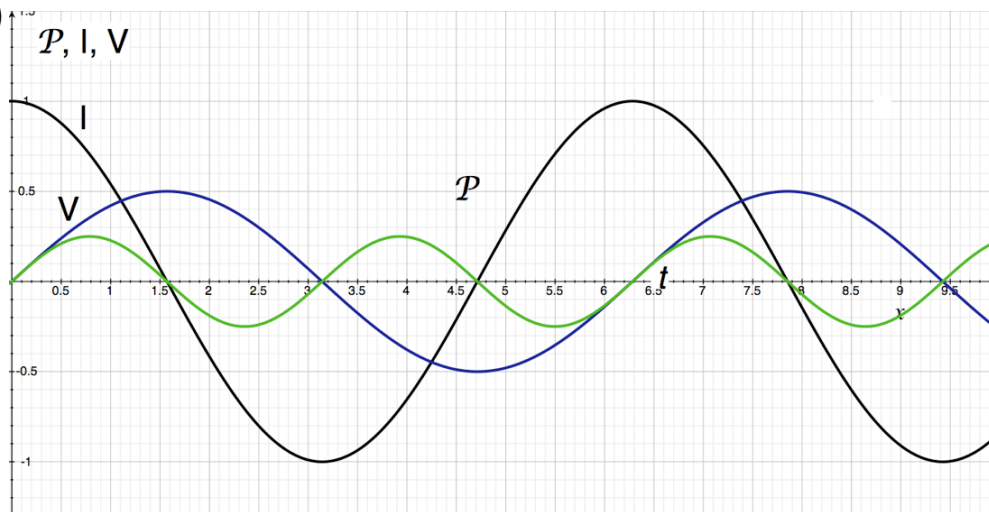

I and V 90° out of phase
average power is ZERO



frequency response?
insulating at dc
conducting at high f

voltage “lags” current



$$Z = \frac{1}{i\omega C} = \frac{-1}{2\pi i f C}$$

filters


low-pass

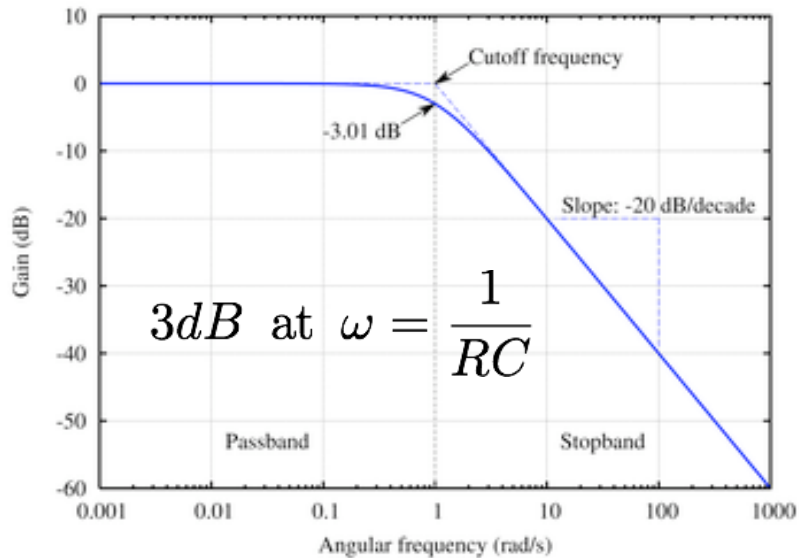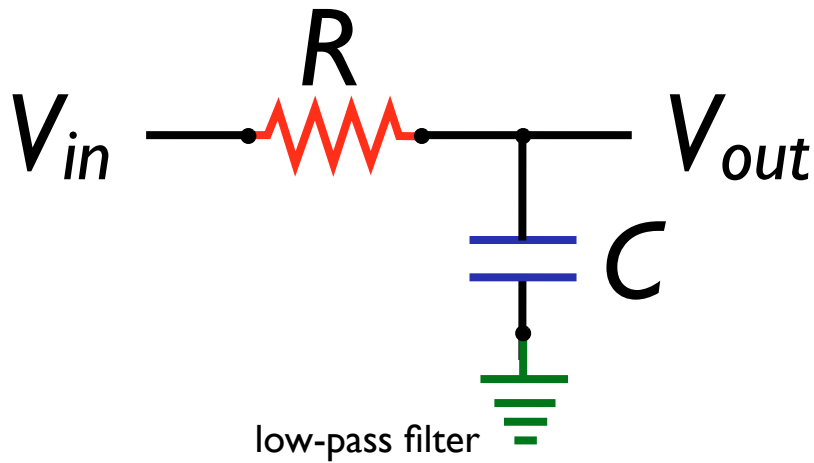

high-pass

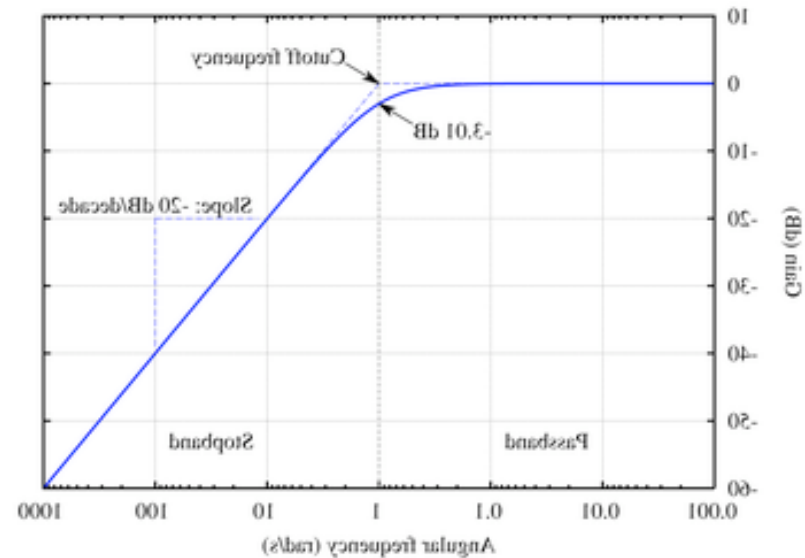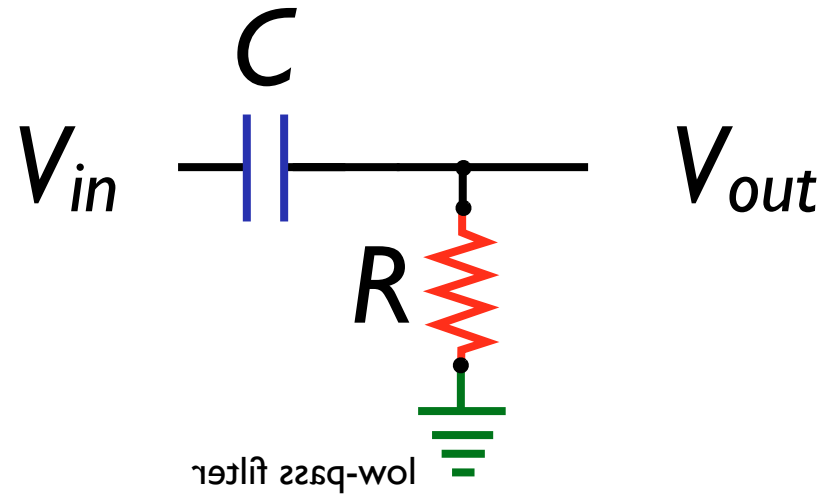


familiar?

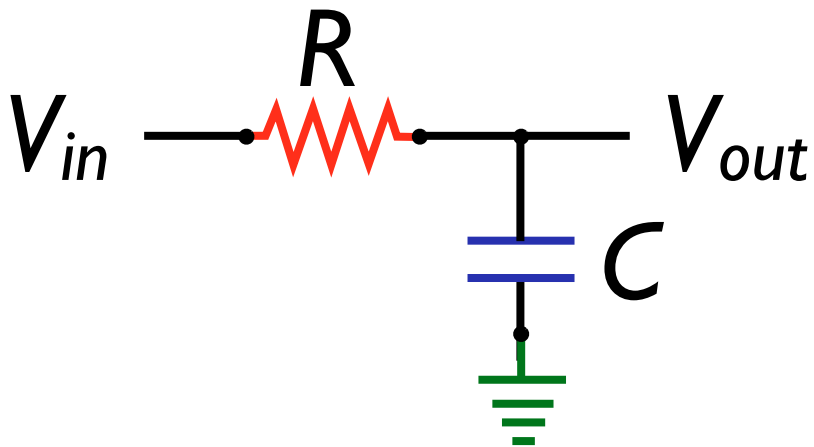

low-pass filter

integrator
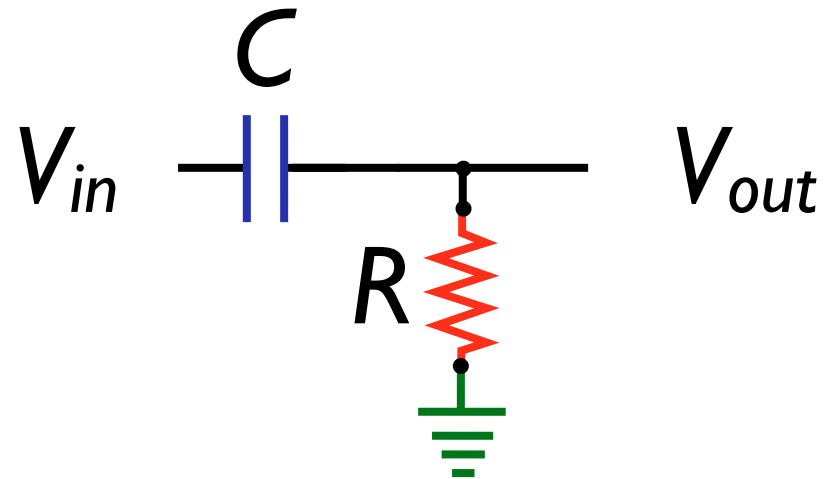
$$V(t) = \frac{1}{RC} \int V_{in}(t) dt + \text{const}$$



high-pass filter

differentiator



$$V(t) \approx RC \frac{d}{dt} V_{in}(t)$$

frequency domain





time domain





high-pass

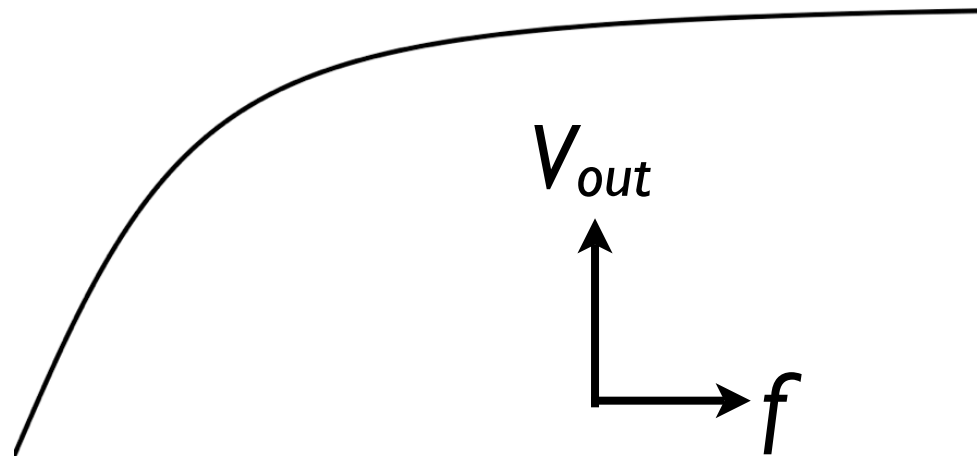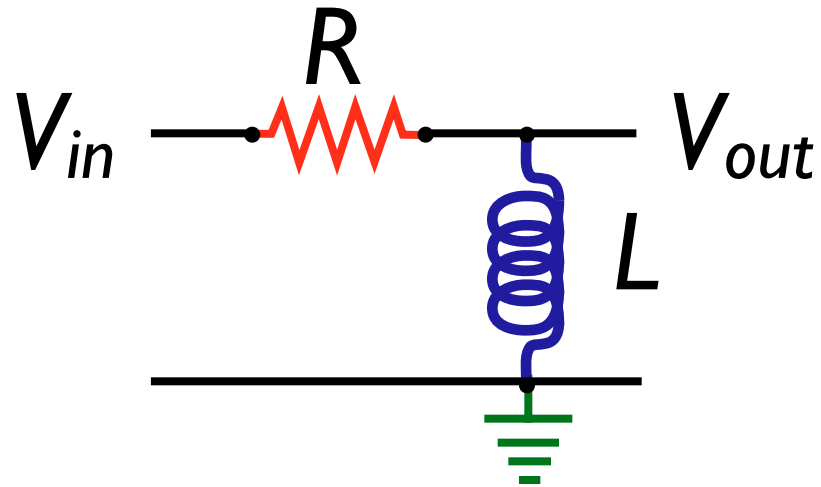



low-pass

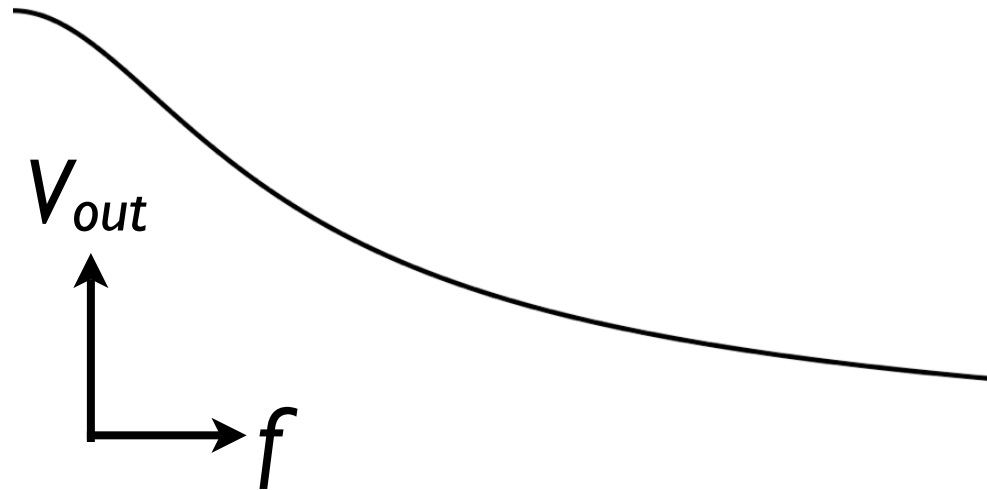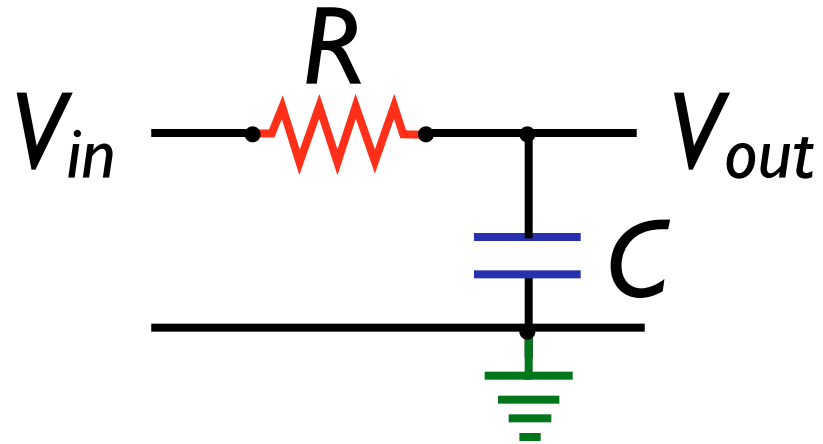


audio crossovers

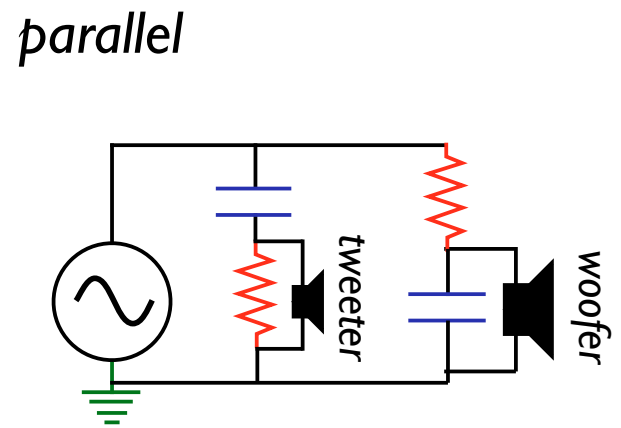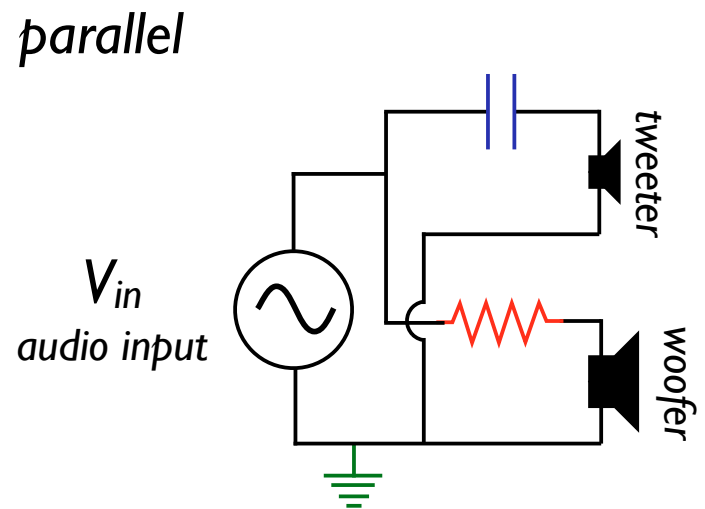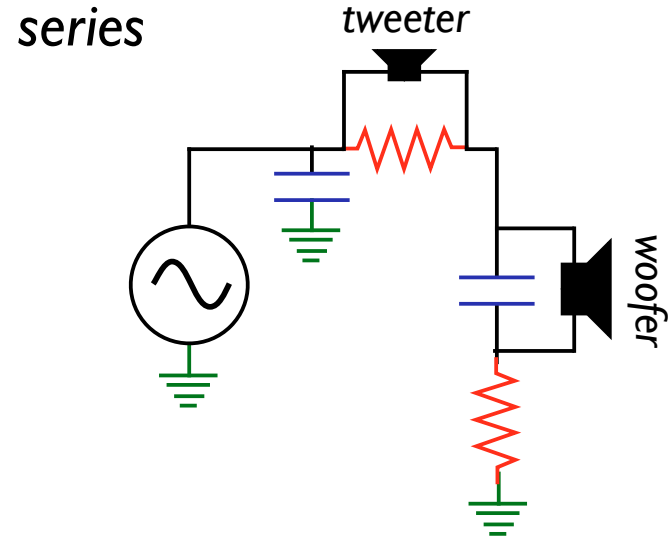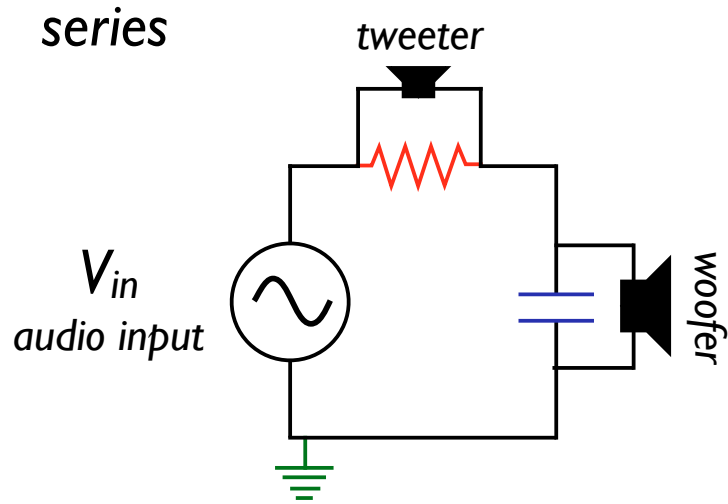

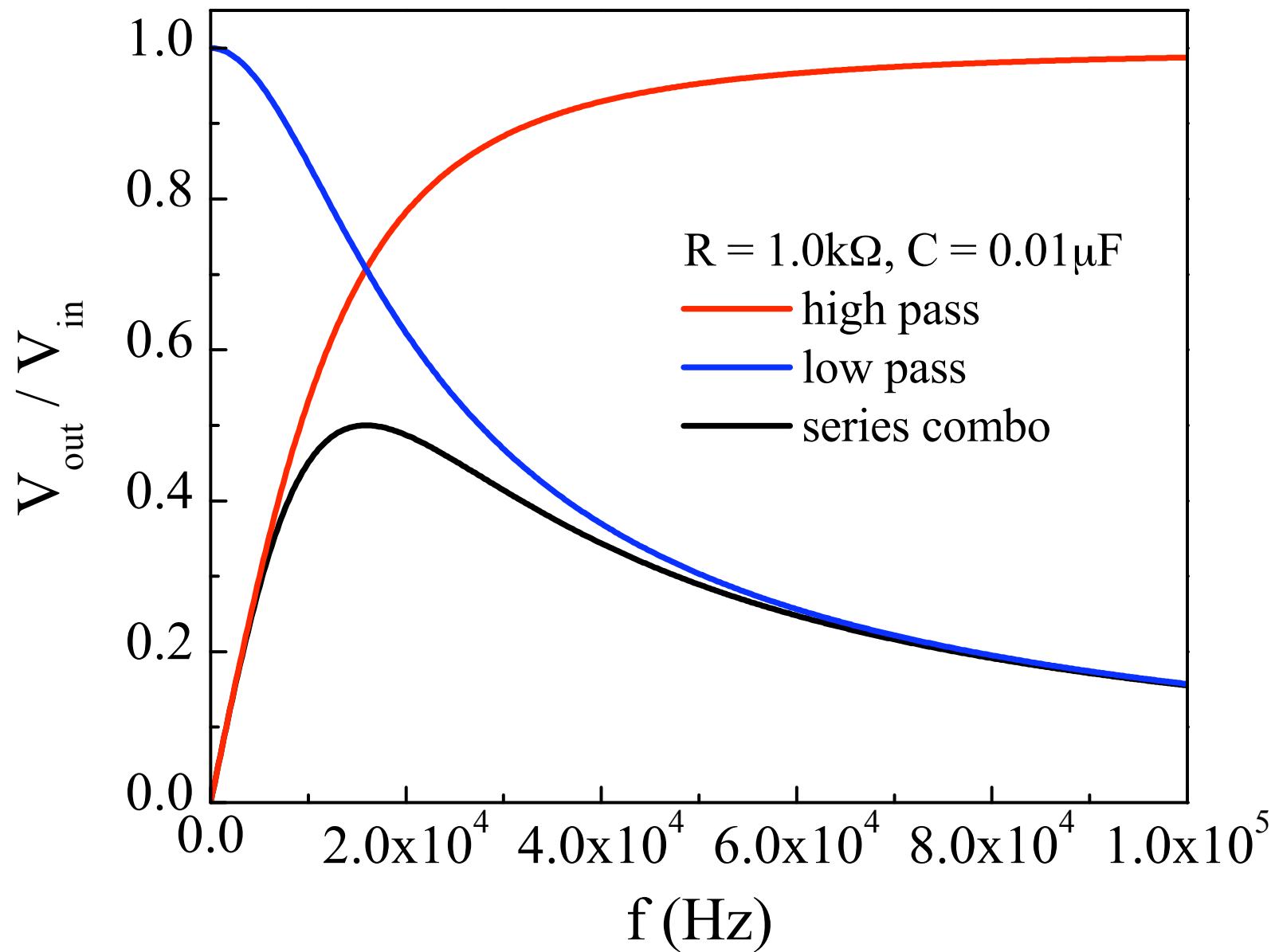

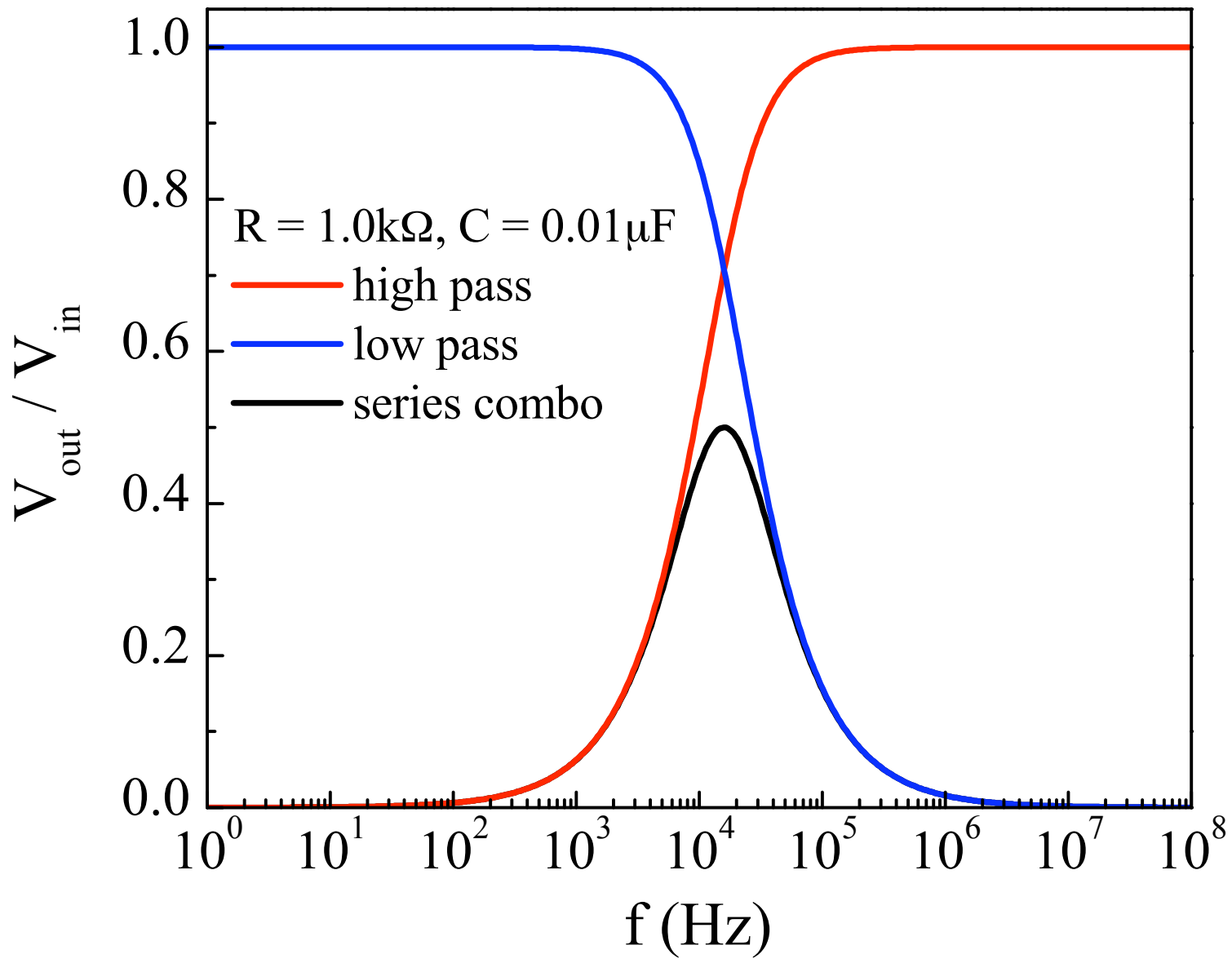


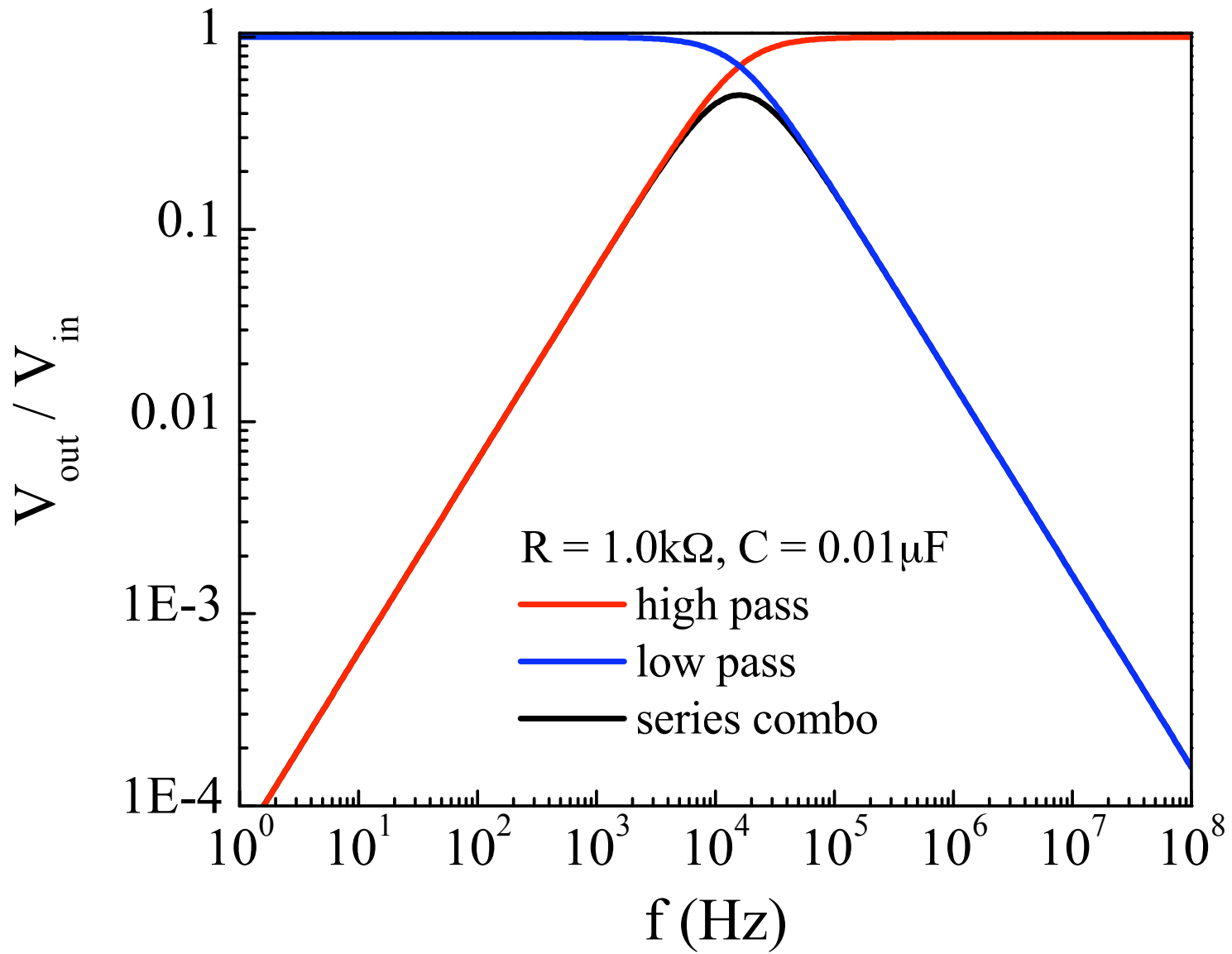

dB/decade ...

Today:

amplify photodiode signal

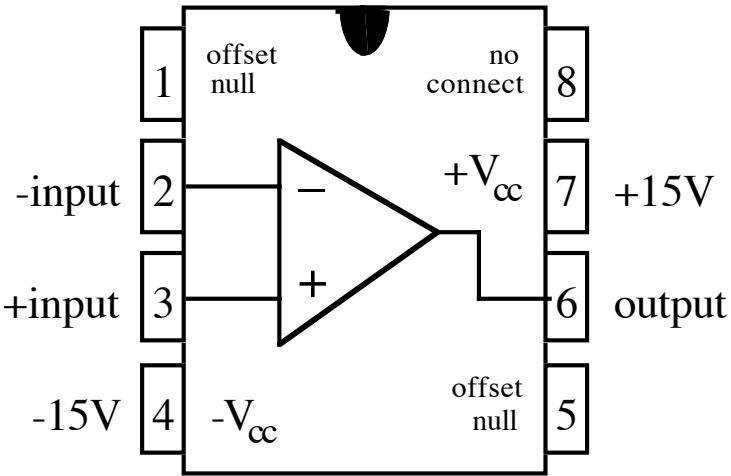

741 pinout

100k

