
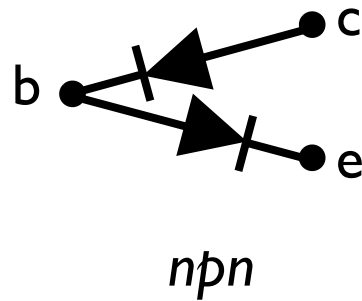


Transistors, so far

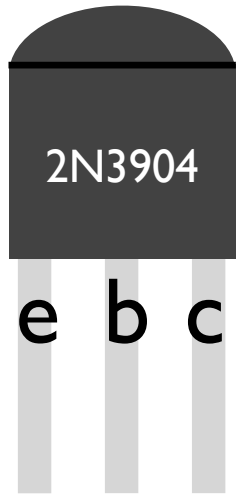


Rules

1. $V_c > V_e$
2. b-e and b-c circuits \sim diodes
3. max values of I_c , I_b , V_{ce}
4. if rules are obeyed,

$$I_c = \beta I_b$$

$\beta \sim 100$, but variable

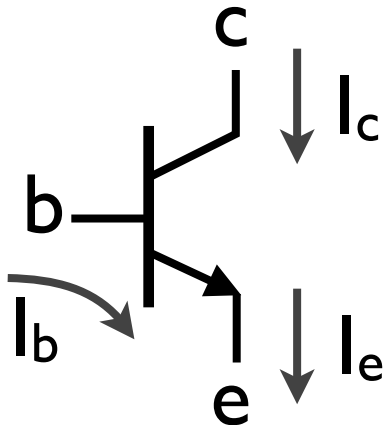


conservation of current:

$$I_e = I_c + I_b = \beta I_b + I_b = (1 + \beta) I_b \approx \beta I_b$$

Simple view

$$I_e = (1 + \beta) I_b$$

$$V_b = V_e + 0.6$$

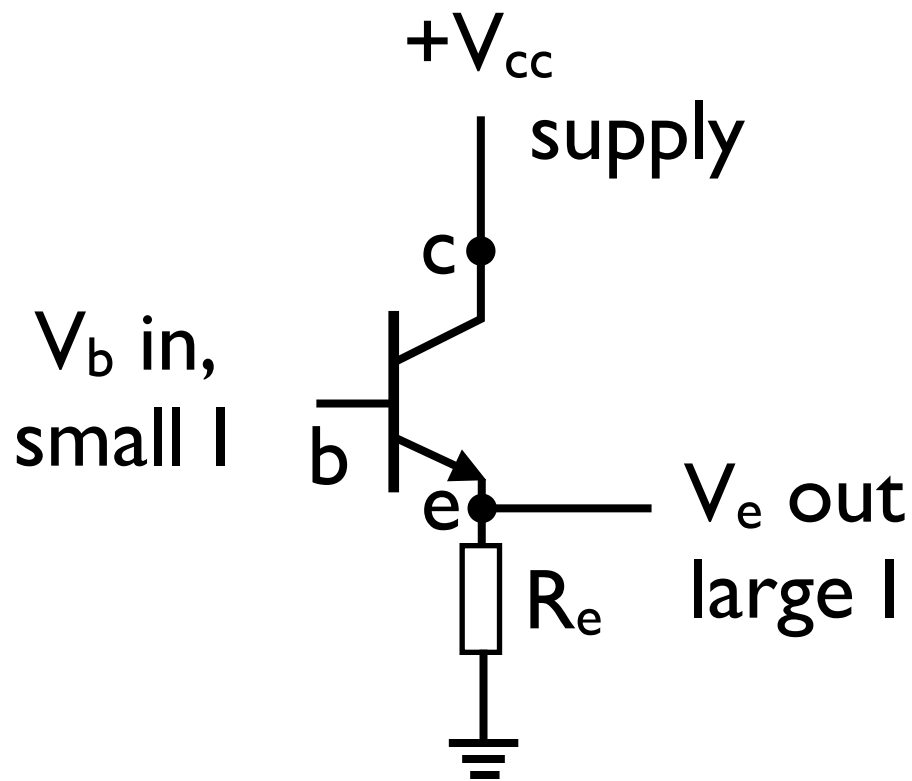


follower:

output voltage ~ same
output *current* larger


output resistance lower

Current Source

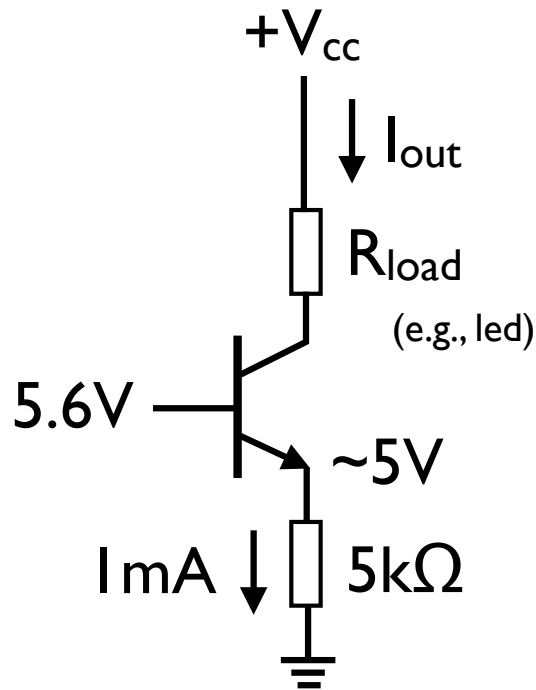- 1) pick load current
- 2) pick emitter resistor and bias
- 3) set up base V divider



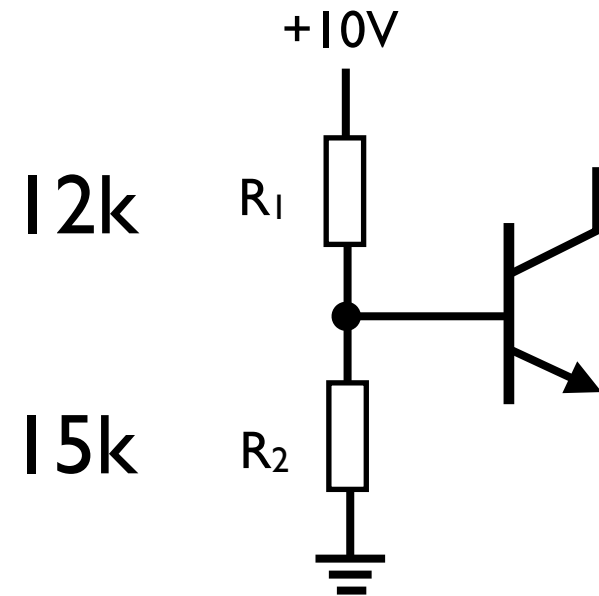want $1mA$, pick $5V$ over $5k$
(keep power $\sim mW$)
make $V_e \sim 1V$ for stability
sets base at $5.6V$



given $10V$ supply, split to $5.6V$
to ignore base current/load ...
resistance into base $\sim \beta R_e$
divider R 's smaller

caveats:



want divider 'stiff' c.f. βR_e so $V_b \sim \text{constant}$

can't push V_e below ground

require $V_e < V_c$

limits voltage drop across load to a bit under V_{supply}

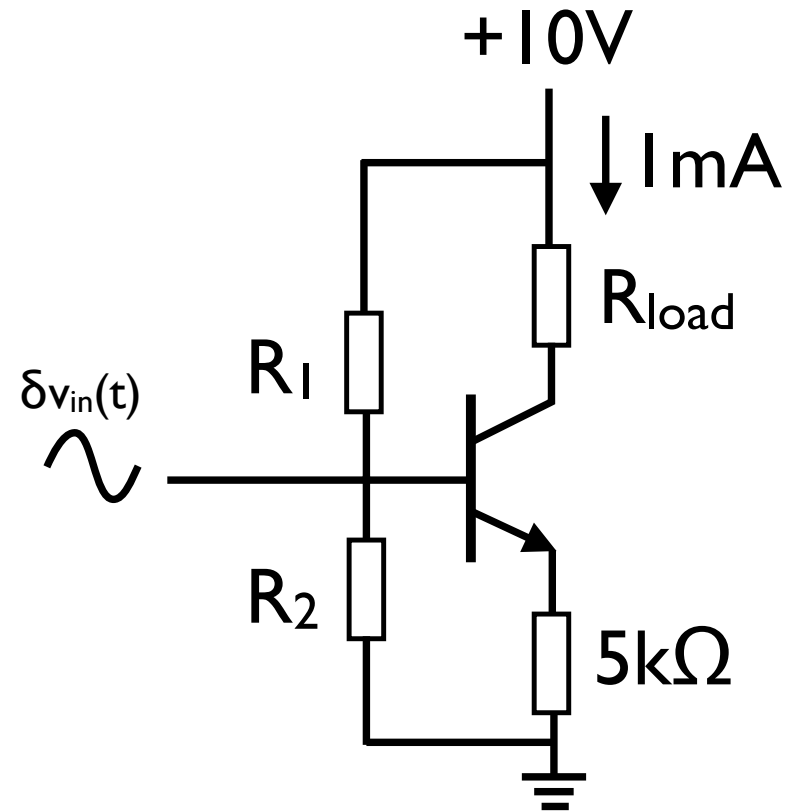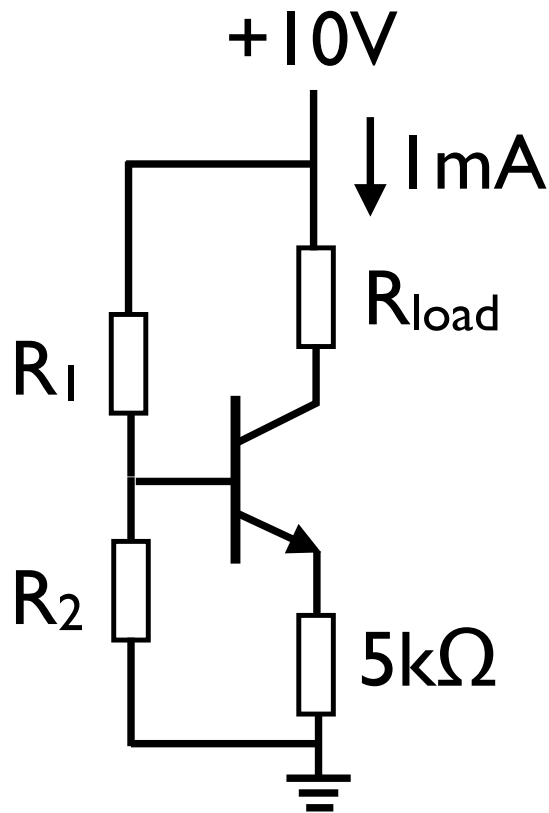still: very good & stable I source, simple



programmable: add a signal at the base ...

Signals: voltage & current varying in time

sine

ramp

pulse

noise

resistor doesn't care


capacitor follows $I = C \, dV/dt$

e.g., differentiator / integrator circuits


really analog signal processing

feed resistor a sine wave
it doesn't care

(a)

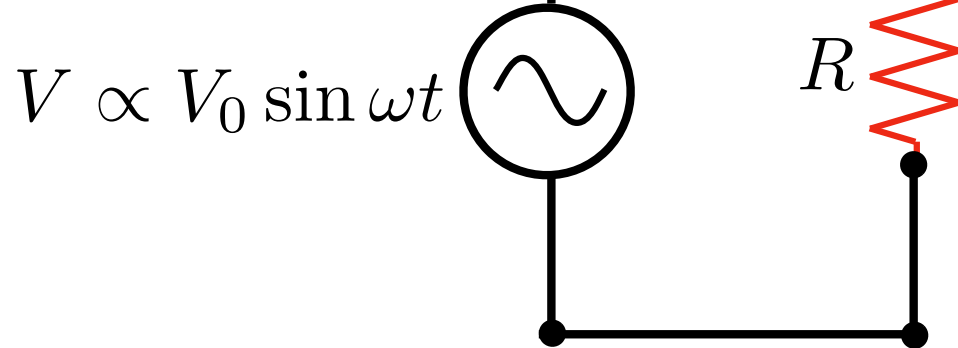


(b)

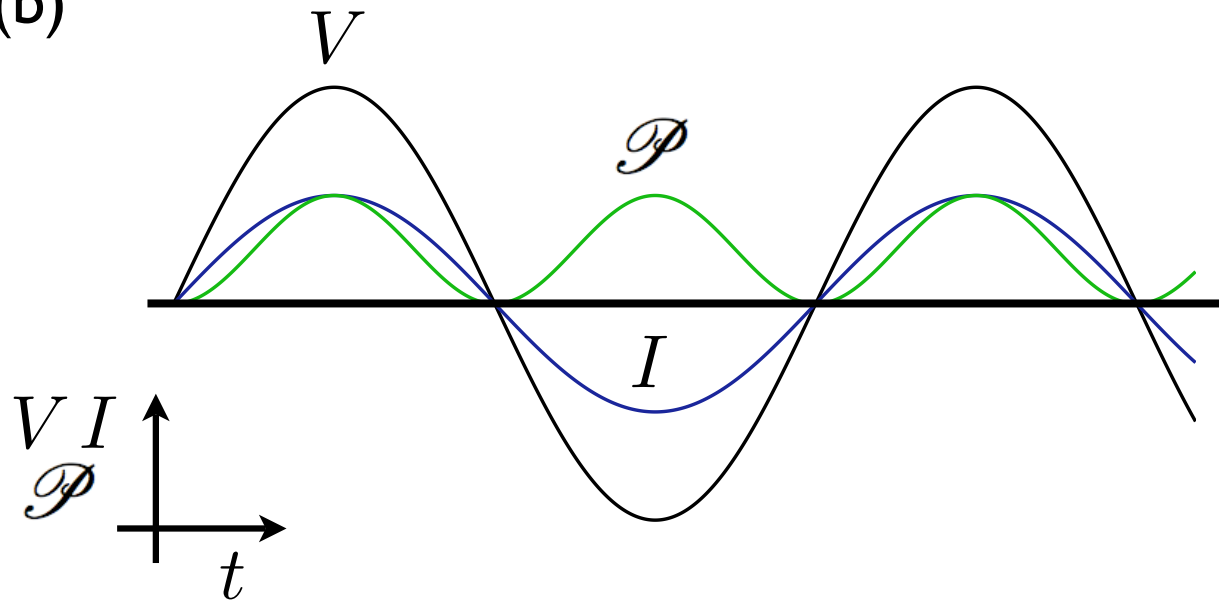


(a)

$$V \propto V_0 \sin \omega t$$


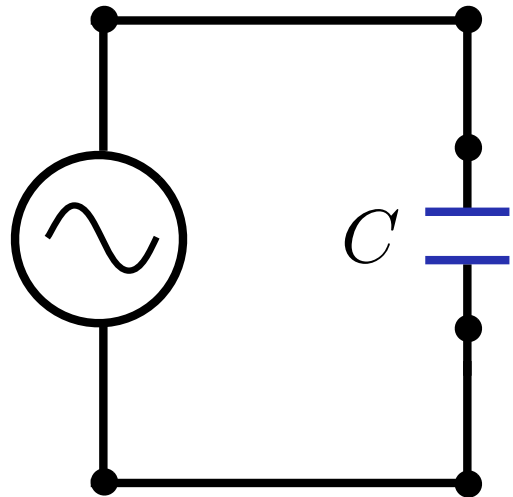


feed capacitor a sine wave ...
 current is cosine! $\sim dV/dt$
 charging/discharging
 power goes in & out


(b)

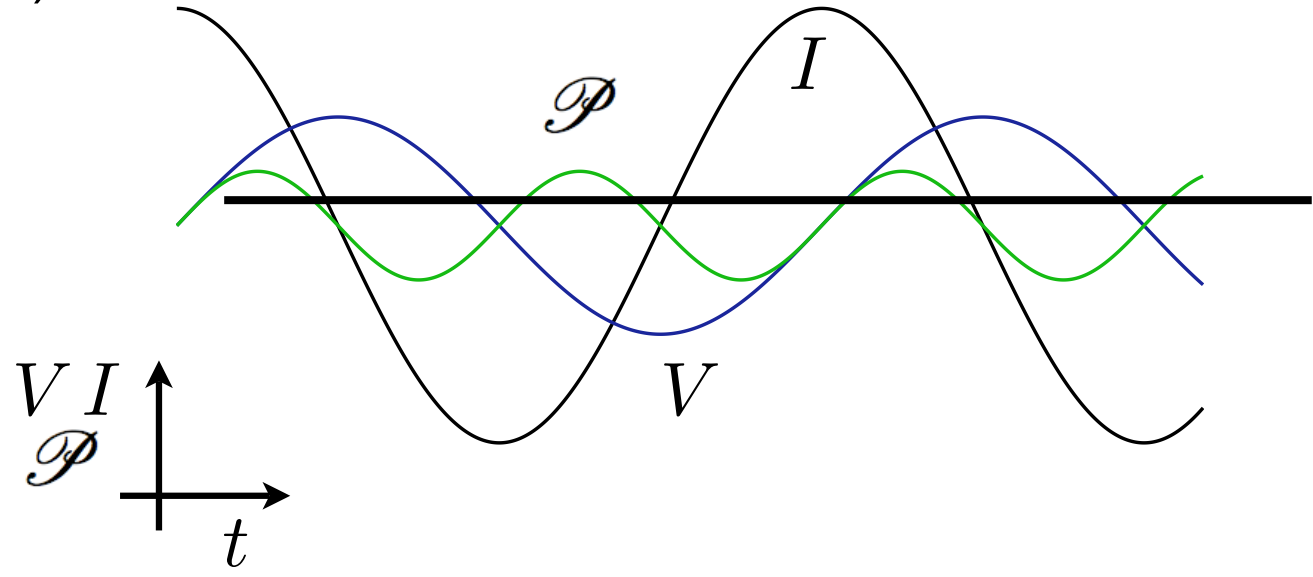


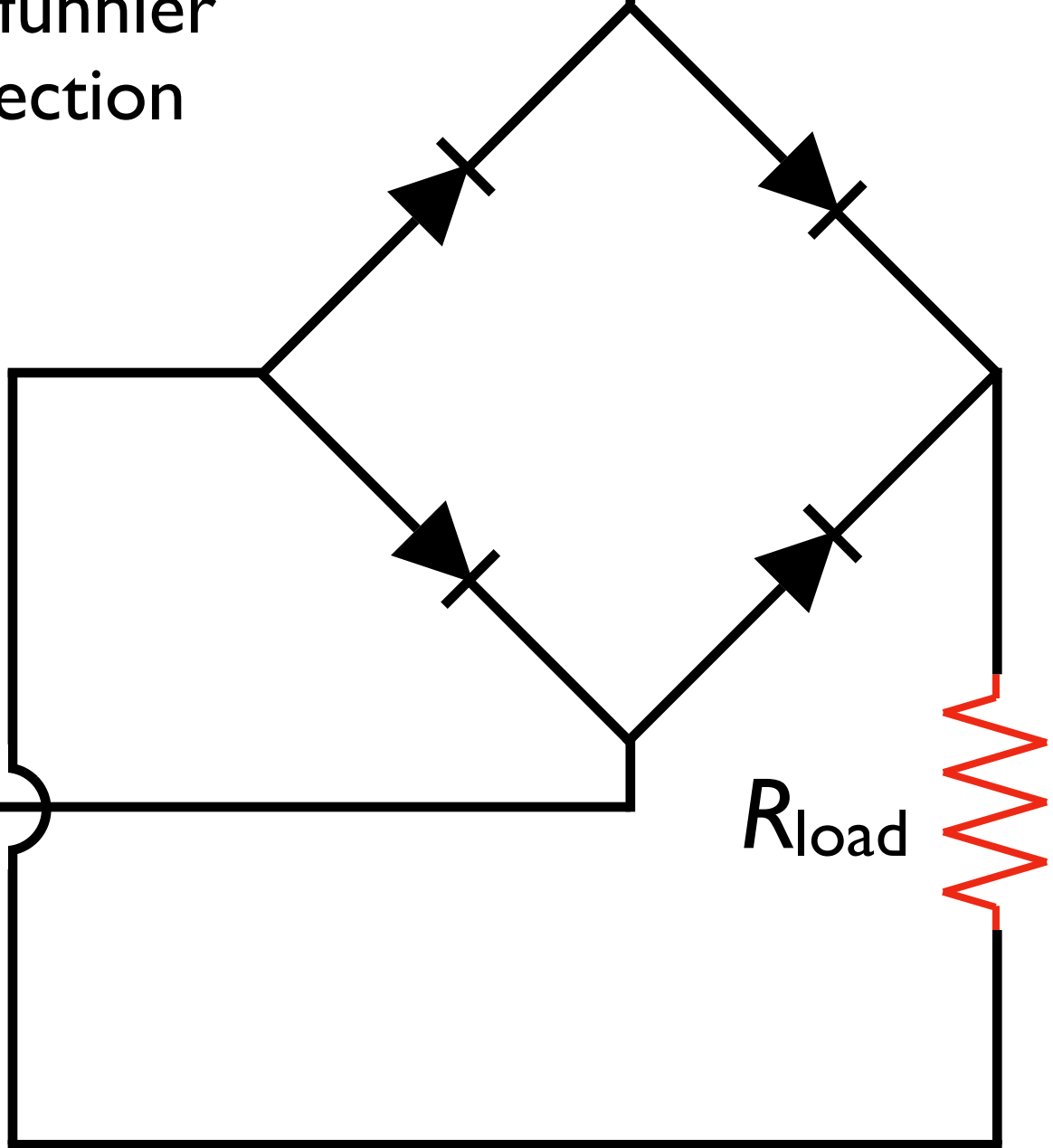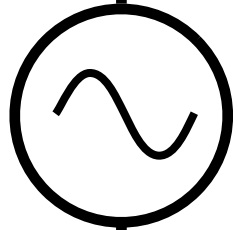
diodes are even funnier
current in 1 direction




wires do not
touch here


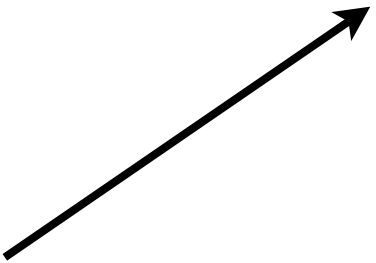


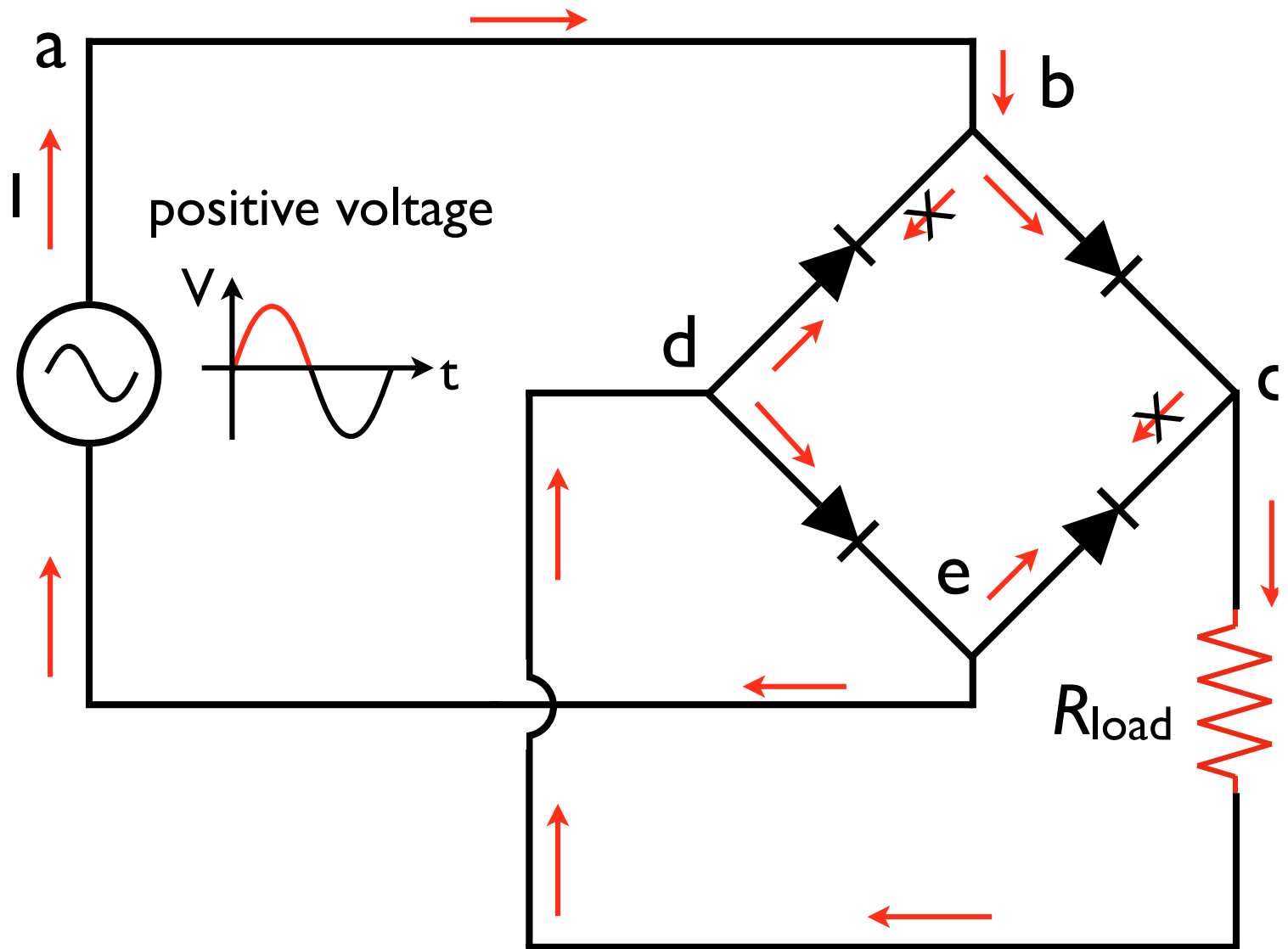

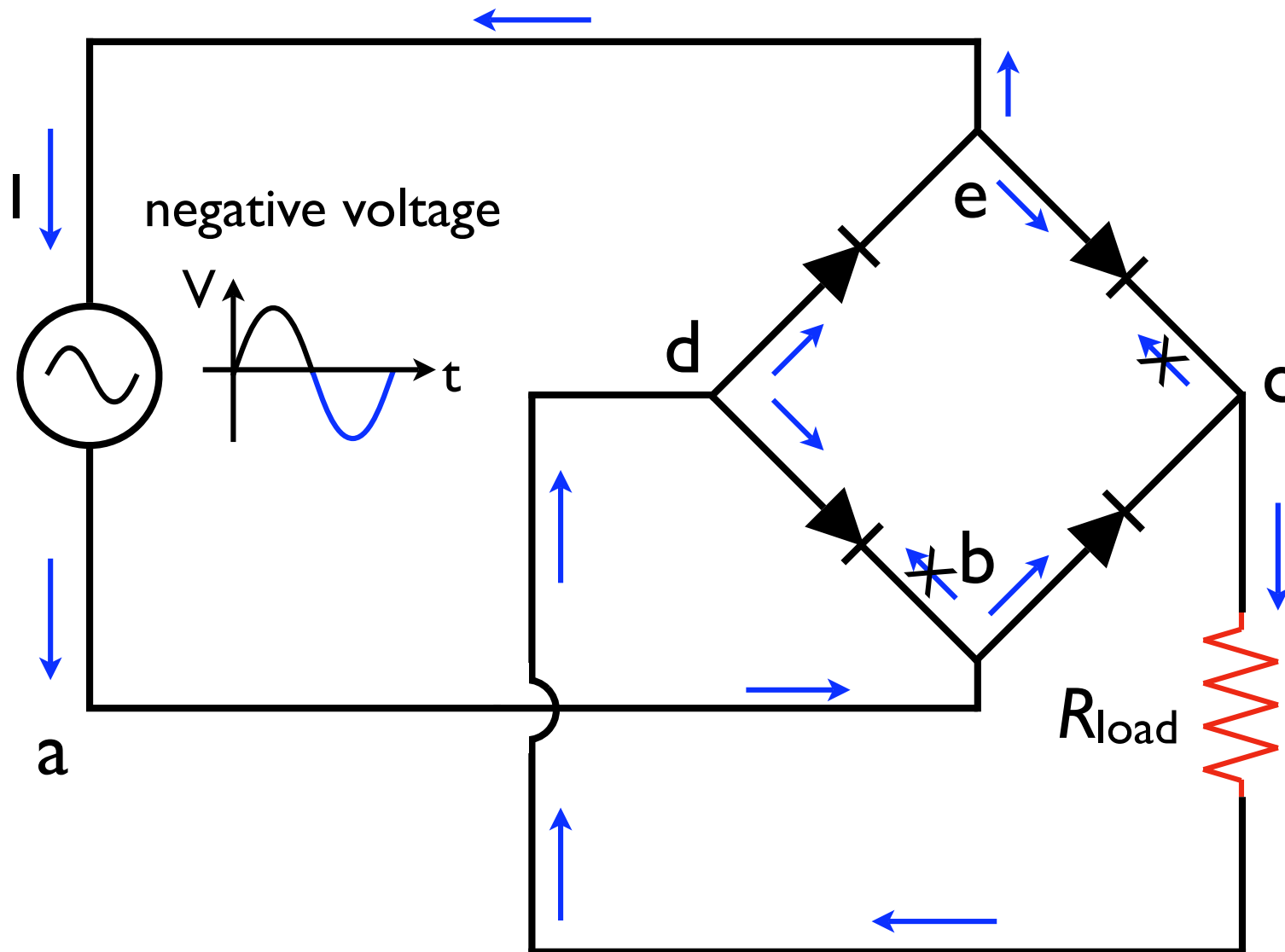

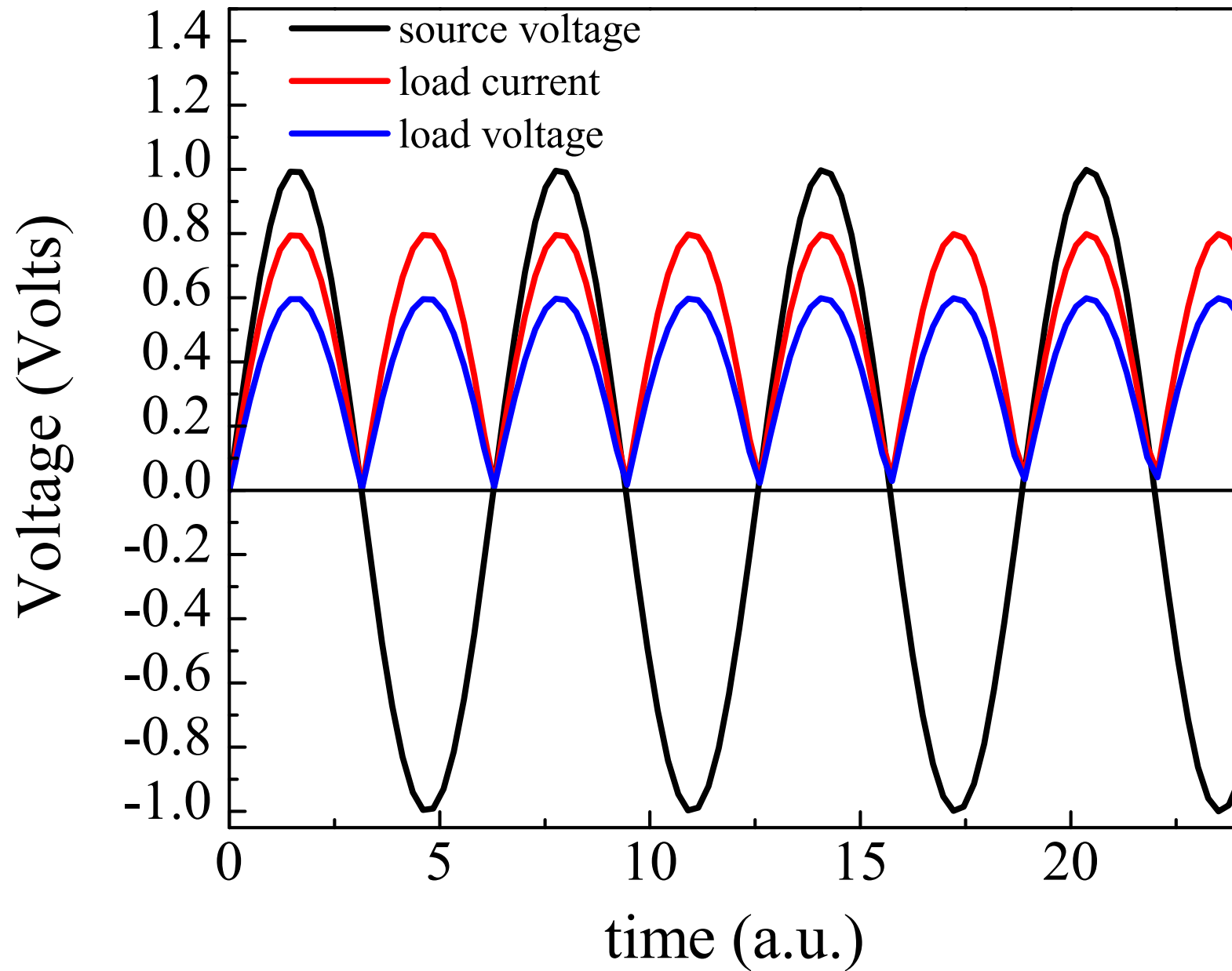

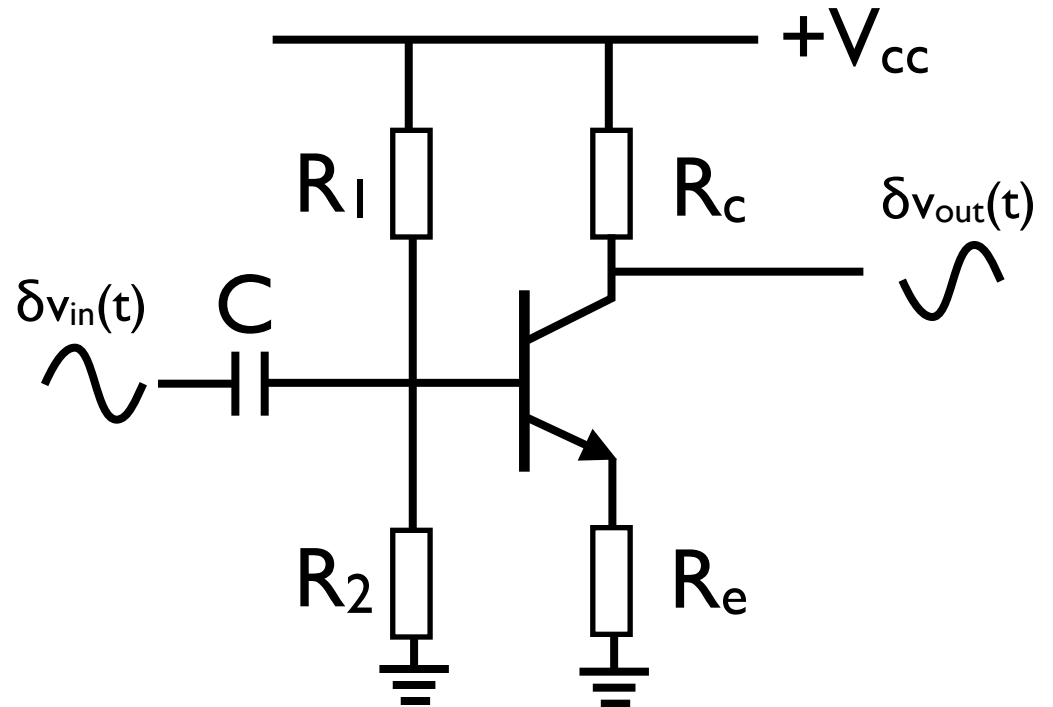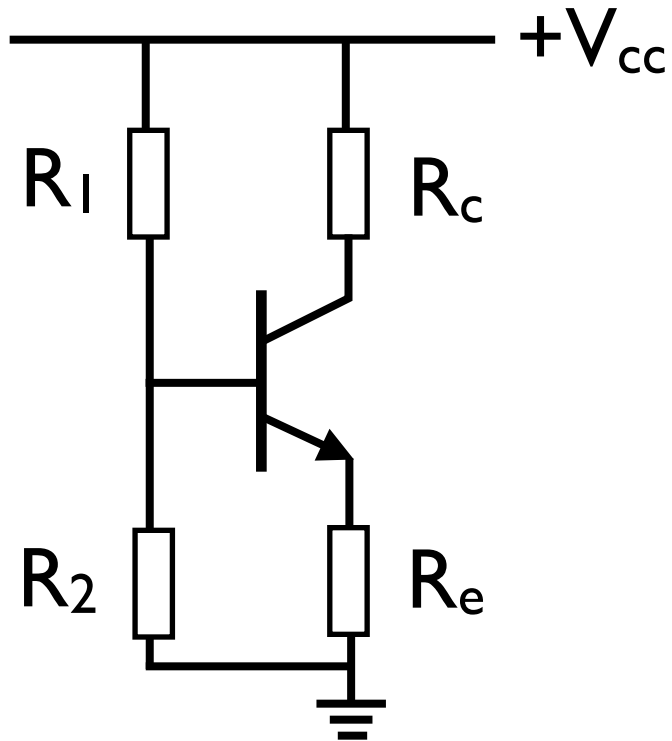look back at I source ... but feed it with a sine wave



just use C to block any constant voltages
(only time-varying gets through)


we'll see later: filtering

static analysis:

1mA through 6k load


base at 1.6V

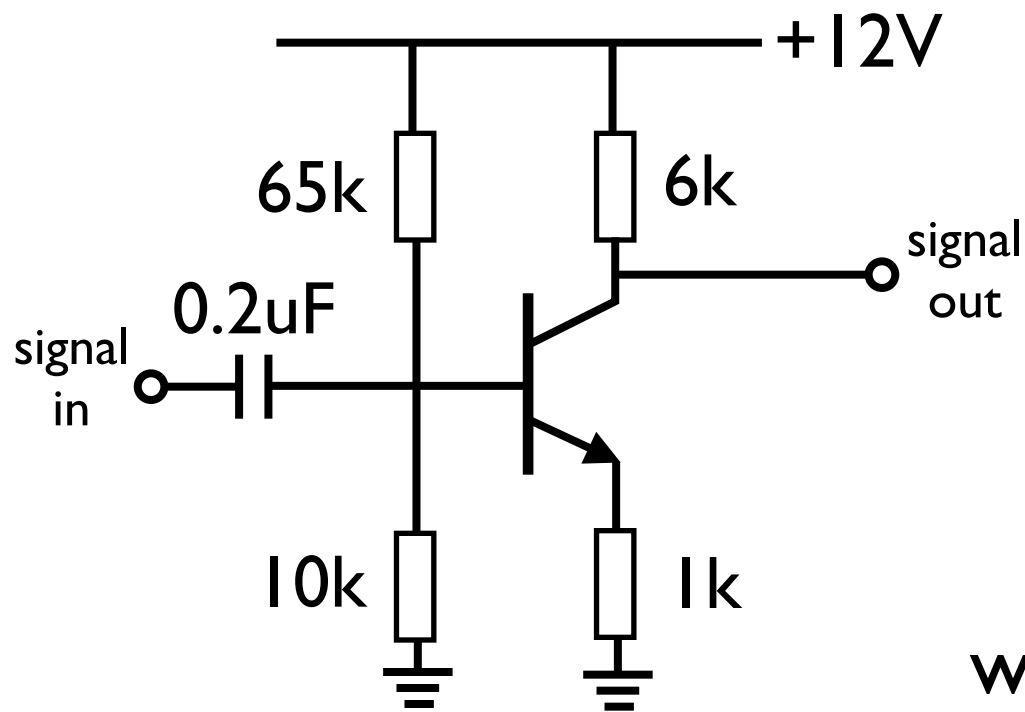what happens for small change in base voltage?



$$V_b - V_e \sim \text{fixed}$$
$$\implies \delta V_e = \delta V_b$$

wiggle at base, emitter follows

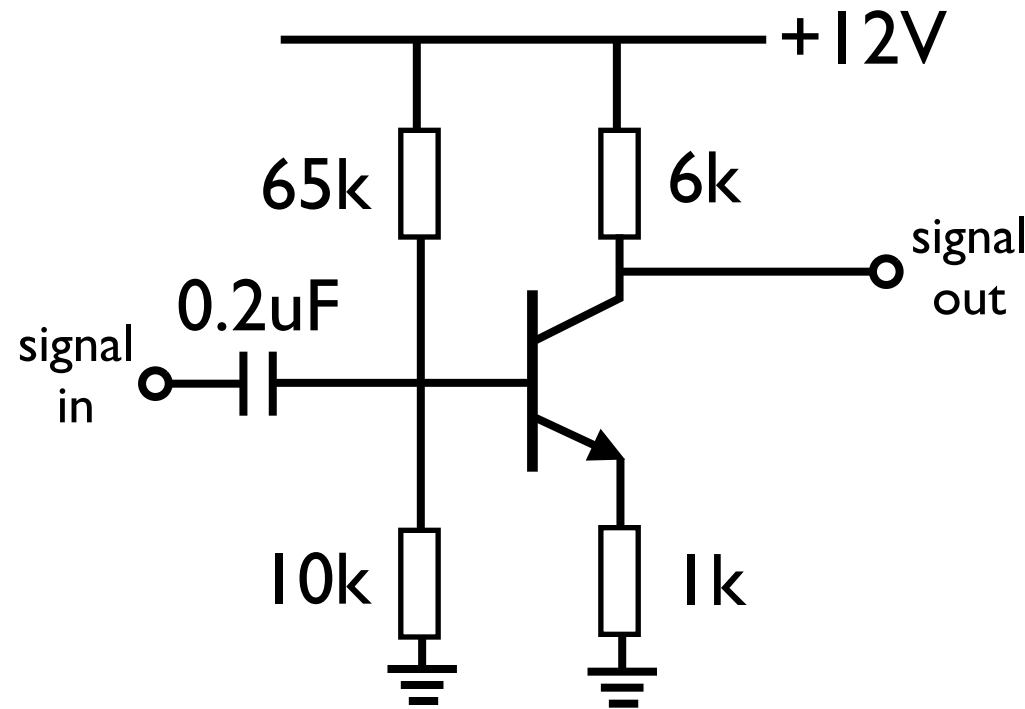

$$\delta v_{\text{in}} = \delta v_e, \quad \delta i_e \approx \delta i_c$$

$$\delta i_e = \delta v_e / R_e = \delta v_{\text{in}} / R_e$$


$$\delta v_{\text{out}} = \delta v_c = -\delta i_c R_c = -\frac{R_c}{R_e} \delta v_{\text{in}}$$

! wiggle input, output wiggles R_c/R_e times larger (but inverted)

*'common emitter amplifier', voltage **gain** of $G = -R_c/R_e$*


no, R_e can't just be zero. thermal drift, instability, distortion ... and power limits

Some generic transistor circuits

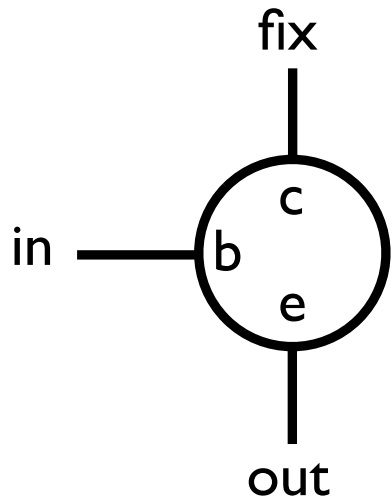


follower

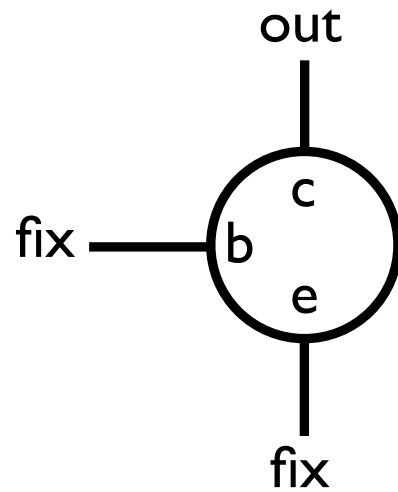$V_{in} \sim V_{out}$
 raises I
 lowers output R




I source

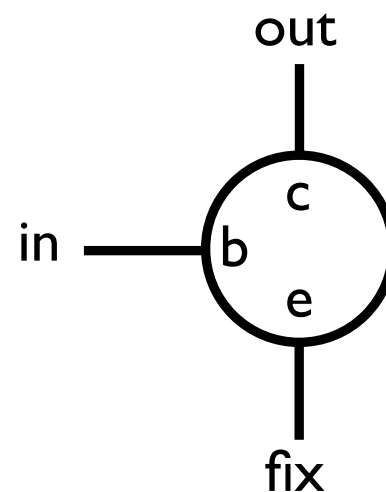fixing V_b fixes V_e
 fixing V_e fixes I_e
 fixing I_e fixes I_c



switch

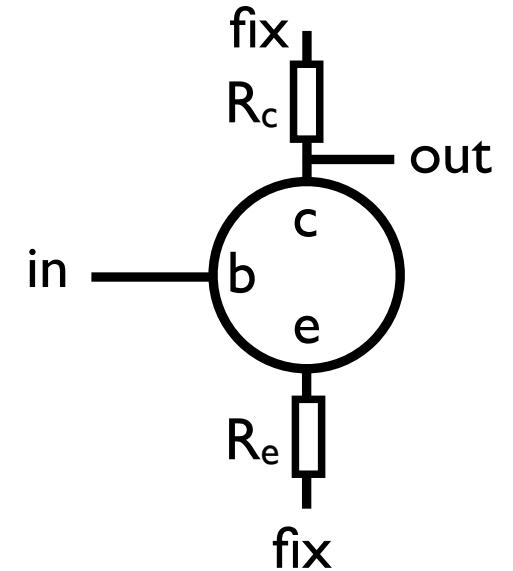$V_b > V_e$, valve opens
 allows I to flow
 from supply to c




amplifier

input fixes V_e
 V_e fixes I_c
 $out/in \sim R_e/R_b$


the comparator

- two inputs: V_+ , V_-
- one output: V_o
- if $V_+ > V_-$, output is open
- if $V_+ < V_-$, output is negative




inputs	output
$V_- > V_+$	negative
$V_+ > V_-$	floating

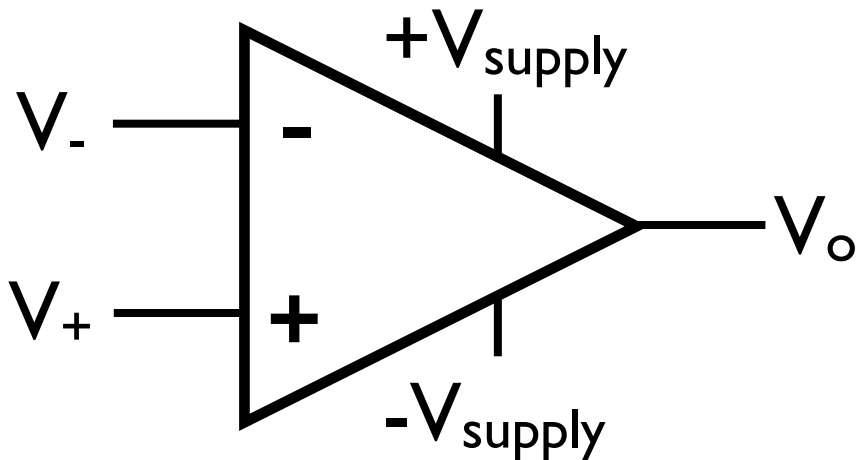

which input is larger?

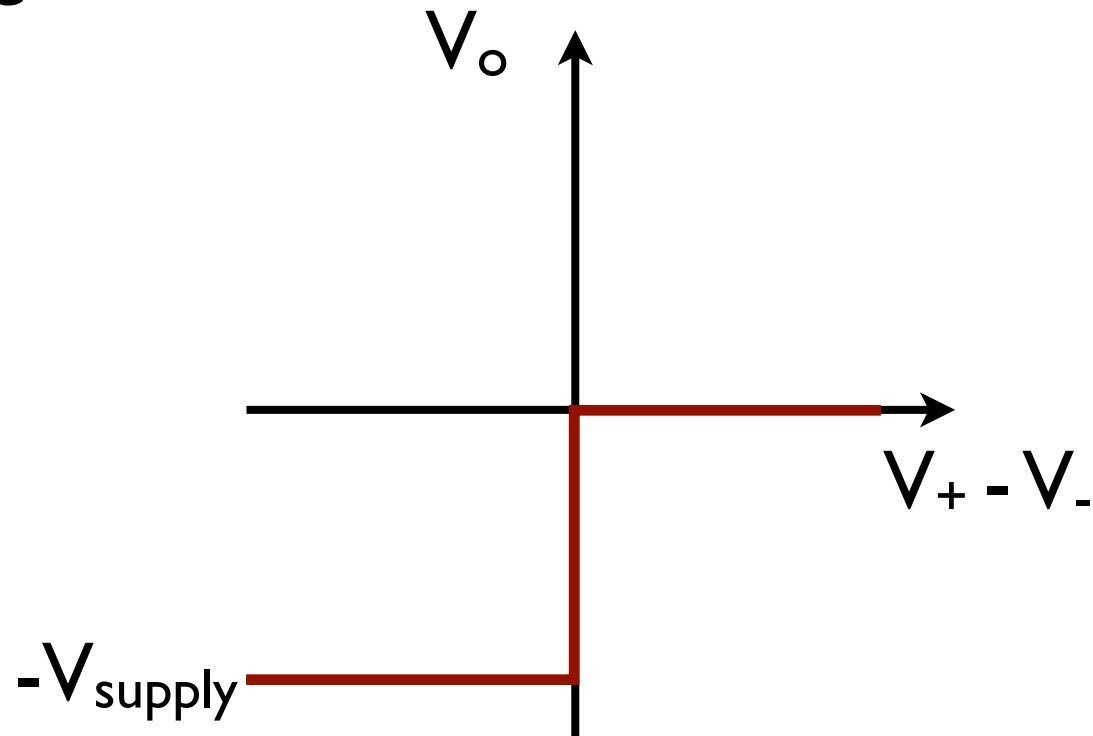


realization & abstraction

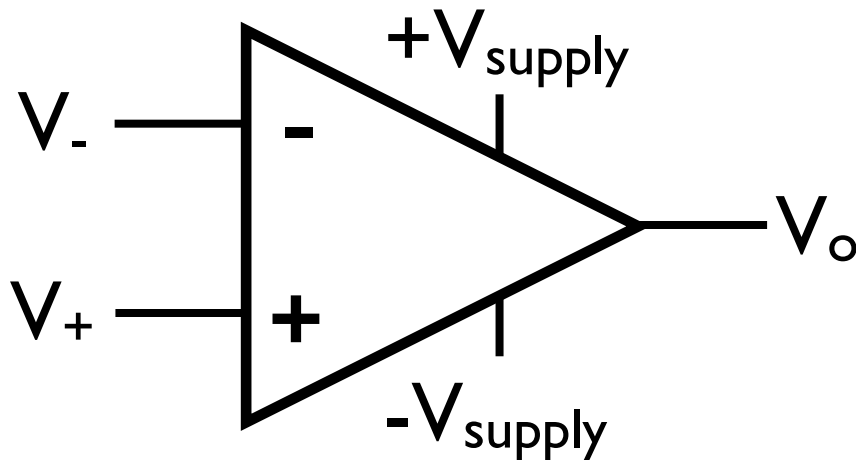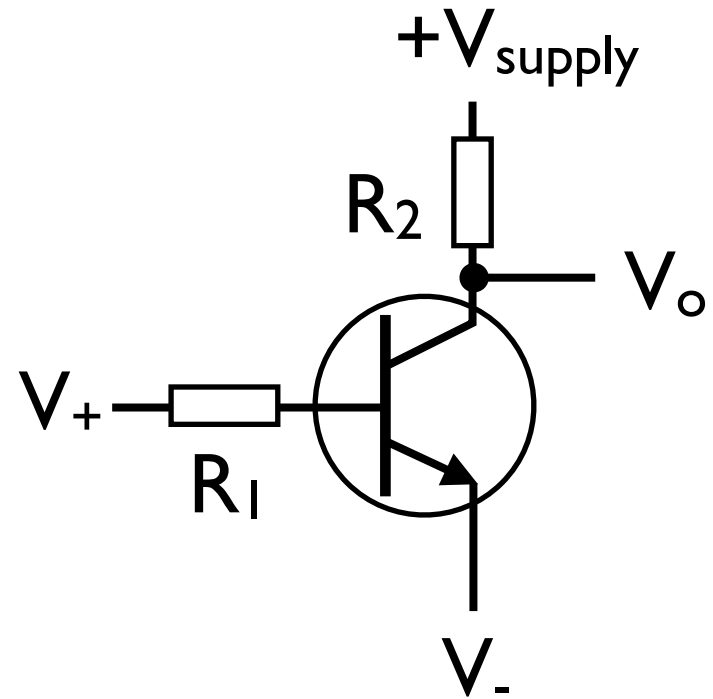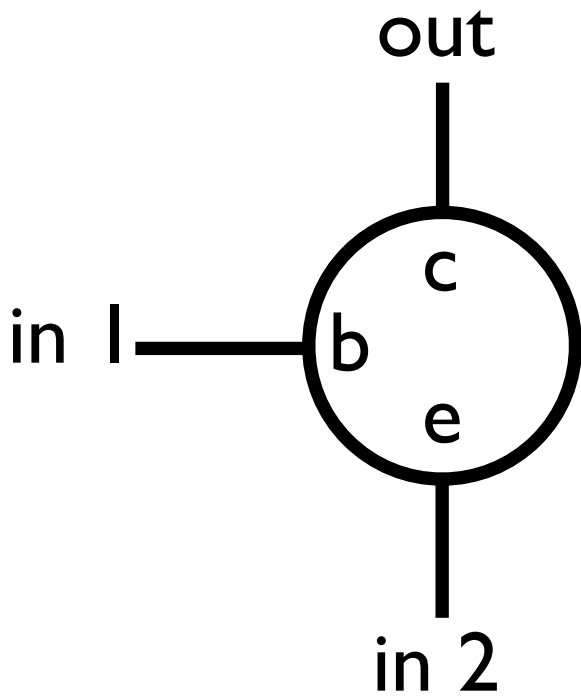

ideal comparator:
inputs draw no current



typical comparator (e.g., LM311)

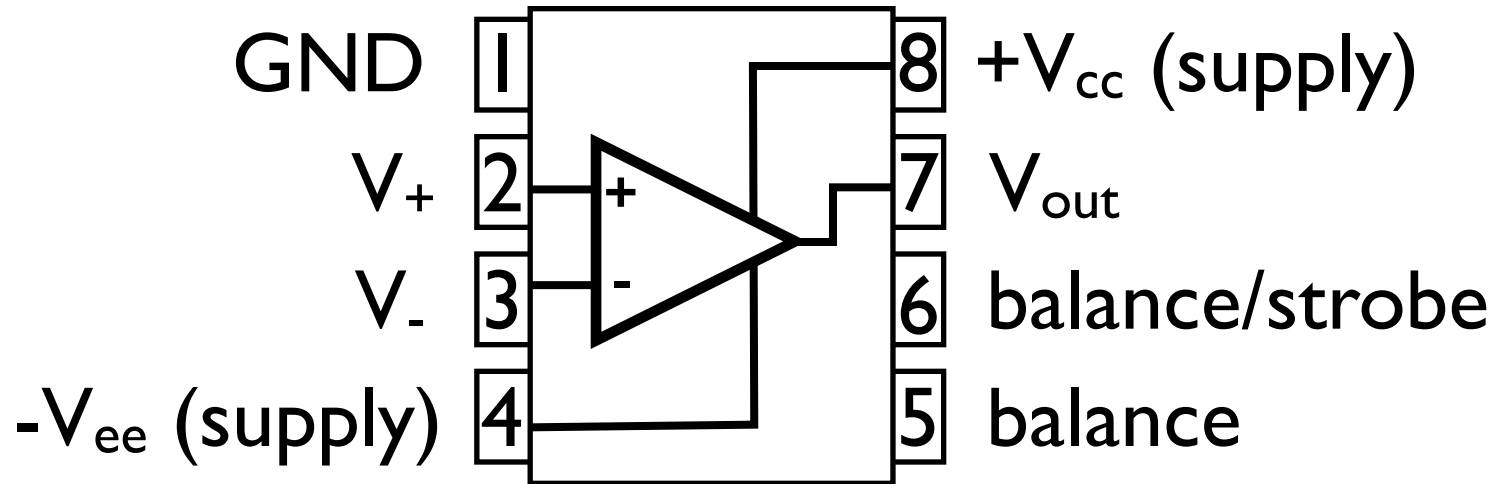

come in double & quad packages (L339)

what to do with them?

threshold detection

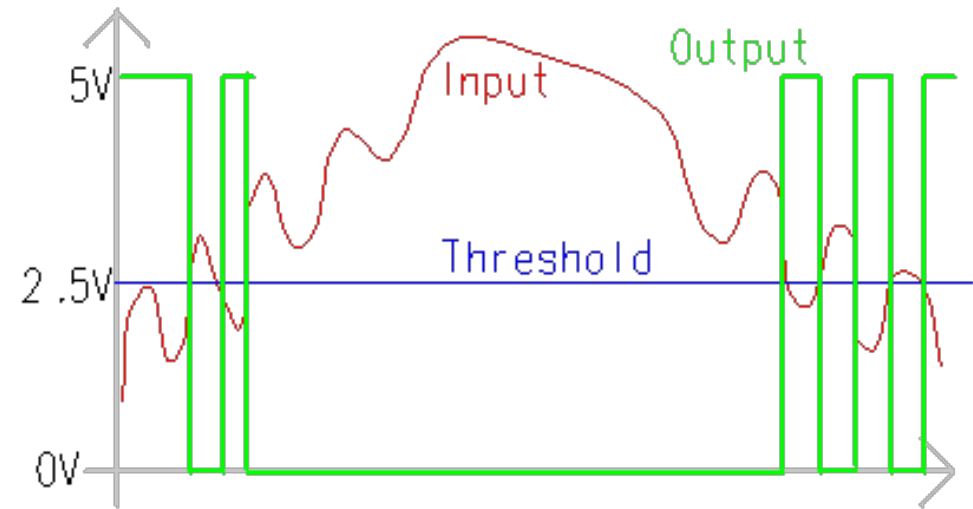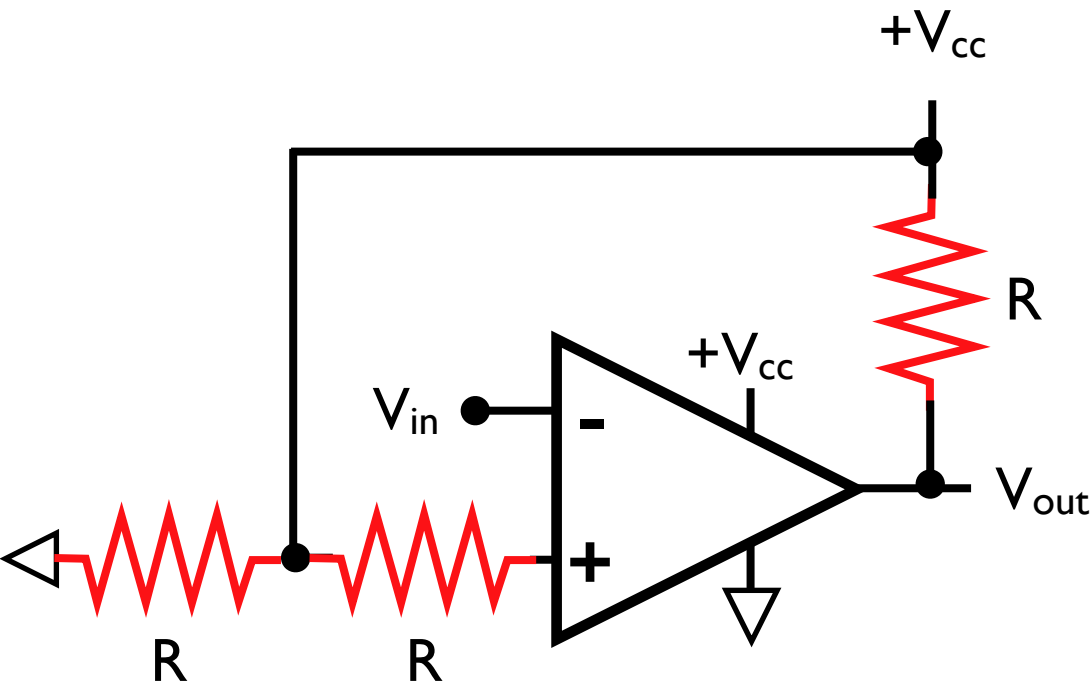

$$V_{out} = \begin{cases} V_{cc}, & V_{in} > V_{cc}/2 \\ 0, & V_{in} < V_{cc}/2 \end{cases}$$

divider ensures $V_{+} = V_{cc}/2$ (threshold)

negative input: $V_{-} = V_{in}$


if $V_{in} < V_{cc}/2$, output is at negative supply (GND)

if $V_{in} > V_{cc}/2$, output floating (pulled up by 10k to V_{cc})

V_{-} could just be a switch/photoR/transducer connected to V_{cc} !

disadvantage: sharp threshold gives 'bouncing' near transition. need some hysteresis ...

zero crossing detector

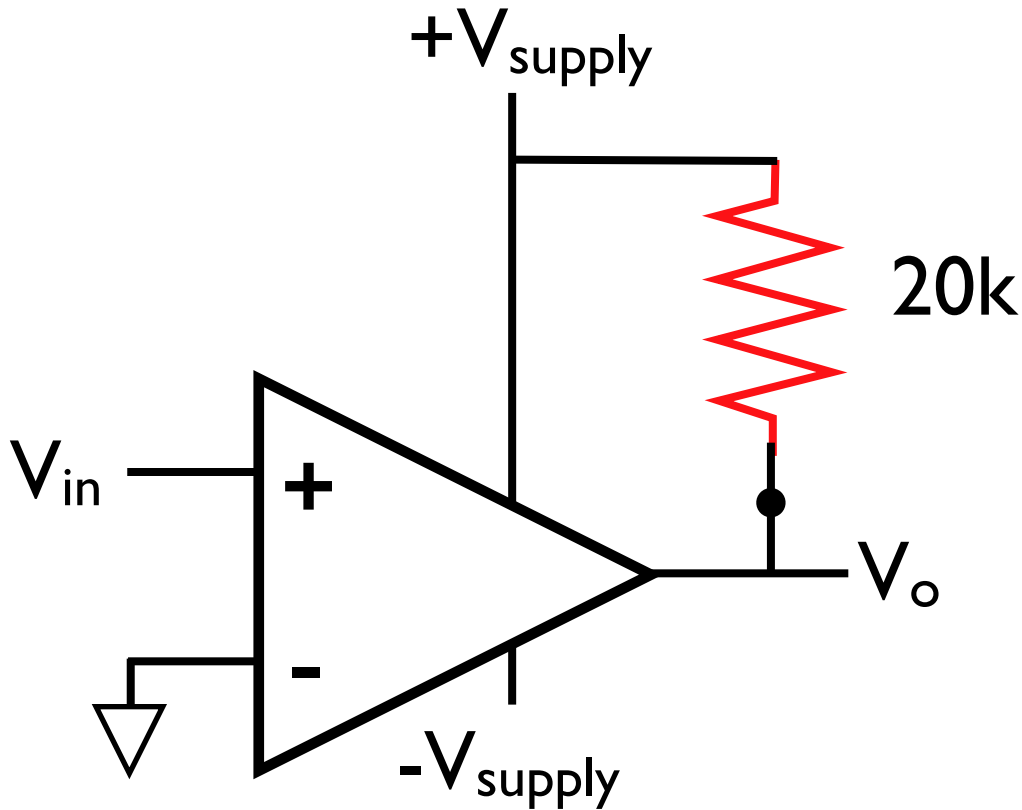

if $V_{in} > 0$, output is floating
but 20k to supply 'pulls up'


if $V_{in} < 0$, output is at $-V_{supply}$
but also pulled up

ground neg supply, 0/1 sig

some uses for comparators


- switching/amp (drive base of transistor)
- A/D conversion & interfacing
- pulse width modulation
- threshold/level detection
- use of feedback allows much more
 - memory (flip-flop, last state?)
 - hysteresis - better regulation (thermostat)
 - oscillators (intermittent wipers)

relaxation oscillator

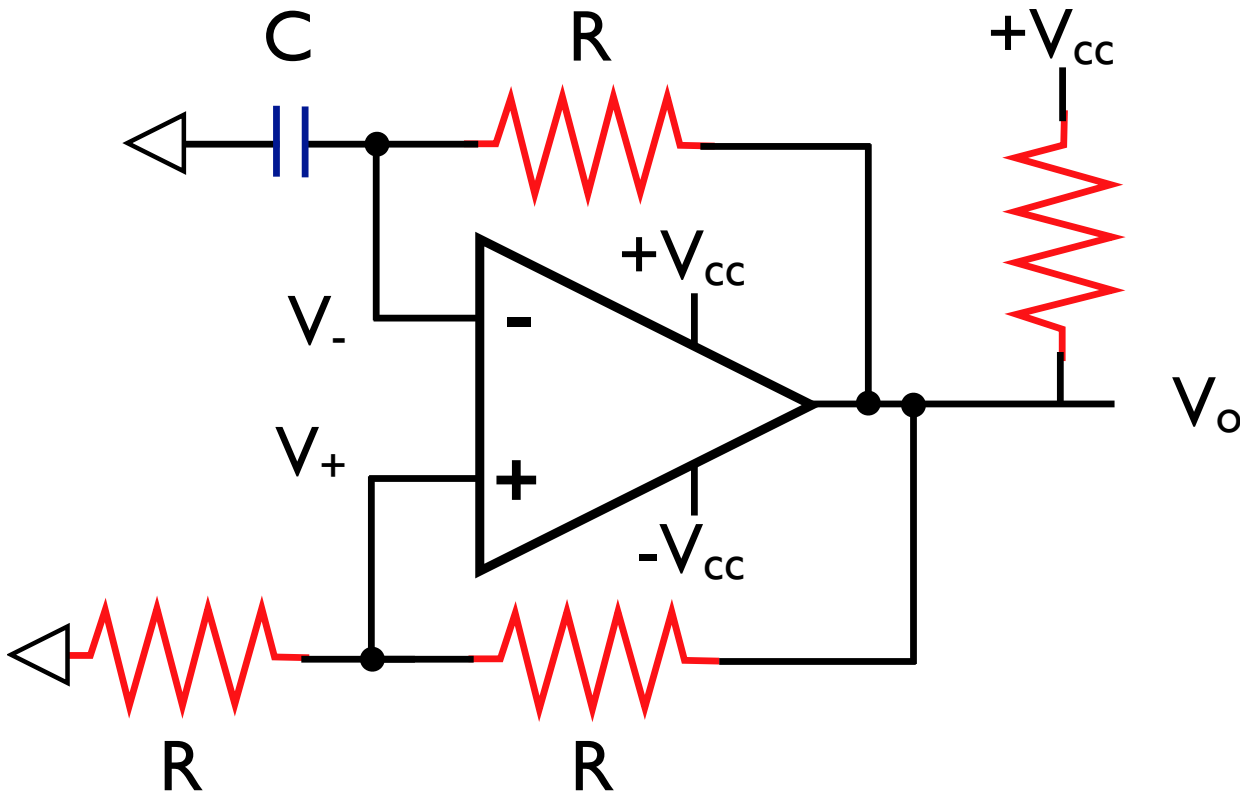


WTF?

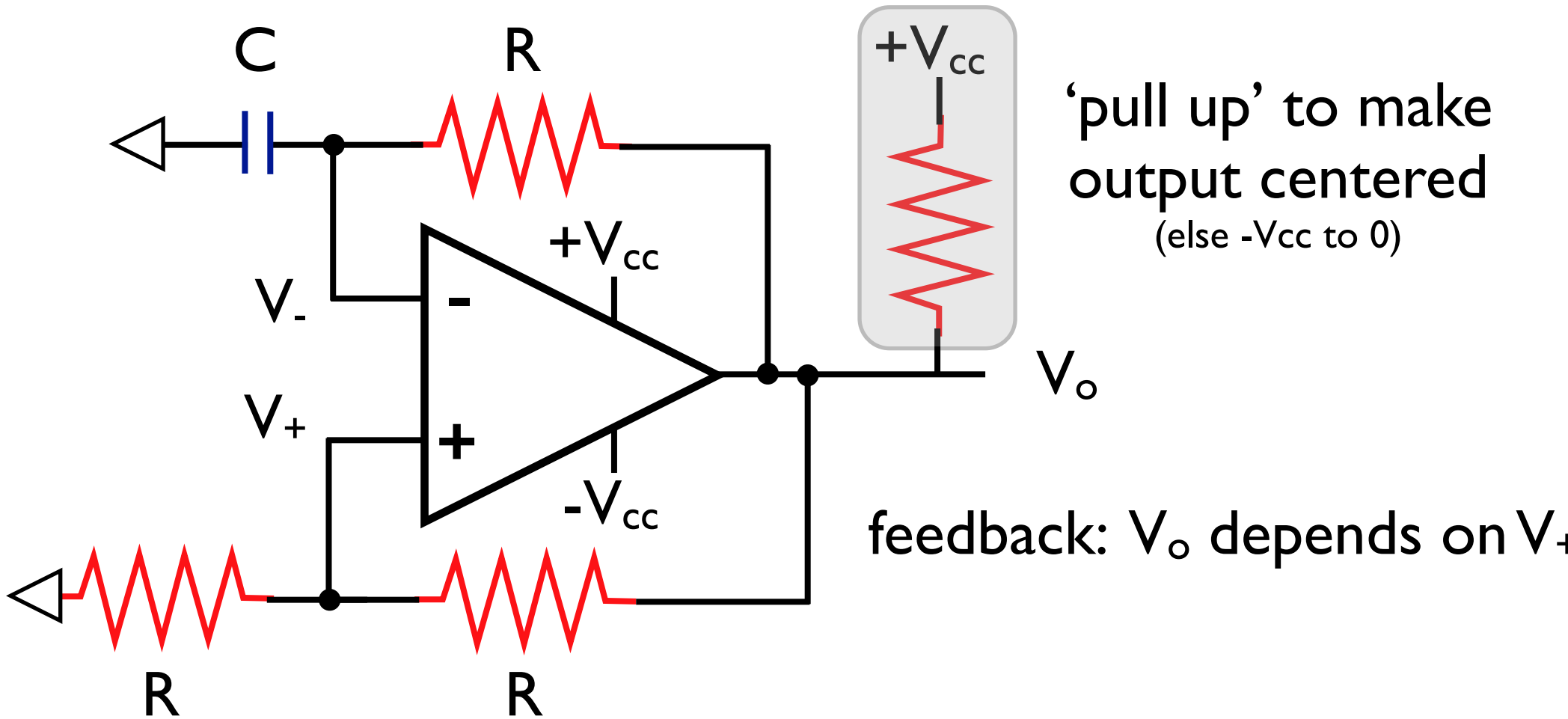use C charge
as comparator input
compare to fixed ref
output feeds back to RC



V_+ is fixed by voltage divider at $V_o/2 = (+/-)V_{cc}/2$
 since inputs draw no current, R and C currents same
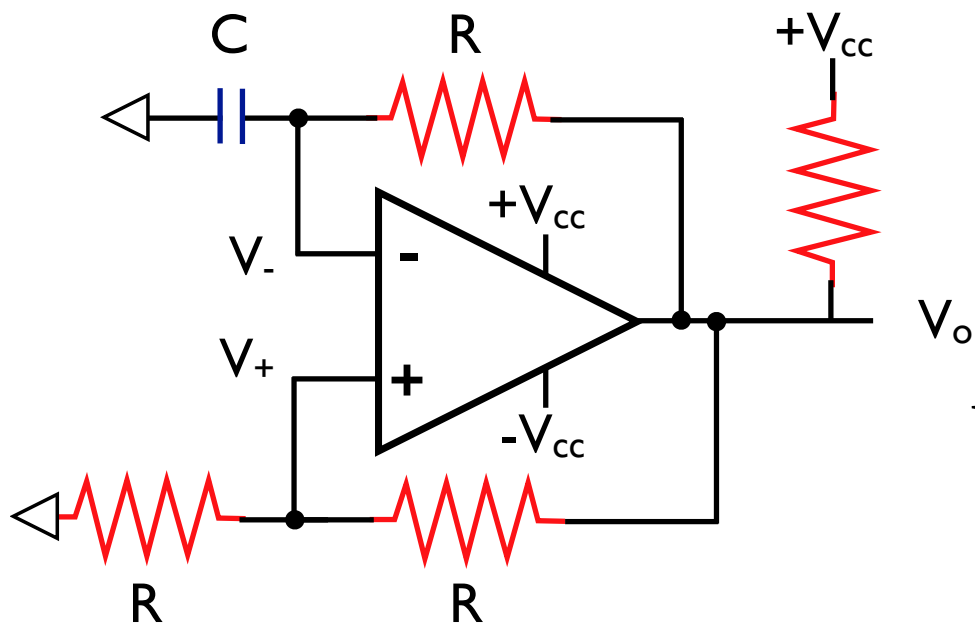
$$C \frac{dV_-}{dt} = \frac{V_o - V_-}{R} \quad \frac{dV_-}{dt} + \frac{V_-}{RC} = \frac{V_o}{RC}$$



$$\frac{dV_-}{dt} + \frac{V_-}{RC} = \frac{V_o}{RC}$$

general solution:

$$V_- = A + Be^{-t/RC} = V_o + Be^{-t/RC}$$

(steady state, $V_- = V_o$)

V_+ is fixed at $V_{cc}/2$; when $V_- < V_{cc}/2$ output goes to $-V_{cc}$
 this discharges C toward $-V_{cc}$ and makes $V_+ = -V_{cc}/2$

when V_- reaches $-V_{cc}/2$:


$V_- < V_+$ and output goes high (pull-up); this charges C

once V_- reaches $V_{cc}/2$

$V_+ < V_-$ so output goes low, discharging C ... starts over

C cycles between $-V_{cc}/2$ and $V_{cc}/2$

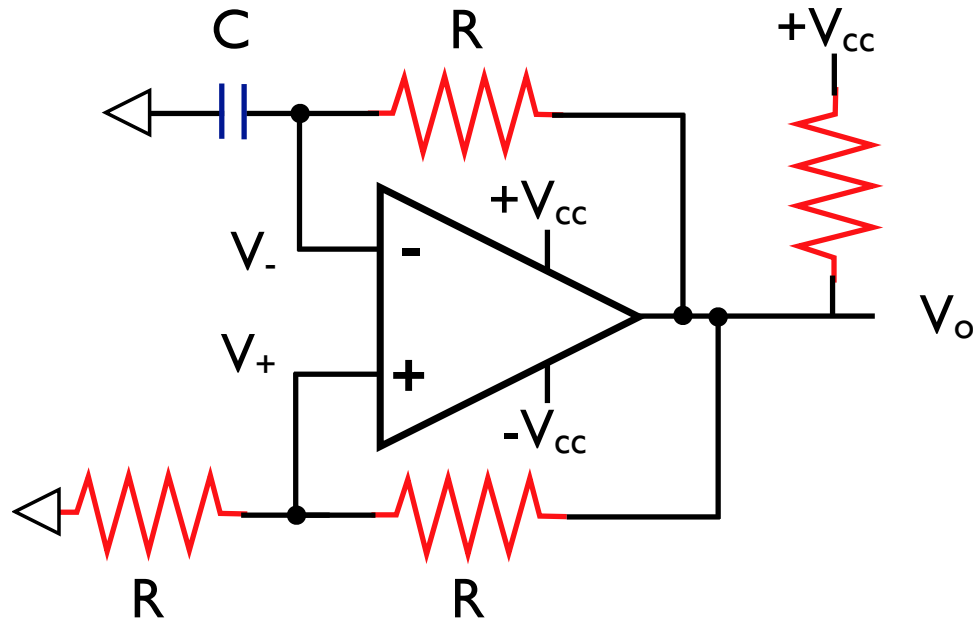this is a half period
we know capacitor $V(t)$!



at $t=0, V_- = -V_{cc}/2$


$$V_- = V_{cc} - \frac{3}{2}V_{cc}e^{-t/RC}$$

time for $V_- = +V_{cc}/2$
is half period ($T/2$)


$$\frac{V_{cc}}{2} = V_{cc} \left(1 - \frac{3}{2}e^{-(T/2)/RC} \right)$$

period is thus:


$$T = 2RC \ln 3$$

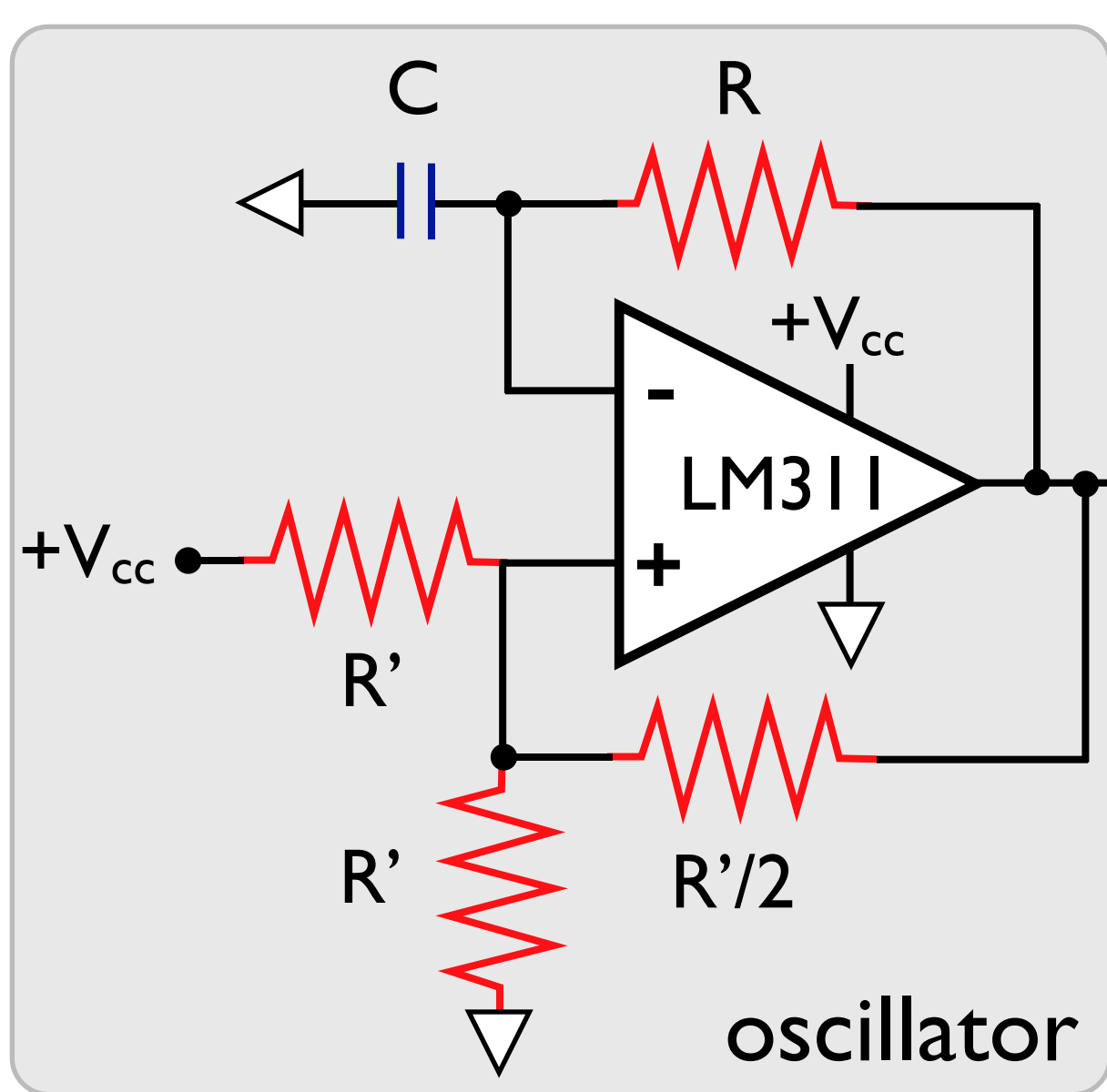

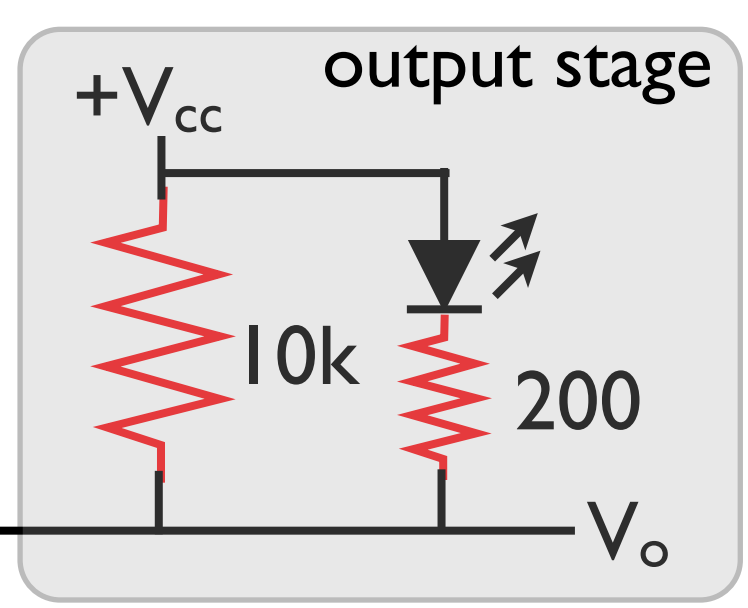pick $RC \sim 0.1-2$ sec
 $R, R' \sim 10k-100k$
 $C \sim \mu F$
 $V_{cc} = 5V$



LED flasher

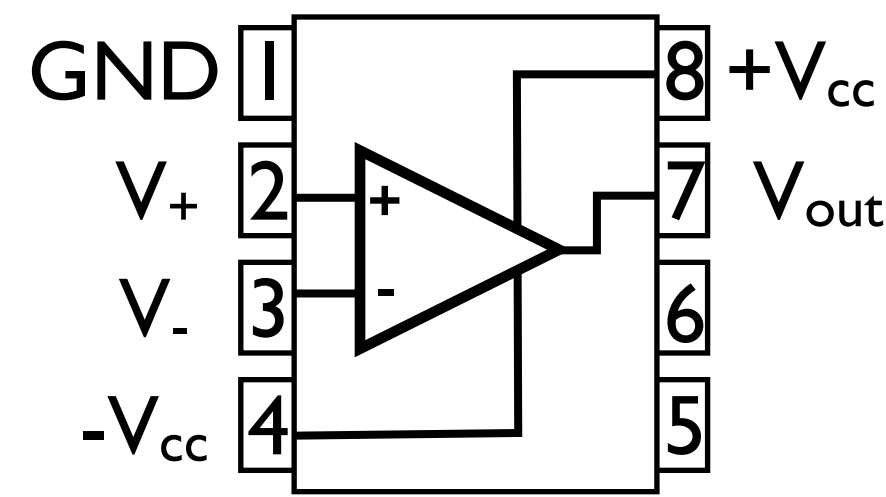

the lab

- build a relaxation oscillator to drive an LED or speaker
 - LED: $< 40\text{Hz}$ or so to see
 - speaker: $\sim 100\text{Hz}-10\text{kHz}$ to hear
- make Arduino count every Nth cycle